

# **Chapter #6: Sequential Logic Design**


## ***Contemporary Logic Design***

**Randy H. Katz  
University of California, Berkeley**


**June 1993**
 
## **Chapter Overview**

- ***Sequential Networks***  
Simple Circuits with Feedback  
R-S Latch  
J-K Flipflop  
Edge-Triggered Flipflops
- ***Timing Methodologies***  
Cascading Flipflops for Proper Operation  
Narrow Width Clocking vs. Multiphase Clocking  
Clock Skew
- ***Realizing Circuits with Flipflops***  
Choosing a FF Type  
Characteristic Equations  
Conversion Among Types
- ***Metastability and Asynchronous Inputs***
- ***Self-Timed Circuits***



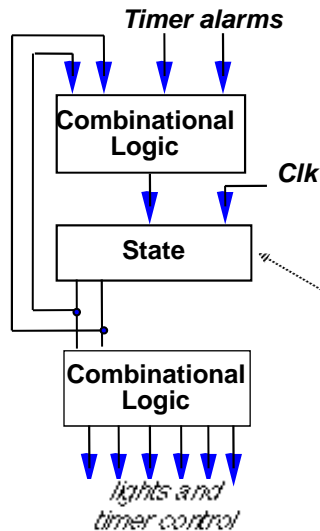Circuits with Feedback:  
Some outputs are also inputs



Traffic Light Controller is a complex sequential logic network

Sequential logic forms basis for building "memory" into circuits

These memory elements are primitive sequential circuits

## Sequential Switching Networks


### Simple Circuits with Feedback

Primitive memory elements created from cascaded gates

Simplest gate component: inverter


Basis for commercial static RAM designs

 Cross-coupled NOR gates and NAND gates also possible




Cascaded Inverters: Static Memory Cell

 Selectively break feedback path to load new value into cell




## Inverter Chains

 

Odd # of stages leads to ring oscillator  
Snapshot taken just before last inverter changes


Output high propagating thru this stage

## Timing Waveform:

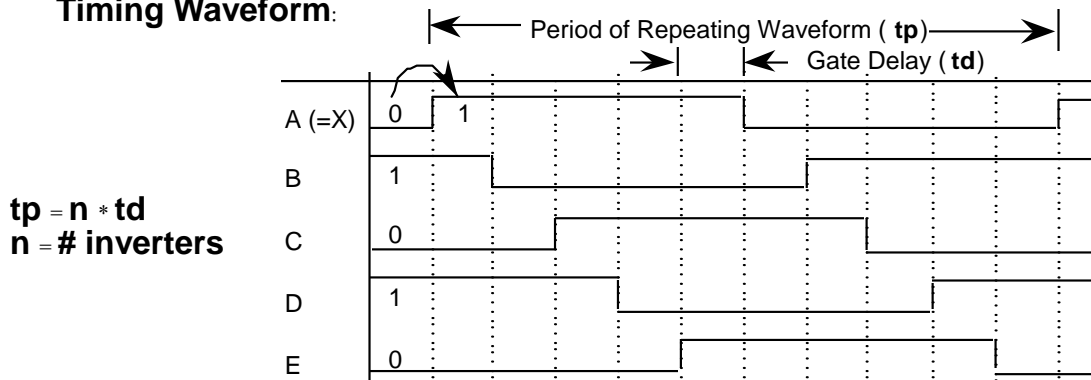


# Sequential Switching Networks

## Inverter Chains

 


Propagation of Signals through the Inverter Chain


## Cross-Coupled NOR Gates

 

 Just like cascaded inverters,  
with capability to force output  
to 0 (reset) or 1 (set)




## Timing Waveform

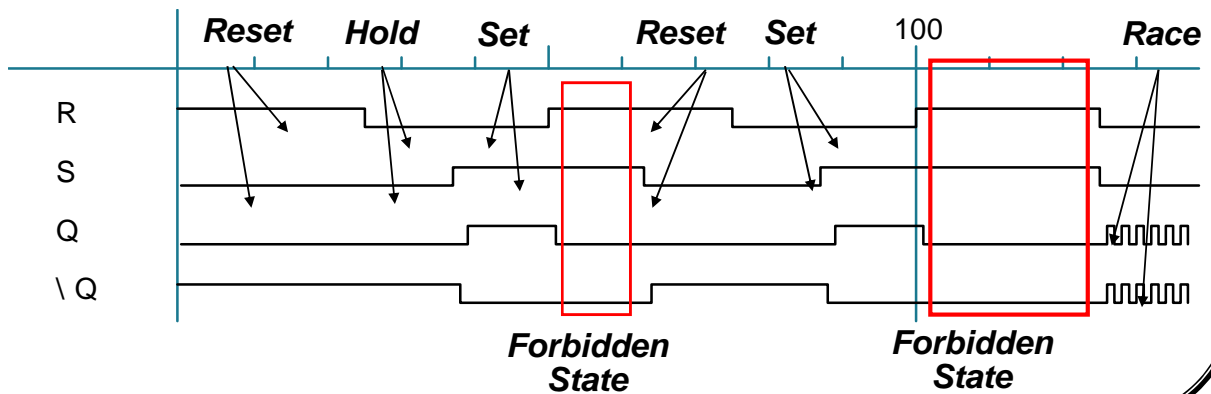




R.H. Katz Transparency No. 6-7

## State behavior or R-S latch

 

### • Truth table of R-S latch behavior

S	R	Q
0	0	hold
0	1	0
1	0	1
1	1	unstable

   





R.H. Katz Transparency No. 6-8

## Sequential Switching Networks


### State Behavior of R-S Latch

S	R	Q
0	0	hold
0	1	0
1	0	1
1	1	unstable

    Truth Table Summary  
of R-S Latch Behavior




## Theoretical R-S latch behavior

 

 
### State diagram

- states: possible values
- transitions: changes based on inputs


possible oscillation  
between states 00 and 11




## Theoretical R-S Latch State Diagram

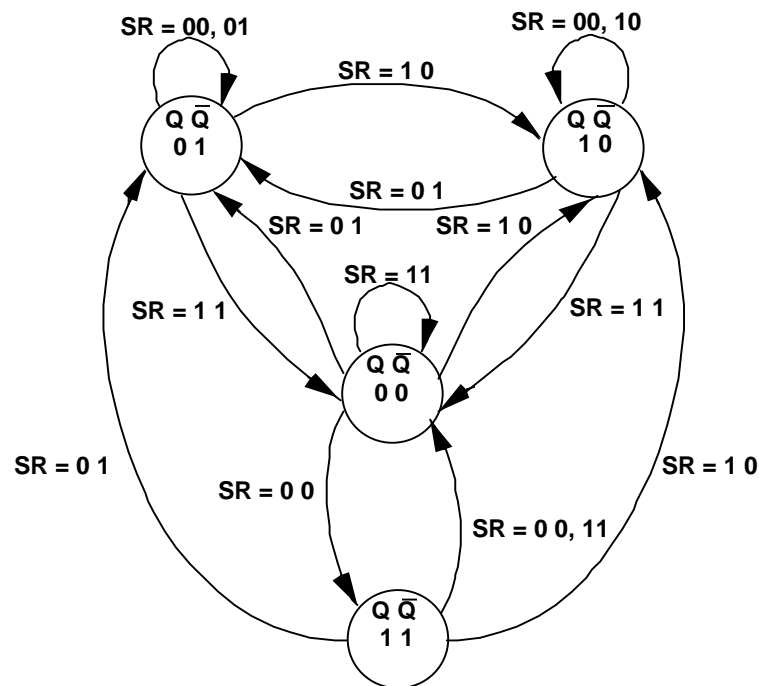


## Observed R-S latch behavior

 

 - **Very difficult to observe R-S latch in the 1-1 state**
  - one of  $R$  or  $S$  usually changes first
- **Ambiguously returns to state 0-1 or 1-0**
  - a so-called "race condition"
  - or non-deterministic transition



## Observed R-S Latch Behavior

 


Very difficult to observe R-S Latch in the 1-1 state

Ambiguously returns to state 0-1 or 1-0

A so-called "race condition"

# Sequential Switching Networks

## Definition of Terms

 

**Clock:**

Periodic Event, causes state of memory element to change

rising edge, falling edge, high level, low level

**Setup Time ( $T_{su}$ )**

Minimum time before the clocking event by which the input must be stable


**Hold Time ( $T_h$ )**

Minimum time after the clocking event during which the input must remain stable


There is a timing "window" around the clocking event during which the input must remain stable and unchanged in order to be recognized

### Level-Sensitive Latch aka Gated R-S Latch

Schematic:

 


Timing Diagram:

 
 
## Clocks


- **Used to keep time**
  - wait long enough for inputs (R' and S') to settle
  - then allow to have effect on value stored
- **Clocks are regular periodic signals**
  - period (time between ticks)
  - duty-cycle (time clock is high between ticks - expressed as % of period)




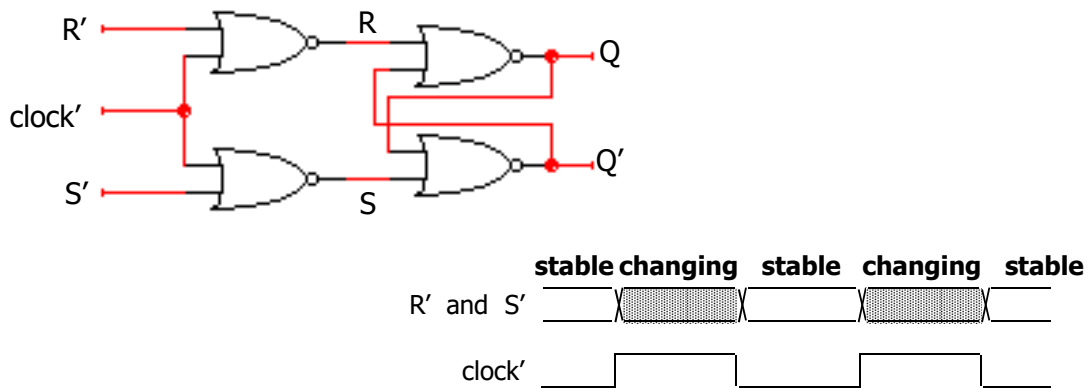
### Controlling an R-S latch with a clock

- can't let R and S change while clock is active (allowing R and S to pass)
- only have half of clock period for signal changes to propagate
- signals must be stable for the other half of clock period




## Sequential Switching Networks

### Latches vs. Flipflops


#### Input/Output Behavior of Latches and Flipflops

Type	When Inputs are Sampled	When Outputs are Valid
unclocked latch	always	propagation delay from input change
level sensitive latch	clock high ( $T_{su}$ , $T_h$ around falling clock edge)	propagation delay from input change
positive edge flipflop	clock lo-to-hi transition ( $T_{su}$ , $T_h$ around rising clock edge)	propagation delay from rising edge of clock
negative edge flipflop	clock hi-to-lo transition ( $T_{su}$ , $T_h$ around falling clock edge)	propagation delay from falling edge of clock
master/slave flipflop	clock hi-to-lo transition ( $T_{su}$ , $T_h$ around falling clock edge)	propagation delay from falling edge of clock

 


**Edge triggered device sample inputs on the event edge**

 **Transparent latches sample inputs as long as the clock is asserted**



**Timing Diagram:**

 


**Behavior the same unless input changes while the clock is high**

## Sequential Switching Elements

**Typical Timing Specifications: Flipflops vs. Latches**

 **74LS74 Positive Edge Triggered D Flipflop**

- Setup time
- Hold time
- Minimum clock width
- Propagation delays (low to high, high to low, max and typical)




**All measurements are made from the clocking event that is, the *rising edge* of the clock**

## Typical Timing Specifications: Flipflops vs. Latches
 
### 74LS76 Transparent Latch

- Setup time
- Hold time
- Minimum Clock Width
- Propagation Delays:  
high to low, low to high,  
maximum, typical  
clock to output



Measurements from falling clock edge  
or rising or falling data edge

# Sequential Switching Elements

## R-S Latch Revisited

Truth Table:  
Next State =  $F(S, R, \text{Current State})$


S	R	Q(t)	Q(t+Δ)	
0	0	0	0	hold
0	0	1	1	
0	1	0	0	reset
0	1	1	0	
1	0	0	1	set
1	0	1	1	
1	1	0	X	not allowed
1	1	1	X	

Derived K-Map:

SR		S			
		00	01	11	10
Q(t)	0	0	0	X	1
	1	1	0	X	1
		R			

Characteristic Equation:

$$Q_+ = S + R \bar{Q}_t$$

 


## Sequential Switching Networks

### J-K Flipflop

How to eliminate the forbidden state?

Idea: use output feedback to guarantee that R and S are never both one

J, K both one yields toggle

 


J(t)	K(t)	Q(t)	Q(t+Δ)	
0	0	0	0	Hold
0	0	1	1	
0	1	0	0	Reset
0	1	1	0	
1	0	0	1	Set
1	0	1	1	
1	1	0	1	Toggle
1	1	1	0	

Characteristic Equation:

$$Q_+ = Q K' + Q J$$

## Sequential Switching Networks

### J-K Latch: Race Condition

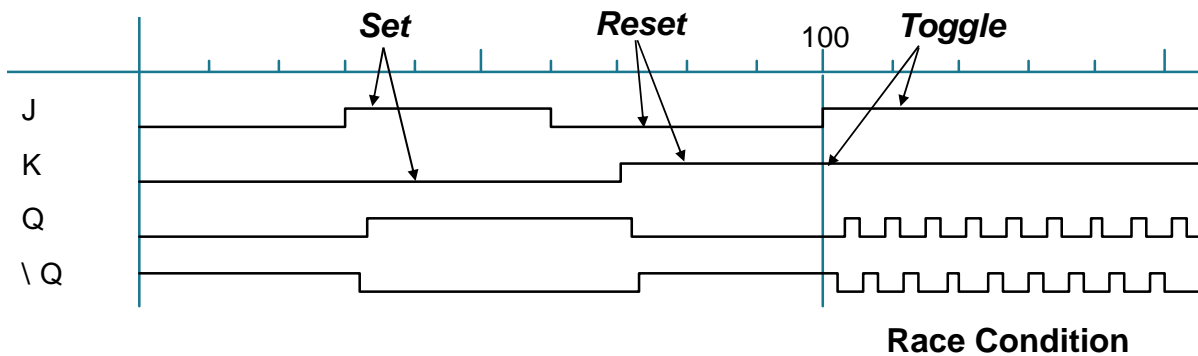



Toggle Correctness: Single State change per clocking event

Solution: Master/Slave Flipflop

## Sequential Switching Network

Contemporary Logic Design  
Sequential Logic

### Master/Slave J-K Flipflop

 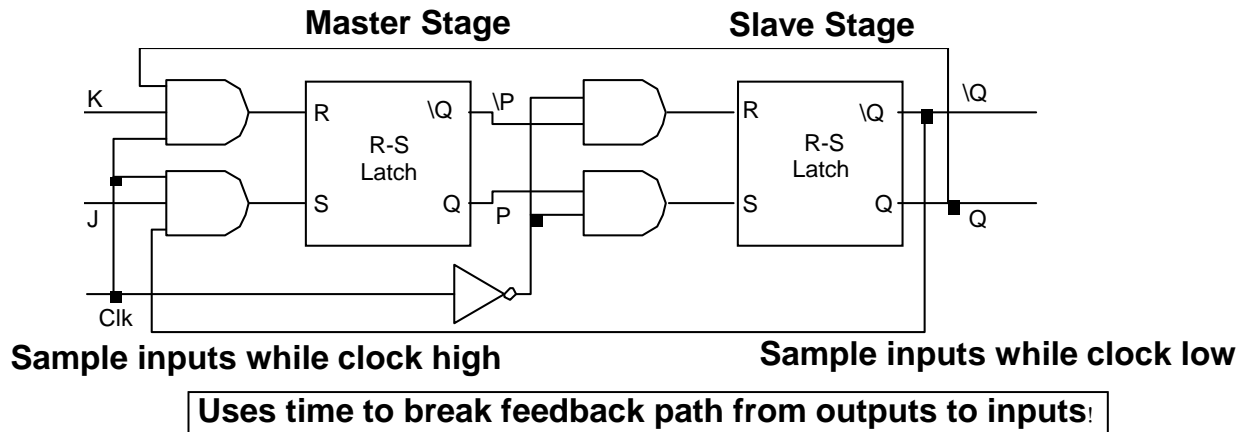

**Correct Toggle Operation**

© R.H. Katz Transparency No. 6-25


## Sequential Switching Networks

Contemporary Logic Design  
Sequential Logic

### Edge-Triggered Flipflops

**1's Catching:** a 0-1-0 glitch on the J or K inputs leads to a state change!  
forces designer to use hazard-free logic

**Solution:** edge-triggered logic

 

**Negative Edge-Triggered D flipflop**

**4-5 gate delays**

**setup, hold times  
necessary to successfully  
latch the input**


**Characteristic Equation:**

$$Q_{+} = D$$


© R.H. Katz Transparency No. 6-26

## Edge-triggered Flipflops

### Step-by-step analysis

 

 
**Negative edge-triggered FF**  
when clock goes high-to-low  
data is latched



**Negative edge-triggered FF**  
when clock is low  
data is held

# Sequential Switching Networks
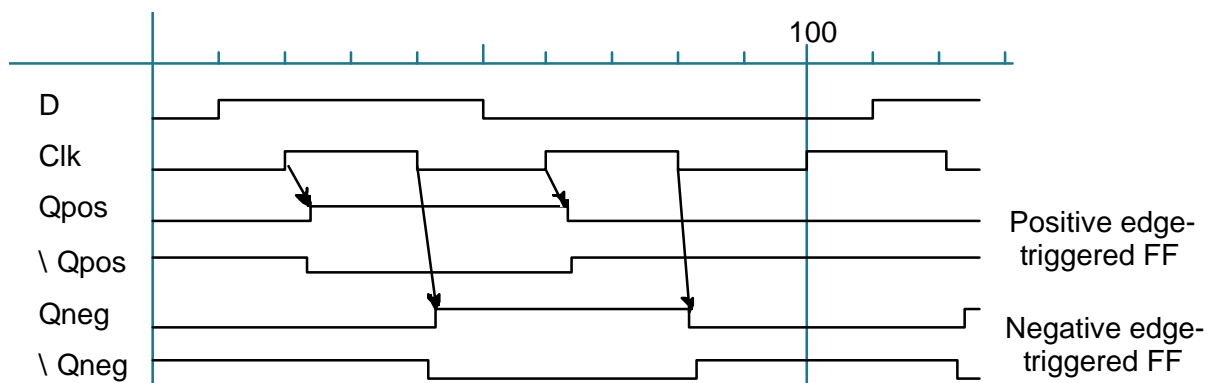
## Positive vs. Negative Edge Triggered Devices



### Positive Edge Triggered

Inputs sampled on rising edge  
Outputs change after rising edge

### Negative Edge Triggered

Inputs sampled on falling edge  
Outputs change after falling edge

### Toggle Flipflop

Formed from J-K with both inputs wired together

## Timing Methodology

### Overview

- Set of rules for interconnecting components and clocks
- When followed, guarantee proper operation of system
- Approach depends on building blocks used for memory elements

*For systems with latches:*

Narrow Width Clocking

Multiphase Clocking (e.g., Two Phase Non-Overlapping)

*For systems with edge-triggered flipflops:*

Single Phase Clocking

- Correct Timing:


- (1) correct inputs, with respect to time, are provided to the FFs
- (2) no FF changes more than once per clocking event

## Timing Methodologies

 
### Cascaded Flipflops and Setup/Hold/Propagation Delays

Shift Register  
S,R are preset, preclear

New value to first stage  
while second stage  
obtains current value  
of first stage



 Correct Operation,  
assuming positive  
edge triggered FF




## Timing Methodologies
 
### Cascaded Flipflops and Setup/Hold/Propagation Delays

Why this works:

- Propagation delays far exceed hold times;  
Clock width constraint exceeds setup time
- This guarantees following stage will latch current value  
before it is replaced by new value
- Assumes infinitely fast distribution of the clock




Timing constraints  
guarantee proper  
operation of  
cascaded components

## Timing Methodologies
 
### Narrow Width Clocking versus Multiphase Clocking

Level Sensitive Latches vs. Edge Triggered Flipflops

- Latches use fewer gates to implement a memory function
- Less complex clocking with edge triggered devices



#### CMOS Dynamic Storage Element

Feedback path broken by two  
phases of the clock  
(just like master/slave idea!)

8 transistors to implement memory function  
but requires two clock signals constrained  
to be non-overlapping

Edge-triggered D-FF: 6 gates (5 x 2-input, 1 x 3-input) = 26 transistors!




## Timing Methodologies

### Narrow Width Clocking for Systems with Latches for State
 
#### Generic Block Diagram for Clocked Sequential System

state implemented by  
latches or edge-triggered FFs



Two-sided Constraints:  
must be careful of very fast signals as well as very slow signals!





Clock Width < fastest propagation through comb. logic  
plus latch prop delay

Clock Period > slowest propagation through comb. logic  
(rising edge to rising edge)

## Timing Methodologies
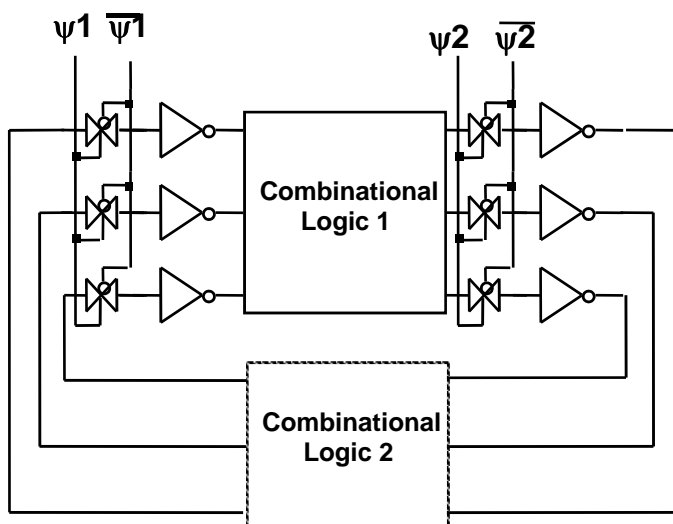 
### Two Phase Non-Overlapped Clocking

Clock Waveforms:  
must never overlap!  
only worry about slow signals



#### Embedding CMOS storage element into Clocked Sequential Logic


Note that Combinational Logic  
can be partitioned into two  
pieces

C/L1: inputs latched and stable  
by end of phase 1; compute  
between phases, latch outputs  
by end of phase 2

C/L2: just the reverse

## Timing Methodologies
 
### Generating Two-Phase Non-Overlapping Clocks




**Single reference clock (or crystal)**

**Phase 1 high while clock is low**

 **Phase 2 high while clock is high**

**Phase X cannot go high until  
phase Y goes low!**



**Non-overlap time can be increased by increasing the delay on  
the feedback path**

## Timing Methodologies


### The Problem of Clock Skew

**Correct behavior assumes next state of all storage elements  
determined by all storage elements *at the same time***

**Not possible in real systems!**

- logical clock driven from more than one physical circuit with timing behavior
- different wire delay to different points in the circuit

 **Effect of Skew on Cascaded Flipflops:**



**Original State:  $Q_0 = 1$ ,  $Q_1 = 1$ ,  $In = 0$**

**Because of skew, next state becomes:  $Q_0 = 0$ ,  $Q_1 = 0$ ,  
not  $Q_0 = 0$ ,  $Q_1 = 1$**

## Timing Methodologies

### *Design Strategies for Minimizing Clock Skew*

Typical propagation delays for LS FFs: 13 ns

Need substantial clock delay (on the order of 13 ns) for skew to be a problem in this relatively slow technology

Nevertheless, the following are good design practices:

- distribute clock signals in general direction of data flows
- wire carrying the clock between two communicating components should be as short as possible
- for multiphase clocked systems, distribute all clocks in similar wire paths; this minimizes the possibility of overlap
- for the non-overlap clock generate, use the phase feedback signals from the furthest point in the circuit to which the clock is distributed; this guarantees that the phase is seen as low everywhere before it allows the next phase to go high

## Realizing Circuits with Different Kinds of FFs

### *Choosing a Flipflop*

**R-S Clocked Latch:**

used as storage element in narrow width clocked systems  
its use is not recommended!  
however, fundamental building block of other flipflop types

**J-K Flipflop:**

versatile building block  
can be used to implement D and T FFs  
usually requires least amount of logic to implement (In, Q, Q+)  
but has two inputs with increased wiring complexity

because of 1's catching, never use master/slave J-K FFs  
edge-triggered varieties exist

**D Flipflop:**

minimizes wires, much preferred in VLSI technologies  
simplest design technique  
best choice for storage registers

**T Flipflops:**

don't really exist, constructed from J-K FFs  
usually best choice for implementing counters

Preset and Clear inputs highly desirable!!

## Characteristic Equations

R-S:  $Q_+ = S + R \bar{Q}$

D:  $Q_+ = D$

J-K:  $Q_+ = J \bar{Q} + K Q$

T:  $Q_+ = T \bar{Q} + T Q$

Derived from the K-maps for  $Q_+ = (Inputs, Q)$


E.g., J=K=0, then  $Q_+ = Q$

J=1, K=0, then  $Q_+ = 1$

J=0, K=1, then  $Q_+ = 0$

J=1, K=1, then  $Q_+ = \bar{Q}$
 
## Implementing One FF in Terms of Another



# Realizing Circuits with Different Kinds of Flipflops

## Design Procedure


Excitation Tables: What are the necessary inputs to cause a particular kind of change in state?

Q	Q <sup>+</sup>	R	S	J	K	T	D
0	0	X	0	0	X	0	0
0	1	0	1	1	X	1	1
1	0	1	0	X	1	1	0
1	1	0	X	X	0	0	1

Implementing D FF with a J-K FF:

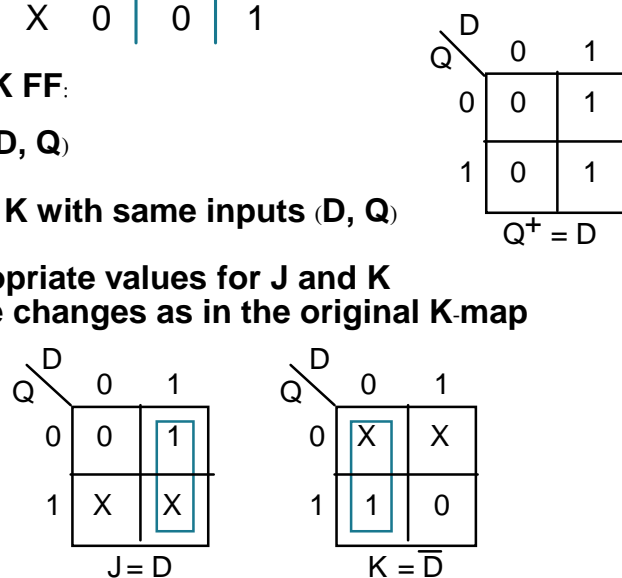- 1) Start with K-map of  $Q_+ = (D, Q)$
- 2) Create K-maps for J and K with same inputs (D, Q)
- 3) Fill in K-maps with appropriate values for J and K to cause the same state changes as in the original K-map

E.g., D = Q = 0,  $Q_+ = 0$   
then J = 0, K = X



**Design Procedure (Continued)****Implementing J-K FF with a D FF:****1) K-Map of  $Q^+ = F(J, K, Q)$** **2,3) Revised K-map using D's excitation table****its the same! that is why design procedure with D FF is simple!**

		J			
		JK		11	10
Q	0	0	0	1	1
	1	1	0	0	1

$$Q^+ = D = J\bar{Q} + \bar{K}Q$$

**Resulting equation is the combinational logic input to D to cause same behavior as J-K FF. Of course it is identical to the characteristic equation for a J-K FF.**

**Metastability and Asynchronous Inputs****Terms and Definitions****Clocked synchronous circuits**

- common reference signal called the clock
- state of the circuit changes in relation to this clock signal

**Asynchronous circuits**

- inputs, state, and outputs sampled or changed independent of a common reference signal

**R-S latch is asynchronous, J-K master/slave FF is synchronous****Synchronous inputs**

- active only when the clock edge or level is active

**Asynchronous inputs**

- take effect immediately, without consideration of the clock

**Compare R, S inputs of clocked transparent latch vs. plain latch**

## Metastability and Asynchronous Inputs

### *Asynchronous Inputs Are Dangerous:*



Since they take effect immediately, glitches can be disastrous

Synchronous inputs are greatly preferred!

But sometimes, asynchronous inputs cannot be avoided  
e.g., reset signal, memory wait signal

## Metastability and Asynchronous Outputs

### *Handling Asynchronous Inputs*

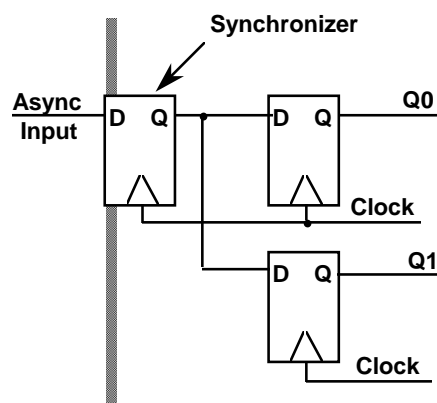 


Never allow asynchronous inputs to be fanned out to more than one FF within the synchronous system

## Metastability and Asynchronous Inputs

Contemporary Logic Design  
Sequential Logic

### What Can Go Wrong

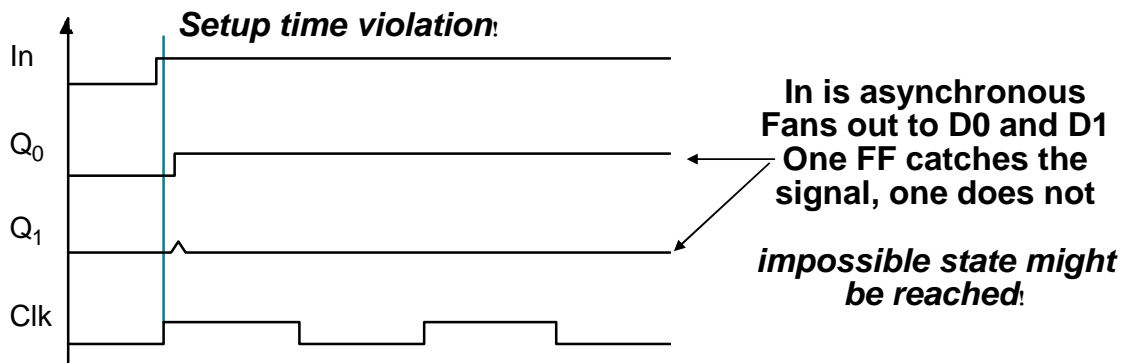


Single FF that receives the asynchronous signal is a *synchronizer*

R.H. Katz Transparency No. 6-45

## Metastability and Asynchronous Inputs


Contemporary Logic Design  
Sequential Logic

### Synchronizer Failure

 


When FF input changes close to clock edge, the FF may enter the *metastable* state: neither a logic 0 nor a logic 1

 It may stay in this state an indefinite amount of time, although this is not likely in real circuits



 Small, but non-zero probability that the FF output will get stuck in an in-between state




Oscilloscope Traces Demonstrating Synchronizer Failure and Eventual Decay to Steady State

R.H. Katz Transparency No. 6-46

## Metastability and Asynchronous Inputs
 
### **Solutions to Synchronizer Failure**

- the probability of failure can never be reduced to 0, but it can be reduced
- slow down the system clock  
this gives the synchronizer more time to decay into a steady state  
synchronizer failure becomes a big problem for very high speed systems
- use fastest possible logic in the synchronizer  
this makes for a very sharp "peak" upon which to balance  
S or AS TTL D-FFs are recommended
- cascade two synchronizers




## Self-Timed and Speed Independent Circuits

### **Limits of Synchronous Systems**


Fully synchronous not possible for very large systems  
because of problems of clock skew

Partition system into components that are locally clocked

 These communicate using "speed independent" protocols



 
### **Request/Acknowledgement Signaling**






### **Synchronous Signaling**

 

 **Master issues read request; Slave produces data and acks back**



**Alternative Synchronous Scheme:**


**Slave issues WAIT signal if it cannot satisfy request in one clock cycle**

### **Asynchronous/Speed Independent Signaling**

**Communicate information by signal levels rather than edges!**

**No clock signal**
 
### **4 Cycle Signaling/Return to Zero Signaling**



(1) master raises request  
slave performs request

(2) slave "done" by raising  
acknowledge


(3) master latches data  
acks by lowering request

(4) slave resets self by lowering  
acknowledge signal

## Self-Timed and Speed Independent Circuits

### *Alternative: 2 cycle signaling*

#### Non-Return-to-Zero

 

- (1) master raises request  
slave services request
- (2) slave indicates that it is  
done by raising acknowledge

Next request indicated by low level of request

Requires additional state in master and slave  
to remember previous setting or request/acknowledge

4 Cycle Signaling is more foolproof


## Self-Timed and Speed Independent Circuits

### *Self-Timed Circuits*

Determine on their own when a given request has been serviced

No internal clocks

 Usually accomplished by modeling worst case delay within  
self-timed component



Models worst case delay  
e.g., if combinational logic is 5 gate levels deep,  
delay line between request in and ack out is  
also 5 levels deep

## **Chapter Summary**

- **Fundamental Building Block of Circuits with State: latch and flipflop**
- **R-S Latch, J-K master/slave Flipflop, Edge-triggered D Flipflop**
- **Clocking Methodologies:**

**For latches: Narrow width clocking vs. Multiphase Non-overlapped  
Narrow width clocking and two sided timing constraints  
Two phase clocking and single sided timing constraints**

**For FFs: Single phase clocking with edge triggered flipflops**

**Cascaded FFs work because propagation delays exceed hold times**

**Beware of Clock Skew**

- **Asynchronous Inputs and Their Dangers**

**Synchronizer Failure: What it is and how to minimize its impact**

- **Speed Independent Circuits**

**Asynchronous Signaling Conventions: 4 and 2 Cycle Handshakes**

**Self-Timed Circuits**