

Chapter # 3: Multi-Level Combinational Logic

Contemporary Logic Design

**Randy H. Katz
University of California, Berkeley**

June 1993

Chapter Overview

- ***Multi-Level Logic***

Conversion to NAND-NAND and NOR-NOR Networks

DeMorgan's Law and Pushing Bubbles

AND-OR-Invert Building Blocks

CAD Tools for Multi-Level Optimization

- ***Time Response in Combinational Networks***



Gate Delays and Timing Waveforms

Hazards/Glitches and How To Avoid Them

Reduced sum of products form:

$$x = A D F + A E F + B D F + B E F + C D F + C E F + G$$

  6 x 3-input AND gates + 1 x 7-input OR gate (may not exist!)
25 wires (19 literals plus 6 internal wires)



Factored form:

$$x = (A + B + C)(D + E)F + G$$

1 x 3-input OR gate, 2 x 2-input OR gates,
1 x 3-input AND gate
10 wires (7 literals plus 3 internal wires)

Multi-Level Logic: Conversion of Forms

NAND-NAND and NOR-NOR Networks

DeMorgan's Law: $(A + B)' = A' \cdot B'$; $(A \cdot B)' = A' + B'$

Written differently: $A + B = (A' \cdot B')'$; $(A \cdot B) = (A' + B')'$

In other words,

OR is the same as NAND with complemented inputs


AND is the same as NOR with complemented inputs

NAND is the same as OR with complemented inputs

NOR is the same as AND with complemented inputs


ORNAND Equivalence

A	\bar{A}	B	\bar{B}	$A + B$	$\overline{\bar{A} \cdot \bar{B}}$	$\bar{A} + \bar{B}$	$\overline{A \cdot B}$
0	1	0	1	0	0	1	1
0	1	1	0	1	1	1	1
1	0	0	1	1	1	1	1
1	0	1	0	1	1	0	0

 

AND/NOR Equivalence

A	\bar{A}	B	\bar{B}	$A \cdot B$	$\overline{A + B}$	$\bar{A} \cdot \bar{B}$	$\overline{A + B}$
0	1	0	1	0	0	1	1
0	1	1	0	0	0	0	0
1	0	0	1	0	0	0	0
1	0	1	0	1	1	0	0

 


It is possible to convert from networks with ANDs and ORs to networks with NANDs and NORs by introducing the appropriate inversions ("bubbles")

To preserve logic levels, each introduced "bubble" must be matched with a corresponding "bubble"



Multi-Level Logic: Conversion of Forms

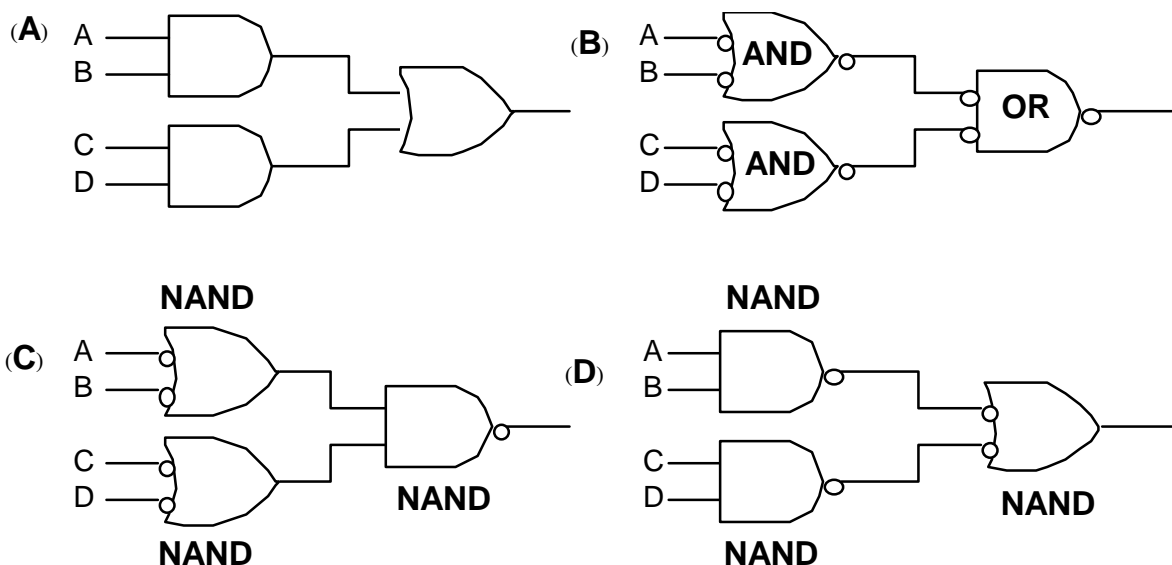Example: Map AND/OR network to NAND/NAND network



Multi-Level Logic: Conversion of Forms

  Example: Map AND/OR network to NAND/NAND network





**Verify equivalence
of the two forms**

$$\begin{aligned} Z &= [(A \cdot B)' (C \cdot D)']' \\ &= [(A' + B') (C' + D')] \\ &= [(A' + B')' \cdot (C' + D')'] \\ &= (A \cdot B) + (C \cdot D) \end{aligned}$$

This is the easy conversion:

Multi-Level Logic: Mapping Between Forms

  Example: Map AND/OR network to NOR/NOR network



**Conserve
"Bubbles"**



**Verify equivalence
of the two forms**

$$Z =$$

**Conserve
"Bubbles"**

Multi-Level Logic: Mapping Between Forms

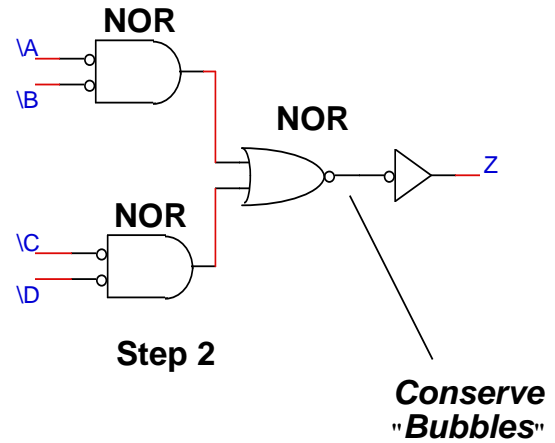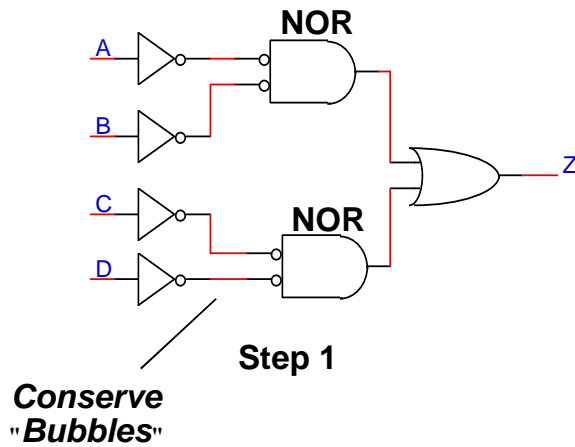Example: Map AND/OR network to NOR/NOR network



Verify equivalence
of the two forms



$$\begin{aligned}
 Z &= \{[(A' + B')' + (C' + D')']'\}' \\
 &= \{(A' + B') \cdot (C' + D')'\}' \\
 &= (A' + B')' + (C' + D')' \\
 &= (A \cdot B) + (C \cdot D)
 \end{aligned}$$

This is the hard conversion:

AND/OR to NAND/NAND more natural

Multi-Level Logic: Mapping Between Forms

  Example: Map OR/AND network to NOR/NOR network





Verify equivalence
of the two forms

$$Z =$$

Multi-Level Logic: Mapping Between Forms

  Example: Map OR/AND network to NOR/NOR network





Verify equivalence
of the two forms

$$\begin{aligned} Z &= [(A + B)' + (C + D)']' \\ &= \{(A + B)'\}' \cdot \{(C + D)'\}' \\ &= (A + B) \cdot (C + D) \end{aligned}$$

This is the easy conversion:

Multi-Level Logic: Mapping Between Forms

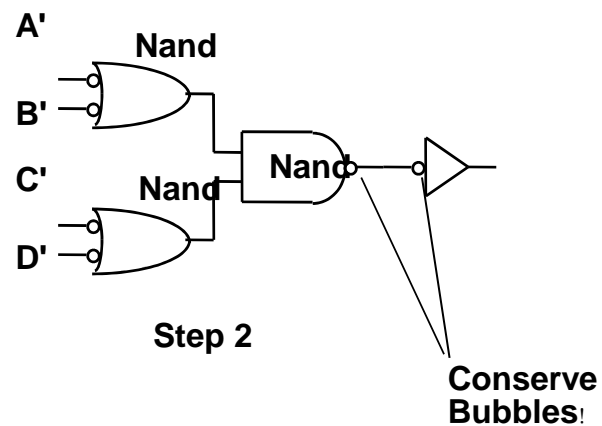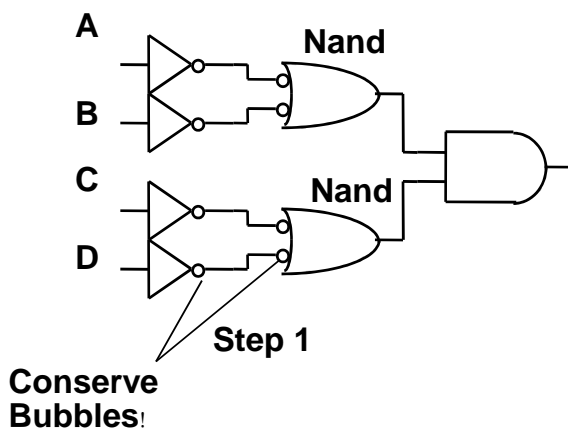Example: Map OR/AND network to NAND/NAND network





Verify equivalence
of the two forms

$$Z =$$

Multi-Level Logic: Mapping Between Forms

Contemporary Logic Design
Multi-Level Logic

 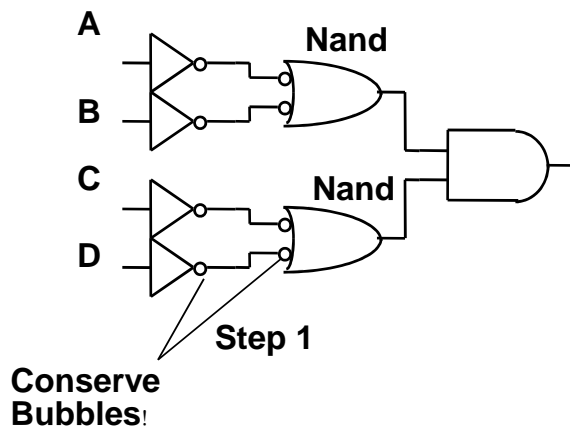Example: Map OR/AND network to NAND/NAND network



*Verify equivalence
of the two forms*

$$\begin{aligned}
 Z &= \{[(A' \cdot B')' \cdot (C' \cdot D')']'\} \\
 &= \{(A' \cdot B') + (C' \cdot D')\}' \\
 &= (A' \cdot B')' \cdot (C' \cdot D')' \\
 &= (A + B) \cdot (C + D)
 \end{aligned}$$

This is the hard conversion:

OR/AND to NOR/NOR more natural

© R.H. Katz Transparency No. 3-13

Multi-Level Logic: More than Two Levels


Contemporary Logic Design
Multi-Level Logic

$$F = A(B + CD) + B'C'$$

**Original
AND-OR Network**

**Introduction and
Conservation of Bubbles**

 
**Redrawn in terms
of conventional
NAND Gates**



© R.H. Katz Transparency No. 3-14

Multi-Level Logic: More than Two Levels

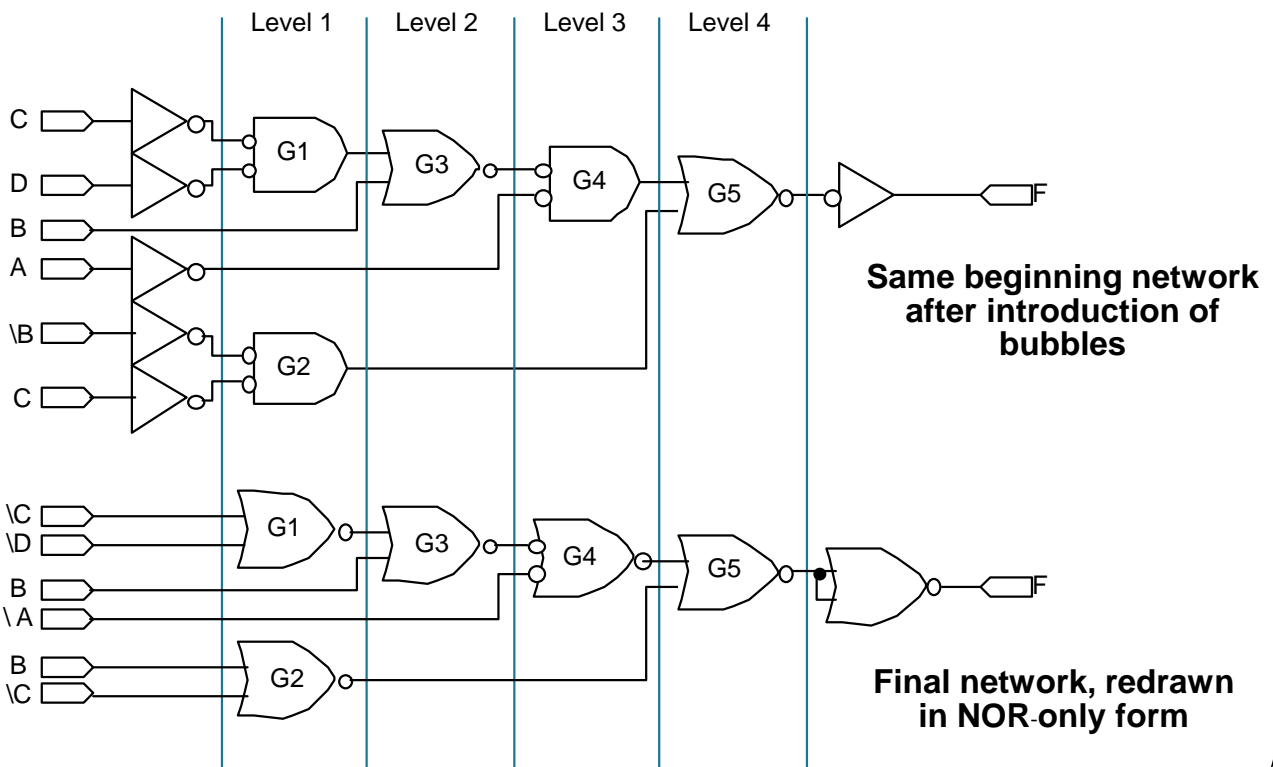Contemporary Logic Design
Multi-Level Logic




© R.H. Katz Transparency No. 3-15

Multi-Level Logic: More than Two Levels

Contemporary Logic Design
Multi-Level Logic

Conversion Example

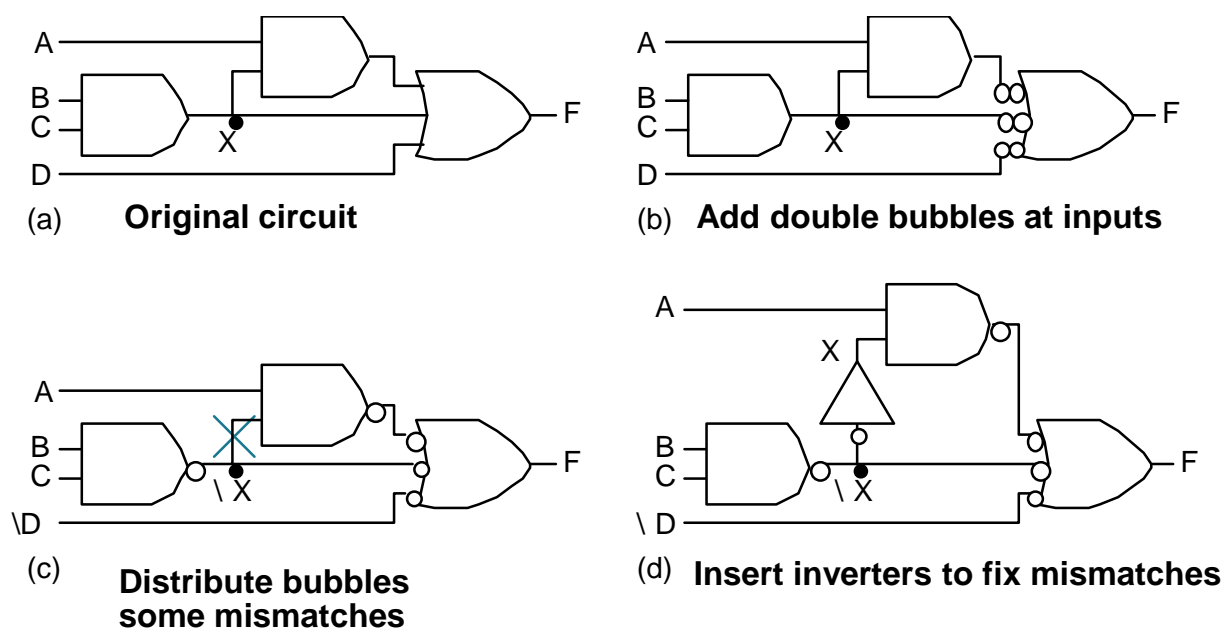


© R.H. Katz Transparency No. 3-16

Multi-Level Logic: AND-OR-Invert Block

Contemporary Logic Design
Multi-Level Logic


AOI Function: Three stage logic— AND, OR, Invert
Multiple gates "packaged" as a single circuit block

logical concept

 


AND OR Invert
two-input two-stack


possible switch implementation

 

2x2 AOI Schematic
Symbol

 

3x2 AOI Schematic
Symbol

 

© R.H. Katz Transparency No. 3-17

Multi-Level Logic: AND-OR-Invert

Contemporary Logic Design
Multi-Level Logic

Example: XOR implementation

$$A \text{ xor } B = A' B + A B'$$

AOI form

$$\begin{aligned} &= (?)' \\ &\quad (A' B + A B')' \\ &\quad (A + B')(A' + B) \\ &\quad (A B + A' B') \end{aligned}$$

General procedure to place in AOI form:

Compute the complement in Sum of Products form by
circling the 0's in the K-map!

$$F = (A' B' + A B)'$$

		A		0	1
B	0	0	1		
	1	1	0		

© R.H. Katz Transparency No. 3-18

Multi-Level Logic: AND-OR-Invert

Example:

C \ AB	A			
	00	01	11	10
0	1	0	0	0
1	1	1	0	1

F' K-map

$$F = B C' + A C' + A B$$

$$F' = A' B' + A' C + B' C$$

Implemented by 2-input 3-stack AOI gate

$$F = (A + B)(A + C')(B + C')$$

$$F' = (B' + C)(A' + C)(A' + B')$$

Implemented by 2-input 3-stack OAI gate

Example:


4-bit Equality Function

$$Z = (A_0 B_0 + A_0' B_0')(A_1 B_1 + A_1' B_1')(A_2 B_2 + A_2' B_2')(A_3 B_3 + A_3' B_3')$$

Each implemented in single 2x2 AOI gate

Multi-Level Logic: AND-OR-Invert

 Example: AOI Implementation of a 4-Bit Equality Tester




High if $A_0 \neq B_0$, Low if $A_0 = B_0$
 $A = B$ active low

> Conservation of bubbles

If all inputs are low
(asserted in negative logic)
then $A_i = B_i, i=0, \dots, 3$
Output Z asserted

Multi-Level Logic: AND-OR-Invert

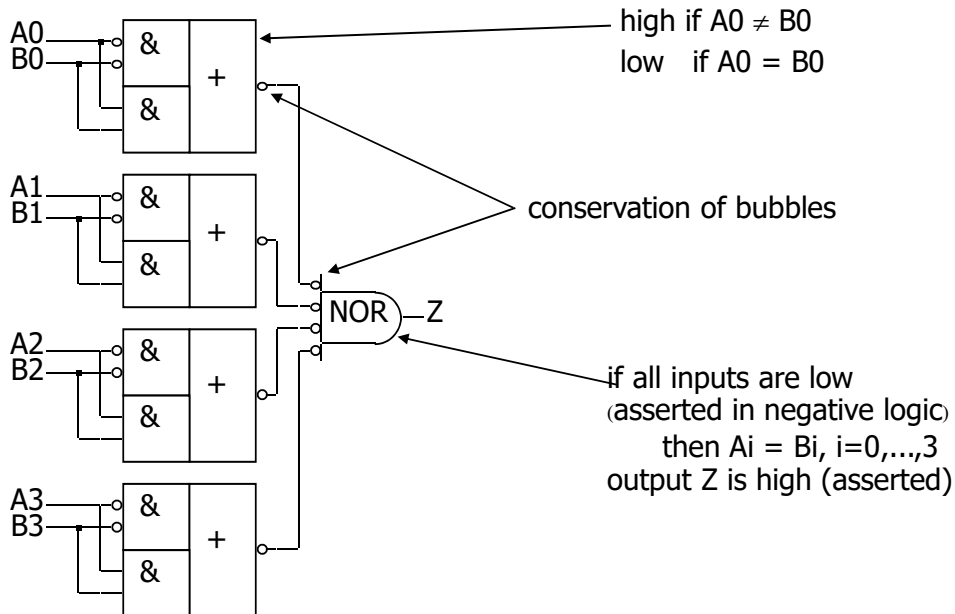Example: AOI Implementation of a 4-Bit Equality Tester




Multi-Level Logic: CAD Tools for Simplification

Multi-Level Optimization:

1. Factor out common sublogic (reduce fan-in, increase gate levels), subject to timing constraints
2. Map factored form onto library of gates
3. Minimize number of literals (correlates with number of wires)

Factored Form:

sum of products of sum of products ...

 

$$X = (A B + B' C) (C + D (E + A C')) + (D + E)(F G)$$

Multi-Level Logic: CAD Tools for Simplification

Operations on Factored Forms:

- Decomposition
- Extraction
- Factoring
- Substitution
- Collapsing

Manipulate network by interactively issuing the appropriate instructions

There exists no algorithm that guarantees "optimal" multi-level network will be obtained

Multi-Level Logic: CAD Tools for Simplification

Decomposition:

Take a single Boolean expression and replace with collection of new expressions:

$$F = A B C + A B D + A' C' D' + B' C' D' \quad (12 \text{ literals})$$


F rewritten as:

$$F = X Y + X' Y'$$


$$X = A B$$

$$Y = C + D$$

(4 literals)

 

Before Decomposition

 

After Decomposition


Extraction: common intermediate subfunctions are factored out

$$\begin{aligned} F &= (A + B) C D + E & (11 \text{ literals}) \\ G &= (A + B) E' \\ H &= C D E \end{aligned}$$


can be re-written as:

$$\begin{aligned} F &= X Y + E & (7 \text{ literals}) \\ G &= X E' \\ H &= Y E \\ X &= A + B \\ Y &= C D \end{aligned}$$

"Kernels": primary divisors

 

Before Extraction

 


After Extraction

Factoring: expression in two level form re-expressed in multi-level form


$$F = A C + A D + B C + B D + E \quad (9 \text{ literals})$$

can be rewritten as:
 
$$F = (A + B) (C + D) + E \quad (5 \text{ literals})$$



Before Factoring

 

After Factoring

Multi-Level Logic: CAD Tools for Simplification

Substitution: function G into function F, express F in terms of G

$$\begin{aligned} F &= A + B C & (5 \text{ literals}) \\ G &= A + B \end{aligned}$$

F rewritten in terms of G:

$$F = G (A + C) \quad (2 \text{ literals})$$

Collapsing: reverse of substitution; use to eliminate levels to meet timing constraints

$$\begin{aligned} F &= G (A + C) \\ &= (A + B) (A + C) \\ &= A A + A C + A B + B C \\ &= A + B C \quad \text{QED} \end{aligned}$$

Multi-Level Logic: CAD Tools for Simplification

Key to implementing these operations: "division" over Boolean functions

$$\begin{array}{ccccc} & & F = P Q + R & & \\ & \swarrow & | & \searrow & \\ \text{divisor} & & \text{quotient} & & \text{remainder} \end{array}$$

example:

$$\begin{aligned} X &= A C + A D + B C + B D + E \\ Y &= A + B \end{aligned}$$

X "divided" by Y is—

$$X = Y (C + D) + E$$

Complexity: finding suitable divisors

$$\begin{aligned} F &= A D + B C D + E \\ G &= A + B \end{aligned}$$

G does not divide F under algebraic division rules

G does divide F under Boolean rules (very large number of these!)

$$F/G = (A + C) D$$

F written as G Q + R

$$\begin{aligned} F &= [G (A + C) D] + E \\ &= (A + B) (A + C) D + E \\ &= (A A + A C + A B + B C) D + E \\ &= (A + B C) D + E \\ &= A D + B C D + E \quad \text{QED} \end{aligned}$$

Multi-Level Logic: CAD Tools for Simplification

misll Session with the Full Adder

```
% misll
UC Berkeley, MIS Release #2.1 (compiled 3-Mar-89 at 5:32 PM)
misll> re fulladder
misll> p
{co} = a b ci + a b ci' + a b' ci + a' b ci
{sum} = a b ci + a b' ci' + a' b ci' + a' b' ci
misll> pf
{co} = a b' ci + b (ci (a' + a) + a ci')
{sum} = ci (a' b' + a b) + ci' (a b' + a' b)
misll> sim1 *
misll> p
{co} = a b + a ci + b ci
{sum} = a b ci + a b' ci' + a' b ci' + a' b' ci
misll> pf
{co} = ci (b + a) + a b
{sum} = ci (a' b' + a b) + ci' (a b' + a' b)
misll> gd *
misll> pf
{co} = a [2] + b ci
{sum} = a' [3] + a [3]
[2] = ci + b
[3] = b' ci' + b ci
```

read eqntott equations

two level minimization

good decomposition

technology independent up to this point

Multi-Level Logic: CAD Tools for Simplification

```
misll> rlib msu.genlib
misll> map
misll> pf
[361] = b' ci' + a'
[328] = b'
[329] = ci'
{co} = [328]' [329]' + [361]'
[3] = b ci' + b' ci
{sum} = [3] a' + [3]' a
misll> pg
[361] 1890:physical 32.00
[328] 1310:physical 16.00
[329] 1310:physical 16.00
{co} 1890:physical 32.00
[3] 2310:physical 40.00
{sum} 2310:physical 40.00
misll> pat
... using library delay model
{sum} : arrival=(2.2 2.2)
{co} : arrival=(2.2 2.2)
[328] : arrival=(1.2 1.2)
[361] : arrival=(1.2 1.2)
[329] : arrival=(1.2 1.2)
[3] : arrival=(1.2 1.2)
ci : arrival=(0.0 0.0)
b : arrival=(0.0 0.0)
a : arrival=(0.0 0.0)
misll> quit
%
```


read library & perform technology mapping

gates that implement the various nodes and their relative areas

timing simulation
unit delay plus 0.2 time units per fan-out

misII and the MSU gate library

VLSI Standard Cells

 

**NOTE: OR-AND-INVERT
equivalent to INVERT-AND-OR**

Number	Name	Function
1310	inv	A'
1120	nor2	$(A+B)'$
1130	nor3	$(A+B+C)'$
1140	nor4	$(A+B+C+D)'$
1220	nand2	$(A \cdot B)'$
1230	nand3	$(A \cdot B \cdot C)'$
1240	nand4	$(A \cdot B \cdot C \cdot D)'$
1660	and2.nand2	$A \cdot B, (A \cdot B)'$
1670	and3.nand3	$A \cdot B \cdot C, (A \cdot B \cdot C)'$
1680	and4.nand4	$A \cdot B \cdot C \cdot D, (A \cdot B \cdot C \cdot D)'$
1760	or2.nor2	$A+B, (A+B)'$
1770	or3.nor3	$A+B+C, (A+B+C)'$
1780	or4	$(A+B+C+D)$
1870	aoi22	$(A \cdot B + C \cdot D)'$
1880	aoi21	$(A + B \cdot C)'$
1860	oai22	$[(A+B)(C+D)]'$
1890	oai21	$[A(B+C)]'$
1970	ao22	$A \cdot B + D \cdot E$
1810	ao222	$A \cdot B + C \cdot D + E \cdot F$
1910	ao2222	$A \cdot B + C \cdot D + E \cdot F + G \cdot H$
1930	ao33	$A \cdot B \cdot C + D \cdot E \cdot F$
2310	xor2	$A \cdot B' + A' \cdot B$
2350	xnor2	$A \cdot B + A' \cdot B'$

© R.H. Katz Transparency No. 3-31

More Examples

mis with standard simplification script:

```
misII -f script -t pla <espresso truth table file>
```

Full Adder:

```
model fulladder
inputs a b ci
outputs sum co
names a b ci co sum
1--01
-1-01
--101
111-1
names a b ci co
11-1
1-11
-111
end
```

mis pla style outputs


input variables

output variable

$$\text{SUM} = A \text{ CO}' + B \text{ CO}' + \text{CI CO}' + A B \text{ CI} \quad (9 \text{ literals})$$

$$\text{CO} = A B + A \text{ CI} + B \text{ CI} \quad (6 \text{ literals})$$

 Note that $A \text{ xor } B \text{ xor } \text{CI} = A' B' \text{ CI} + A B' \text{ CI}' + A' B \text{ CI}' + A B \text{ CI}$ (12 literals!)



Multilevel Implementation of Full Adder: 5 Logic Levels!

Two-bit Adder

```
.inputs a b c d
.outputs x y z
names a c z [22]x
---11
11--1
-10-1
names a b c d x z [22]y
1---0--1
--1---11
-11-0--1
--110--1
---100-1
names a b c d z
-0-11
-1-01
0-101
names a d z [22]
1101
end
```


Mis Output

$$Z = B' D + B D' + A' C D'$$

$$[22] = A D Z'$$

$$X = [22] + A C + C Z'$$
 
$$Y = A X + C [22] + B C X' + C D X' + D X' Z'$$



8 logic levels!

BCD Increment By 1

```

model bcdincrement
inputs a b c d
outputs w x y z
names a b c d z w
1---11
0111-1
names a b c w z x
01-0-1
0-1001
names a c z y
-111
0001
names a b c d z
0--01
-0001
end

```


Mis Output

$$Z = A' D' + B' C' D'$$

$$Y = C Z + A' C' Z'$$

$$W = A Z + A' B C D$$

$$X = A' B W' + A' C W' Z'$$

 

Time Response in Combinational Networks

- emphasis on timing behavior of circuits
- waveforms to visualize what is happening
- simulation to create these waveforms
- momentary change of signals at the outputs: *hazards*
can be useful— pulse shaping circuits
can be a problem — *glitches*: incorrect circuit operation

Terms:



gate delay— time for change at input to cause change at output
minimum delay vs. typical/nominal delay vs. maximum delay
careful designers design for the worst case!

rise time— time for output to transition from low to high voltage

fall time— time for output to transition from high to low voltage


Time Response in Combinational Networks

Pulse Shaping Circuit

  


Time Response in Combinational Networks

Another Pulse Shaping Circuit

 

Close Switch

Open Switch

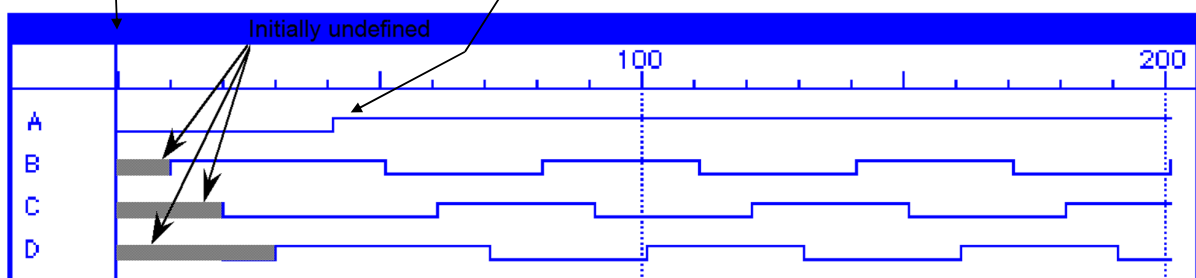

Time Response in Combinational Networks

Hazards/Glitches and How to Avoid Them

Unwanting switching at the outputs

Occur because delay paths through the circuit experience different propagation delays

Danger if logic "makes a decision" while output is unstable
OR hazard output controls an *asynchronous* input (these respond immediately to changes rather than waiting for a synchronizing signal called a *clock*)

Usual solutions:

wait until signals are stable (by using a clock)


never, never, never use circuits with asynchronous inputs

design hazard-free circuits


Suggest that first two approaches be used, but we'll tell you about hazard-free design anyway!

Time Response in Combinational Networks


Hazards/Glitches and How to Avoid Them

 

 Input change causes output to go from 1 to 0 to 1



 Input change causes output to go from 0 to 1 to 0






Input change causes a double change
from 0 to 1 to 0 to 1 OR
from 1 to 0 to 1 to 0

Kinds of Hazards

Time Response in Combinational Circuits

Glitch Example

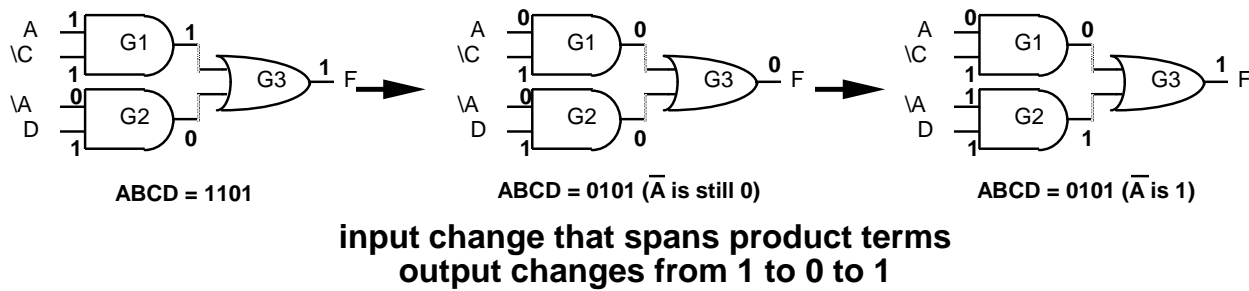  

Time Response in Combinational Networks

Glitch Example

General Strategy: add redundant terms

$$F = A'D + AC' \text{ becomes } A'D + AC' + C'D$$

This eliminates 1-hazard? How about 0-hazard?


Re-express F in PoS form:

$$F = (A' + C')(A + D)$$

Glitch present!

Add term: $(C' + D)$

 This expression is equivalent
to the hazard-free SoP form of F



Time Response in Combinational Networks

Glitch Example

Start with expression that is free of static 1-hazards

$$F = A C' + A' D + C' D$$

Work with complement:

$$F' = (A C' + A' D + C' D)'$$

$$= (A' + D)(A + D')(C + D')$$

$$= A C + A C D' + C D' + A' C D' + A' D'$$

$$= A C + C D' + A' D'$$

covers all the adjacent 0's in the K-map

free of static-1 and static-0 hazards!

Time Response in Combinational Networks

Detecting Static Hazards in Multi-Level Circuits

Calculate transient output function

variables and complements are treated as independent variables

cannot use $X + X' = 1$ or $X \cdot X' = 0$ for simplifications

Example:

$$F = A B C + (A + D)(A' + C')$$

$$F1 = A B C + A A' + A C' + A' D + C' D$$

2-level form

AB		A			
		00	01	11	10
CD	00	0	0	1	1
	01	1	1	1	1
	11	1	1	1	0
	10	0	0	1	0
		B			

ABCD: 1111 to 1110, covered by term ABC, so no 1-hazard present

ABCD: 1110 to 1100, term ABC goes low while term AC' goes high


some static hazards are present!

Static 1-hazards

Solution:

Add redundant terms to insure all adjacent transitions are covered by terms

$$F_2 = A C' + A' D + C' D + A B + B D$$

 

Static 0-Hazards

Similar to previous case, but work with the complement of F

If terms of the transient output function cover all 0 transitions, then no 0-hazards are present

$$\begin{aligned}\bar{F} &= [A B C + (A + D)(A' + C')]'] \\ &= (A' + B' + C')(A' D' + A C) \\ &= A' D' + A' B D' + A' C D' + A B' C \\ &= A' D' + A B' C \\ &\quad + B' C D'\end{aligned}$$

$$F = (A + D)(A' + B + C')(B + C' + D)$$


0-hazard free

equivalent to F2 on last slide

AB \ CD		A			
		00	01	11	10
C	00	0	0	1	1
	01	1	1	1	1
	11	1	1	1	0
	10	0	0	1	0
		B		D	

0-hazard on transition from 1010 to 0010

Static 0-Hazards

 

Designing Networks for Hazard-free operation

Simply place transient output function in a form that guarantees that all adjacent ones are covered by a term

no term of the transient output function contains both a variable and its complement

AB		A			
CD		00	01	11	10
		0	0	1	1
C	01	1	1	1	1
	11	1	1	1	0
D	10	0	0	1	0

$$F(A,B,C,D) = m(1,3,5,7,8,9,12,13,14,15)$$


$$F = AB + A'D + BD + AC' + C'D$$

$$= (A' + B + C')D + A(B + C')$$

(factored by distributive law, which does not introduce hazards since it does not depend on the complementarity laws for its validity)

Dynamic Hazards

Example with Dynamic Hazard

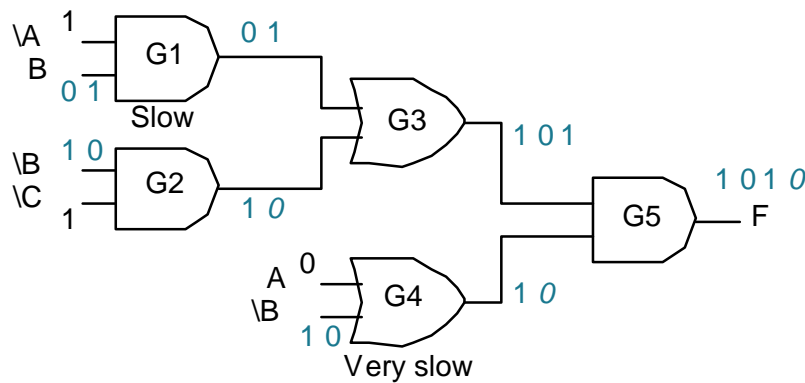

Three different paths from B or B' to output

ABC = 000, F = 1 to ABC = 010, F = 0

different delays along the paths:

G1 slow, G4 very slow

Handling dynamic hazards very complex

Beyond our scope

Chapter Review

- Transition from Simple Gates to more complex gate building blocks
- Conversion from AND/OR, OR/AND to NAND/NAND, NOR/NOR
- Multi-Level Logic: Reduced gate count, fan-ins, but increased delay
- Use of misII to optimize multi-level logic and to perform mappings
- Time Response in Combinational Logic:
 - Gate Delay, Rise Time, Fall Time
 - Hazards and Hazard-free Design