

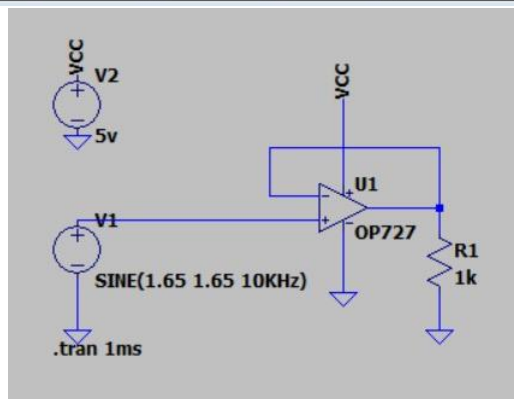
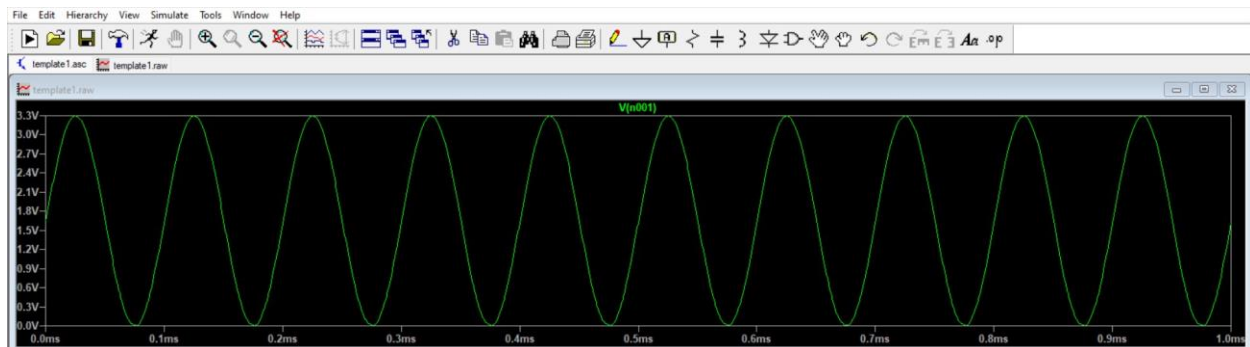


1. Voltage Follower


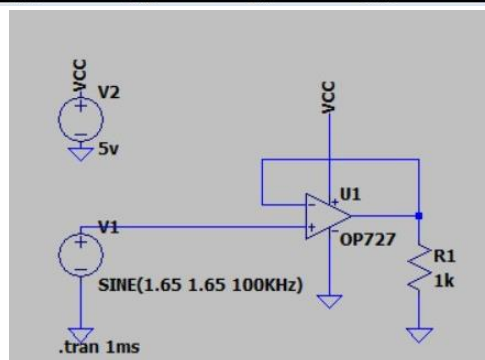


Freq = 10KHZ


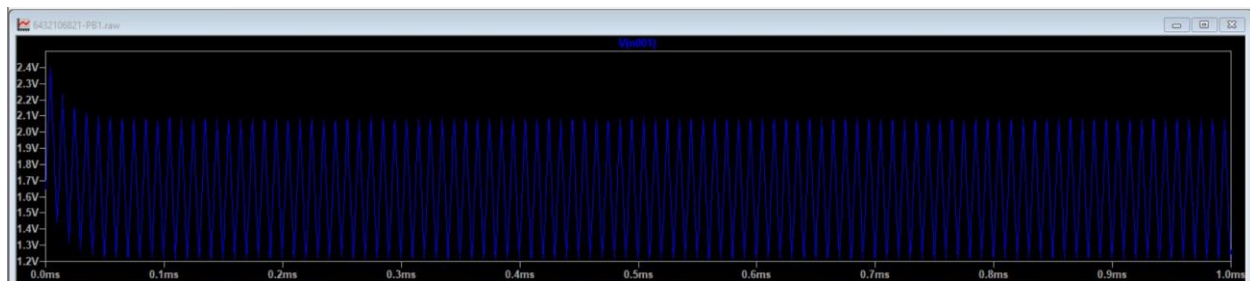


Freq = 100KHz

2. Inverting Amplifier

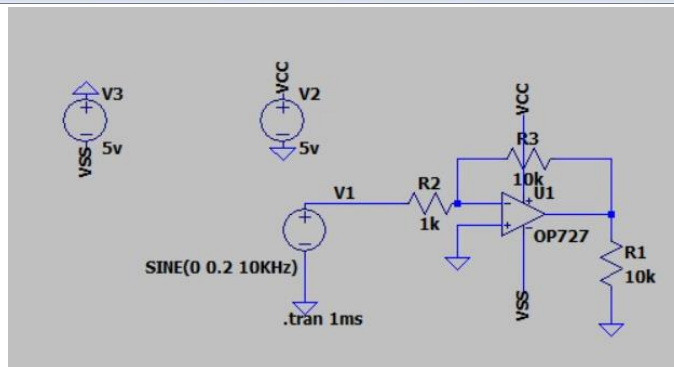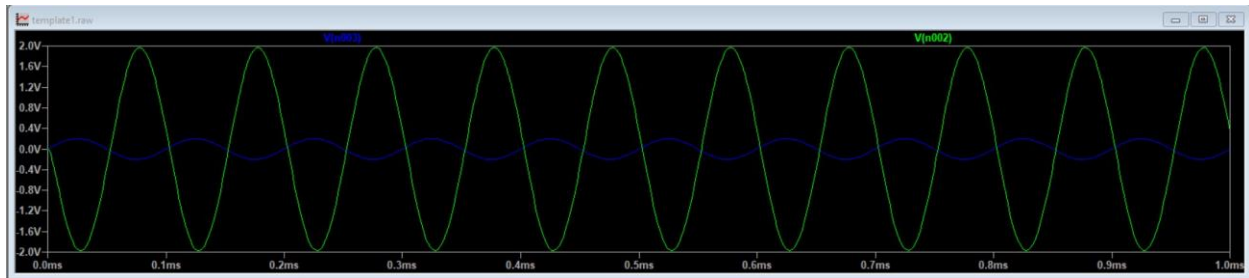

3. Non-inverting Amplifier

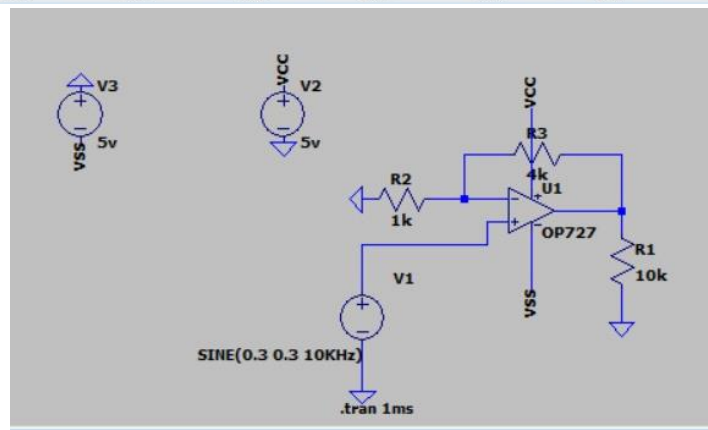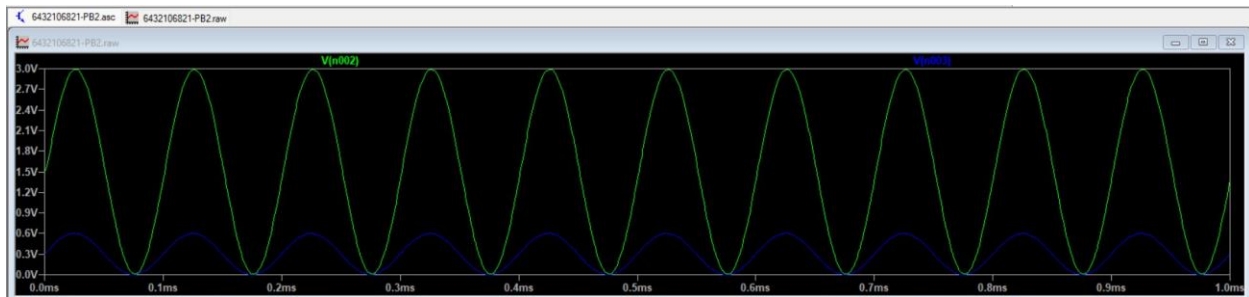

4. Current Source

