

Chapter #9: Finite State Machine Optimization

Contemporary Logic Design

**Randy H. Katz
University of California, Berkeley**

July 1993

Chapter Outline

- *Procedures for optimizing implementation of an FSM*

State Reduction

State Assignment

- *Computer Tools for State Assignment: Nova, Mustang, Jedi*
- *Choice of Flipflops*
- *FSM Partitioning*

Motivation

Basic FSM Design Procedure:

- (1) Understand the problem
- (2) Obtain a formal description
- (3) Minimize number of states
- (4) Encode the states
- (5) Choose FFs to implement state register
- (6) Implement the FSM





**This
Chapter!**

Next Chapter

Motivation

State Reduction

  

Odd Parity Checker: two alternative state diagrams

- Identical output behavior on all input strings
- FSMs are *equivalent*, but require different implementations
- Design state diagram without concern for # of states, Reduce later

Motivation

State Reduction (continued)

Implement FSM with fewest possible states

- **Least number of flipflops**
- **Boundaries are power of two number of states**
- **Fewest states usually leads to more opportunities for don't cares**
- **Reduce the number of gates needed for implementation**

State Reduction

Goal

Identify and combine states that have equivalent behavior

Equivalent States: for all input combinations, states transition to the same or equivalent states

Odd Parity Checker: S0, S2 are equivalent states

Both output a 0

Both transition to S1 on a 1 and self-loop on a 0

Algorithmic Approach

- **Start with state transition table**
- **Identify states with same output behavior**
- **If such states transition to the same next state, they are equivalent**
- **Combine into a single new renamed state**
- **Repeat until no new states are combined**

State Reduction

Row Matching Method

Example FSM Specification:

Single input X, output Z

Taking inputs grouped four at a time, output 1 if last four inputs were the string 1010 or 0110

Example I/O Behavior:

X = 0010 0110 1100 1010 0011 ...
Z = 0000 0001 0000 0001 0000 ...

Upper bound on FSM complexity:


Fifteen states ($1 + 2 + 4 + 8$)

Thirty transitions ($2 + 4 + 8 + 16$)

sufficient to recognize any binary string of length four!

Row Matching Method

State Diagram for Example FSM:

 

Row Matching Method**Initial State Transition Table:**

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1	S_2	0	0
0	S_1	S_3	S_4	0	0
1	S_2	S_5	S_6	0	0
00	S_3	S_7	S_8	0	0
01	S_4	S_9	S_{10}	0	0
10	S_5	S_{11}	S_{12}	0	0
11	S_6	S_{13}	S_{14}	0	0
000	S_7	S_0	S_0	0	0
001	S_8	S_0	S_0	0	0
010	S_9	S_0	S_0	0	0
011	S_{10}	S_0	S_0	1	0
100	S_{11}	S_0	S_0	0	0
101	S_{12}	S_0	S_0	1	0
110	S_{13}	S_0	S_0	0	0
111	S_{14}	S_0	S_0	0	0

Row Matching Method

Initial State Transition Table:

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Res et	S ₀	S ₁	S ₂	0	0
0	S ₁	S ₃	S ₄	0	0
1	S ₂	S ₅	S ₆	0	0
00	S ₃	S ₇	S ₈	0	0
01	S ₄	S ₉	S ₁₀	0	0
10	S ₅	S ₁₁	S ₁₂	0	0
11	S ₆	S ₁₃	S ₁₄	0	0
000	S ₇	S ₀	S ₀	0	0
001	S ₈	S ₀	S ₀	0	0
010	S ₉	S ₀	S ₀	0	0
011	S ₁₀	S ₀	S ₀	1	0
100	S ₁₁	S ₀	S ₀	0	0
101	S ₁₂	S ₀	S ₀	1	0
110	S ₁₃	S ₀	S ₀	0	0
111	S ₁₄	S ₀	S ₀	0	0

Row Matching Method

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Res et	S ₀	S ₁	S ₂	0	0
0	S ₁	S ₃	S ₄	0	0
1	S ₂	S ₅	S ₆	0	0
00	S ₃	S ₇	S ₈	0	0
01	S ₄	S ₉	S' ₁₀	0	0
10	S ₅	S ₁₁	S' ₁₀	0	0
11	S ₆	S ₁₃	S ₁₄	0	0
000	S ₇	S ₀	S ₀	0	0
001	S ₈	S ₀	S ₀	0	0
010	S ₉	S ₀	S ₀	0	0
011 or 101	S' ₁₀	S ₀	S ₀	1	0
100	S ₁₁	S ₀	S ₀	0	0
110	S ₁₃	S ₀	S ₀	0	0
111	S ₁₄	S ₀	S ₀	0	0

Row Matching Method

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Res et	S ₀	S ₁	S ₂	0	0
0	S ₁	S ₃	S ₄	0	0
1	S ₂	S ₅	S ₆	0	0
00	S ₃	S ₇	S ₈	0	0
01	S ₄	S ₉	S' ₁₀	0	0
10	S ₅	S ₁₁	S' ₁₀	0	0
11	S ₆	S ₁₃	S ₁₄	0	0
000	S ₇	S ₀	S ₀	0	0
001	S ₈	S ₀	S ₀	0	0
010	S ₉	S ₀	S ₀	0	0
011 or 101	S' ₁₀	S ₀	S ₀	1	0
100	S ₁₁	S ₀	S ₀	0	0
110	S ₁₃	S ₀	S ₀	0	0
111	S ₁₄	S ₀	S ₀	0	0

Row Matching Method

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1	S_2	0	0
0	S_1	S_3	S_4	0	0
1	S_2	S_5	S_6	0	0
00	S_3	S_7'	S_7'	0	0
01	S_4	S_7'	S_{10}'	0	0
10	S_5	S_7'	S_{10}'	0	0
11	S_6	S_7'	S_7'	0	0
not (011 or 101)	S_7'	S_0	S_0	0	0
011 or 101	S_{10}'	S_0	S_0	1	0

Row Matching Method

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1	S_2	0	0
0	S_1	S_3	S_4	0	0
1	S_2	S_5	S_6	0	0
00	S_3	S'_7	S'_7	0	0
01	S_4	S'_7	S'_{10}	0	0
10	S_5	S'_7	S'_{10}	0	0
11	S_6	S'_7	S'_7	0	0
not (011 or 101)	S'_7	S_0	S_0	0	0
011 or 101	S'_{10}	S_0	S_0	1	0


State Reduction

Row Matching Method

**Final Reduced
State Transition Table**

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3'	S4'	0	0
1	S2	S4'	S3'	0	0
00 or 11	S3'	S7'	S7'	0	0
01 or 10	S4'	S7'	S10'	0	0
not (011 or 101)	S7'	S0	S0	0	0
011 or 101	S10'	S0	S0	1	0

**Corresponding State
Diagram**

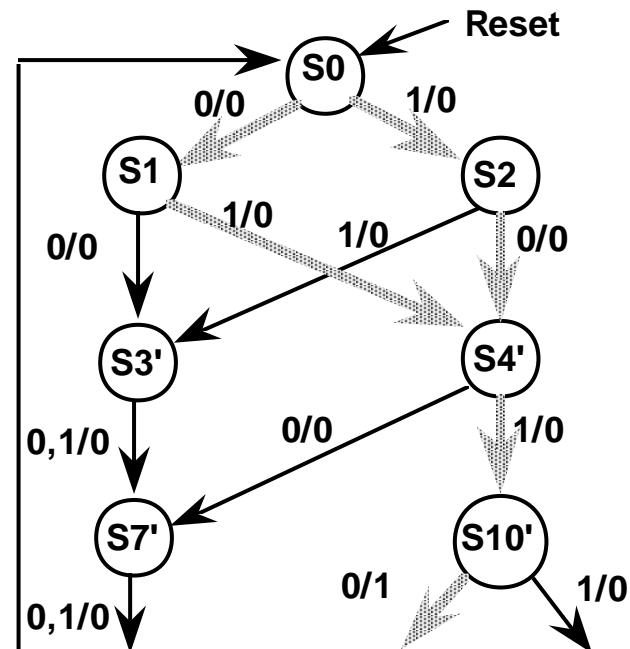

State Reduction

Row Matching Method

- Straightforward to understand and easy to implement
- Problem: does not allow yield the most reduced state table!

Example: 3 State Odd Parity Checker

Present State	Next State		Output
	X=0	X=1	
S ₀	S ₀	S ₁	0
S ₁	S ₁	S ₂	1
S ₂	S ₂	S ₁	0

**No way to combine states S₀ and S₂
based on Next State Criterion!**

State Reduction

Implication Chart Method

New example FSM:

Single input X, Single output Z

Output a 1 whenever the serial sequence 010 or 110 has been observed at the inputs

State transition table:

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S ₀	S ₁	S ₂	0	0
0	S ₁	S ₃	S ₄	0	0
1	S ₂	S ₅	S ₆	0	0
00	S ₃	S ₀	S ₀	0	0
01	S ₄	S ₀	S ₀	1	0
10	S ₅	S ₀	S ₀	0	0
11	S ₆	S ₀	S ₀	1	0

State Reduction

Implication Chart Method

Enumerate all possible combinations of states taken two at a time

Next States
Under all
Input
Combinations

S0						
S1						
S2						
S3						
S4						
S5						
S6						
	S0	S1	S2	S3	S4	S5

Naive Data Structure:
 X_{ij} will be the same as X_{ji}
Also, can eliminate the diagonal

S1					
S2					
S3					
S4					
S5					
S6					
	S0	S1	S2	S3	S4

Implication Chart

State Reduction

Implication Chart

Filling in the Implication Chart

Entry X_{ij} — Row is S_i , Column is S_j

S_i is equivalent to S_j if outputs are the same and next states are equivalent


X_{ij} contains the next states of S_i , S_j which must be equivalent if S_i and S_j are equivalent

If S_i , S_j have different output behavior, then X_{ij} is crossed out

 
Example:

S_0 transitions to S_1 on 0, S_2 on 1;
 S_1 transitions to S_3 on 0, S_4 on 1;

So square $X_{\langle 0,1 \rangle}$ contains entries S_1 - S_3 (transition on zero)
 S_2 - S_4 (transition on one)



Implication Chart Method

 

Starting Implication Chart

S2 and S4
have different
I/O behavior

This implies that
S1 and S0 cannot
be combined

Implication Chart Method


Results of First Marking Pass

Second Pass Adds No New Information

S3 and S5 are equivalent

S4 and S6 are equivalent


This implies that S1 and S2 are too!

 

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1'	S_1'	0	0
0 or 1	S_1'	S_3'	S_4'	0	0
00 or 10	S_3'	S_0	S_0	0	0
01 or 11	S_4'	S_0	S_0	1	0

Reduced State
Transition Table

Multiple Input State Diagram Example

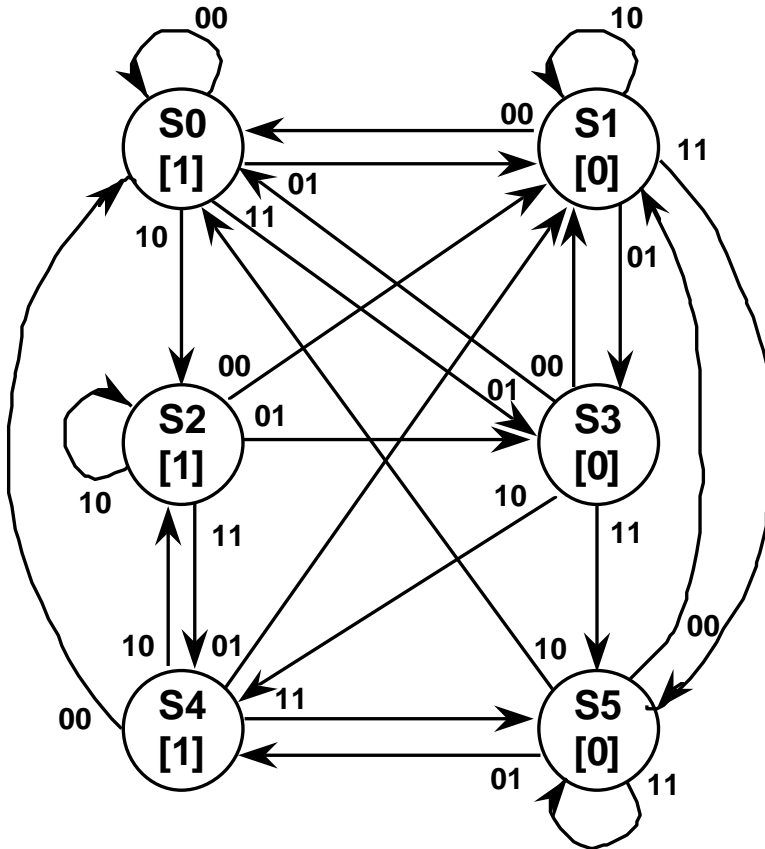


State Diagram

Present State	Next State				Output
	00	01	10	11	
S ₀	S ₀	S ₁	S ₂	S ₃	1
S ₁	S ₀	S ₃	S ₁	S ₅	0
S ₂	S ₁	S ₃	S ₂	S ₄	1
S ₃	S ₁	S ₀	S ₄	S ₅	0
S ₄	S ₀	S ₁	S ₂	S ₅	1
S ₅	S ₁	S ₄	S ₀	S ₅	0

Symbolic State Diagram

State Reduction

Multiple Input Example

 

Implication Chart

Present State	Next State				Output
	00	01	10	11	
S_0'	S_0'	S_1	S_2	S_3'	1
S_1	S_0'	S_3'	S_1	S_3'	0
S_2	S_1	S_3'	S_2	S_0'	1
S_3'	S_1	S_0'	S_0'	S_3'	0


Minimized State Table

State Reduction

Implication Chart Method

Does the method solve the problem with the odd parity checker?

Implication Chart

 

**S_0 is equivalent to S_2
since nothing contradicts this assertion!**

State Reduction

Implication Chart Method

The detailed algorithm:

1. **Construct implication chart, one square for each combination of states taken two at a time**
2. **Square labeled S_i, S_j , if outputs differ than square gets "X". Otherwise write down implied state pairs for all input combinations**
3. **Advance through chart top-to-bottom and left-to-right. If square S_i, S_j contains next state pair S_m, S_n and that pair labels a square already labeled "X", then S_i, S_j is labeled "X".**
4. **Continue executing Step 3 until no new squares are marked with "X".**
5. **For each remaining unmarked square S_i, S_j , then S_i and S_j are equivalent.**

When FSM implemented with gate logic, number of gates will depend on mapping between symbolic state names and binary encodings

4 states = 4 choices for first state, 3 for second, 2 for third, 1 for last
= 24 different encodings (4!)

Example for State Assignment: Traffic Light Controller

HG HY FG FY				HG HY FG FY				Inputs			Present State		Next State		Outputs				
00	01	10	11	10	00	01	11	C	TL	TS	Q ₁	Q ₀	P ₁	P ₀	ST	H ₁	H ₀	F ₁	F ₀
00	01	10	11	10	00	01	11	0	X	X	HG		HG		0	00		10	
00	01	11	10	10	00	11	01	X	0	X	HG		HG		0	00		10	
00	10	01	11	10	01	00	11	1	1	X	HG		HY		1	00		10	
00	10	11	01	10	01	11	00	X	X	0	HY		HY		0	01		10	
00	11	01	10	10	11	00	01	X	X	1	HY		FG		1	01		10	
00	11	10	01	10	11	01	00	1	0	X	FG		FG		0	10		00	
01	00	10	11	11	00	01	10	0	X	X	FG		FY		1	10		00	
01	00	11	10	11	01	00	10	X	1	X	FG		FY		1	10		00	
01	10	00	11	11	01	10	00	X	X	0	FY		FY		0	10		01	
01	10	11	00	11	10	00	01	X	X	1	FY		HG		1	10		01	
01	11	00	10	11	10	00	01												
01	11	10	00	11	10	01	00												

**24 state assignments
for the traffic light
controller**

Symbolic State Names: HG, HY, FG, FY

State Assignment

Some Sample Assignments for the Traffic Light Controller

Espresso input format:

```
.i 5
.o 7
.ilb c tl ts q1 q0
.ob p1 p0 st h1 h0 f1 f0
.p 10
0-- HG HG 00010
-0- HG HG 00010
11- HG HY 10010
--0 HY HY 00110
--1 HY FG 10110
10- FG FG 01000
0-- FG FY 11000
-1- FG FY 11000
--0 HY FY 01001
--1 HY HG 11001
.e
```

Two assignments: HG = 00, HY = 01, FG = 11, FY = 10
HG = 00, HY = 10, FG = 01, FY = 11

State Assignment

Random Assignments Evaluated with Espresso

```
.i 5
.o 7
.ilb c tl ts q1 q0
.ob p1 p0 st h1 h0 f1 f0
.p 9
11-00 0110000
10-11 1101000
--101 1010000
--010 1001001
---01 0100100
--110 0011001
---0- 0000010
0--11 1011000
-1-11 1011000
.e
```

26 literals
9 unique terms
several 5 and 4
input gates
13 gates total


```
.i 5
.o 7
.ilb c tl ts q1 q0
.ob p1 p0 st h1 h0 f1 f0
.p 8
11-0- 1010000
--010 1000100
0--01 1010000
--110 0110100
--111 0011001
----0 0000010
---01 0101000
--011 1101001
.e
```

21 literals
8 unique terms
no 5 input gates, 2 4 input gates
14 gates total

Pencil & Paper Heuristic Methods

State Maps: similar in concept to K-maps

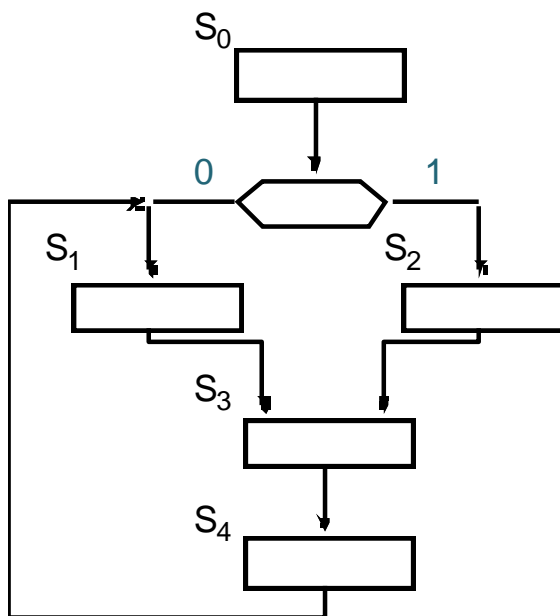If state X transitions to state Y, then assign "close" assignments to X and Y



State Name	Assignment		
	Q_2	Q_1	Q_0
S_0	0	0	0
S_1	1	0	1
S_2	1	1	1
S_3	0	1	0
S_4	0	1	1

Assignment

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	S_0		S_4	S_3
1		S_1	S_2	

State Map

State Name	Assignment		
	Q_2	Q_1	Q_0
S_0	0	0	0
S_1	0	0	1
S_2	0	1	0
S_3	0	1	1
S_4	1	1	1

Assignment

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	S_0	S_1	S_3	S_2
1			S_4	

State Map

State Assignment

Paper and Pencil Methods

Minimum Bit Distance Criterion


<i>Transition</i>	<i>First Assignment Bit Changes</i>	<i>Second Assignment Bit Changes</i>
S0 to S1:	2	1
S0 to S2:	3	1
S1 to S3:	3	1
S2 to S3:	2	1
S3 to S4:	1	1
S4 to S1:	2	2
	<hr/>	<hr/>
	13	7

Traffic light controller: HG = 00, HY = 01, FG = 11, FY = 10
yields minimum distance encoding but not best assignment!

State Assignment

Paper & Pencil Methods

 
Alternative heuristics based on input and output behavior as well as transitions:



Highest Priority


Adjacent assignments to:

 states that share a common next state
(group 1's in next state map)



Medium Priority

 states that share a common ancestor state
(group 1's in next state map)




Lowest Priority

states that have common output behavior
(group 1's in output map)

State Assignment

Pencil and Paper Methods

Example: 3-bit Sequence Detector

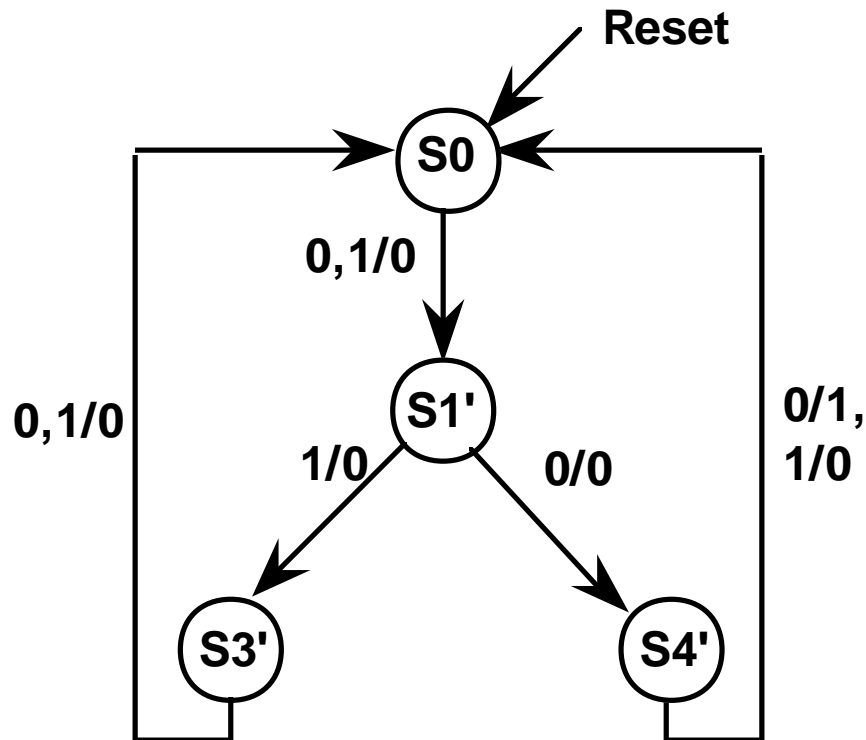

Highest Priority: (S3', S4')

Medium Priority: (S3', S4')

Lowest Priority:

0/0: (S0, S1', S3')

1/0: (S0, S1', S3', S4')

State Assignment

Paper and Pencil Methods

		Q0		0	1
Q1	0	S0	S1'		
	1	S3'	S4'		

Reset State = 00

Highest Priority Adjacency


		Q0		0	1
Q1	0	S0	S1'		
	1	S3'	S4'		

Not much difference in these two assignments

State Assignment

Paper & Pencil Methods

Another Example: 4 bit String Recognizer

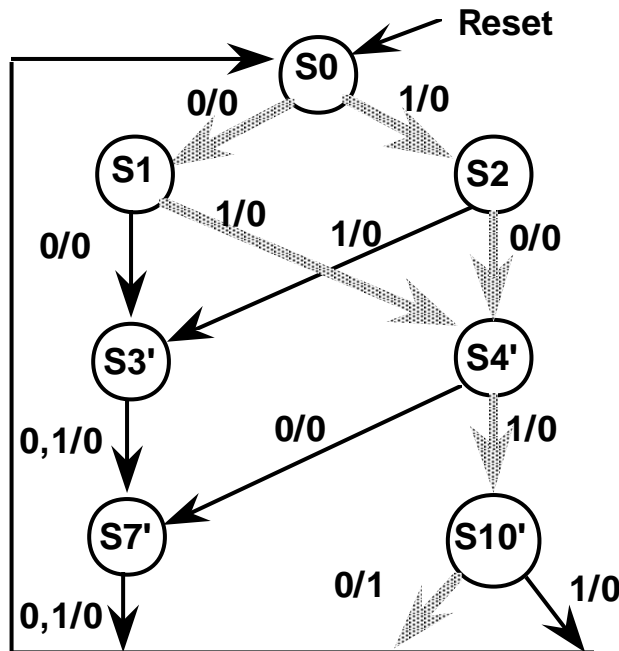

Highest Priority: (S3', S4'), (S7', S10')

Medium Priority:
(S1, S2), 2x(S3', S4'), (S7', S10')

Lowest Priority:
0/0: (S0, S1, S2, S3', S4', S7')
1/0: (S0, S1, S2, S3', S4', S7')

State Assignment

Paper & Pencil Methods

State Map

Q1 \ Q0	00	01	11	10
0	S0			
1				

Q1 \ Q0	00	01	11	10
0	S0		S3'	
1			S4'	

Q1 \ Q0	00	01	11	10
0	S0		S3'	S7'
1			S4'	S10'

Q1 \ Q0	00	01	11	10
0	S0	S1	S3'	S7'
1		S2	S4'	S10'

(a)

Q1 \ Q0	00	01	11	10
0	S0			
1				

Q1 \ Q0	00	01	11	10
0	S0			
1	S7'			S10'

Q1 \ Q0	00	01	11	10
0	S0		S3'	
1	S7'		S4'	S10'

Q1 \ Q0	00	01	11	10
0	S0	S1	S3'	
1	S7'	S2	S4'	S10'

(b)

00 = Reset = S0

(S1, S2), (S3', S4'), (S7', S10')
placed adjacently

Effect of Adjacencies on Next State Map

Current State	Next State	
	X = 0	X = 1
(S ₀) 000	001	101
(S ₁) 001	011	111
(S ₂) 101	111	011
(S ₃) 011	010	010
(S ₄) 111	010	110
(S ₇) 010	000	000
(S ₁₀) 110	000	000

Q ₀ \ Q ₂ Q ₁	00	01	11	10
00	0	0	0	X
01	1	0	0	X
11	1	0	1	0
10	0	0	0	1

P₂

Q ₀ \ Q ₂ Q ₁	00	01	11	10
00	0	0	0	X
01	0	0	0	X
11	1	1	1	1
10	1	1	1	1

P₁

Q ₀ \ Q ₂ Q ₁	00	01	11	10
00	1	0	0	X
01	1	0	0	X
11	1	0	0	1
10	1	0	0	1

P₀

Current State	Next State	
	X = 0	X = 1
(S ₀) 000	001	010
(S ₁) 001	011	100
(S ₂) 010	100	011
(S ₃) 011	101	101
(S ₄) 100	101	110
(S ₇) 101	000	000
(S ₁₀) 110	000	000

Q ₀ \ Q ₂ Q ₁	00	01	11	10
00	0	1	0	1
01	0	0	0	1
11	1	1	X	0
10	0	1	X	0

P₂

Q ₀ \ Q ₂ Q ₁	00	01	11	10
00	0	0	0	0
01	1	1	0	1
11	0	0	X	0
10	1	0	X	0

P₁

Q ₀ \ Q ₂ Q ₁	00	01	11	10
00	1	0	0	1
01	0	1	0	0
11	0	1	X	0
10	1	1	X	0

P₀

First encoding exhibits a better clustering of 1's in the next state map

State Assignment

One Hot Encodings

n states encoded in n flipflops

HG = 0001

HY = 0010

FG = 0100

FY = 1000

Complex logic for
discrete gate implementation

```
.i 7
.o 9
.ilb c t1 ts q3 q2 q1 q0
.ob p3 p2 p1 p0 st h1 h0 f1 f0
.p 10
0--0001000100010
-0-0001000100010
11-0001001010010
--00010001000110
--10010010010110
10-0100010001000
0--0100100011000
-1-0100100011000
--00010100001001
--10010000111001
.e
```

Espresso Inputs

```
.i 7
.o 9
.ilb c t1 ts q3 q2 q1 q0
.ob p3 p2 p1 p0 st h1 h0 f1 f0
.p 8
10-0100010001000
11-0001001010010
-0-0001000100010
0--0001000100010
0--0100100011000
-1-0100100011000
--00010101001111
--10010010111111
.e
```

Espresso Outputs

State Assignment

Computer-Based Methods

NOVA: State Assignment for 2-Level Circuit Networks

Input Constraints: states with same i/o mapped to same next state

Output Constraints: states which are successors of same predecessor

NOVA Input File for the Traffic Light Controller

inputs current_state next_state outputs

0--	HG	HG	00010
-0-	HG	HG	00010
11-	HG	HY	10010
--0	HY	HY	00110
--1	HY	FG	10110
10-	FG	FG	01000
0--	FG	FY	11000
-1-	FG	FY	11000
--0	FY	FY	01001
--1	FY	HG	11001

```
nova -e <encoding strategy> -t <nova input file>
```

State Assignment

Computer-Based Methods

Greedy: satisfy as many input constraints as possible

Hybrid: satisfy input constraints, more sophisticated improvement strategy

I/O Hybrid: satisfy both input and output constraints

Exact: satisfy ALL input conditions

Input Annealing: like hybrid, but uses an even improvement strategy

1-Hot: uses a 1-hot encoding

Random: uses a randomly generated encoding

State Assignment

Computer-Based Methods

	<u>HG</u>	<u>HY</u>	<u>FG</u>	<u>FY</u>	<u># of Product Terms</u>
Greedy (-e ig):	00	11	01	10	9
Hybrid (-e ih):	00	11	10	01	9
Exact (-e ie):	11	10	01	00	10
IO Hybrid (-e ioh):	00	01	11	10	9
I Annealing (-e ia):	01	10	11	10	9
Random (-e r):	11	00	01	10	9

-z HG on the command line forces NOVA to assign 00 to state HG

State Assignment

Computer Based Methods

More NOVA Examples:

3-bit Recognizer

- S0 S1 0
0 S1 S3 0
1 S1 S4 0
- S3 S0 0
0 S4 S0 1
1 S4 S0 0


	S0	S1'	S3'	S4'	terms
Greedy:	00	01	11	10	4
Hybrid:	00	01	10	11	4
Exact:	00	01	10	11	4
IO Hyb:	00	10	01	11	4
I Ann:	00	01	11	10	4
Random:	00	11	10	01	4

Computer Based Methods

More NOVA Examples:

4-bit Recognizer

0	S0	S1	0
1	S0	S2	0
0	S1	S3	0
1	S1	S4	0
0	S2	S4	0
1	S2	S3	0
-	S3	S7	0
0	S4	S7	0
1	S4	S7	0
-	S7	S0	0
0	S10	S0	1
1	S10	S0	0

 

Same adjacencies as
the heuristic method

	S0	S1	S2	S3'	S4'	S7'	S10'	terms
Greedy:	100	110	010	011	111	000	001	7
Hybrid:	101	110	111	001	011	000	010	7
Exact:	101	110	111	001	011	000	010	7
IO Hyb:	110	011	001	100	101	000	010	7
I Ann:	100	101	001	111	110	000	010	6
Rand:	011	100	101	110	111	000	001	7

State Assignment

Mustang

Oriented towards multi-level logic implementation

Goal is to reduce literal count, rather than product terms

Input Format:

.i	3			# inputs
.o	5			# outputs
.s	2			# of state bits
0--	HG	HG	00010	
-0-	HG	HG	00010	
11-	HG	HY	10010	
--0	HY	HY	00110	
--1	HY	FG	10110	
10-	FG	FG	01000	
0--	FG	FY	11000	
-1-	FG	FY	11000	
--0	FY	FY	01001	
--1	FY	HG	11001	

State Assignment

Mustang

Goal: maximum common subexpressions in next state function

Encoding Strategies:

Random

Sequential

One-Hot

***Fan-in:* states with common predecessors given adjacent assignment**

***Fan-out:* state with common next state and outputs given adjacent assignments**

State Assignment

Mustang

Traffic Light:

	HG	HY	FG	FY	# product terms
Random:	01	10	11	00	9
Sequential:	01	10	11	00	9
Fan-in:	00	01	10	11	8
Fan-out:	10	11	00	01	8

3 Bit String Recognizer:

	S0	S1	S3'	S4'	# product terms
Random:	01	10	11	00	5
Sequential:	01	10	11	00	5
Fan-in:	10	11	00	01	4
Fan-out:	10	11	00	01	4

4 Bit String Recognizer:

	S0	S1	S2	S3'	S4'	S7'	S10'	# product terms
Random:	101	010	011	110	111	001	000	8
Sequential:	001	010	011	100	101	110	111	8
Fan-in:	100	010	011	000	001	101	110	8
Fan-out:	110	010	011	100	101	000	001	6

To obtain multilevel implementations, must run misII

State Assignment

JEDI

of states; encoding bit length

Input Format:

Kinds of states

Kinds of outputs

```
.i 4
.o 4
.enum States 4 2 HG HY FG FY
.enum Colors 3 2 GREEN RED YELLOW
0--HG HG 0 GREEN RED
-0-HG HG 0 GREEN RED
11-HG HY 1 GREEN RED
--0 HY HY 0 YELLOW RED
--1 HY FG 1 YELLOW RED
10-FG FG 0 RED GREEN
0--FG FY 1 RED GREEN
-1-FG FY 1 RED GREEN
--0 FY FY 0 RED YELLOW
--1 FY HG 1 RED YELLOW
```

General encoding problems: best encodings for states and outputs

Encoding Strategies:

Random

Straightforward

One Hot

Input Dominant

Output Dominant

Modified Output Dominate

I/O Combination

State Assignment

JEDI

Traffic Light:

	HG	HY	FG	FY	Grn	Yel	Red	# product terms
Input:	00	10	11	01	11	01	00	9
Output:	00	01	11	10	10	11	01	9
Comb:	00	10	11	01	10	00	01	9
Output':	01	00	10	11	10	00	01	10

3 Bit String Recognizer:

	S0	S1	S3'	S4'	# product terms
Input:	01	10	11	00	4
Output:	01	10	11	00	4
Comb.:	10	11	00	01	4
Output':	10	11	00	01	4

4 Bit String Recognizer:

	S0	S1	S2	S3'	S4'	S7'	S10'	# product terms
Input:	111	101	100	010	110	011	001	7
Output:	101	110	100	010	000	111	011	7
Comb.:	100	011	111	110	010	000	101	7
Output':	001	100	101	010	011	000	111	8

To obtain multilevel implementations, must run misII

State Assignment

Mustang vs. Jedi

Traffic Light Controller

Mustang

$$\begin{aligned} Q1 &= HL0 \cdot TS + FL0 \cdot TS' + FL0' \cdot P1 \\ Q0 &= Q1 \cdot C' \cdot P1 + C \cdot TL \cdot P0' + TS' \cdot P0 \\ ST &= Q0 \cdot P0' + Q0' \cdot P0 \\ HL1 &= FL0 + P1 \cdot P0' \\ HL0 &= P1' \cdot P0 \\ FL1 &= P1' \\ FL0 &= HL0' \cdot P0 \end{aligned}$$

Fewer wires

Jedi

$$\begin{aligned} Q1 &= HL1 \cdot C \cdot TL + HL0 + FL1 \cdot C \cdot TL' \\ Q0 &= HL0 \cdot TS + FL1 + FL0 \cdot TS' \\ ST &= Q1 \cdot HL1 + Q1' \cdot FL0 + HL1' \cdot FL1' \cdot TS \\ HL1 &= P1' \cdot P0' \\ HL0 &= P1 \cdot P0' \\ FL1 &= HL0' \cdot P1 \\ FL0 &= HL1' \cdot P1' \end{aligned}$$

Fewer literals

Choice of Flipflops

J-K FFs: reduce gate count, increase # of connections

D FFs: simplify implementation process, decrease # of connections

Procedure:

- 1. Given state assignments, derive the next state maps from the state transition table**
- 2. Remap the next state maps given excitation tables for a given FF**
- 3. Minimize the remapped next state function**

Examples

4 bit Sequence Detector using NOVA derived state assignment

**Encoded State
Transition Table**

Present State	Next State		Output	
	I=0	I=1	I=0	I=1
000 (S_0)	011 (S_1)	010 (S_2)	0	0
011 (S_1)	101 (S_3)	111 (S_4)	0	0
010 (S_2)	111 (S_4)	101 (S_3)	0	0
101 (S_3)	100	100 (S_7)	0	0
111 (S_4)	(S_7)	110	0	0
100 (S_7)	100	(S_{10})	0	0
110 (S_{10})	(S_7)	000	1	0

**Encoded Next
State Map**

Present State	Next State	
	I=0	I=1
000	011	010
001	XXX	XXX
010	111	101
011	101	111
100	000	000
101	100	100
110	000	000
111	100	110

Choice of Flipflops

D FF Implementation

$$D_{Q2+} = \overline{Q2} \cdot Q1 + Q0$$

$$D_{Q1+} = Q1 \cdot Q0 \cdot I + \overline{Q2} \cdot \overline{Q0} \cdot I + Q2 \cdot Q1$$

$$D_{Q0+} = \overline{Q2} \cdot Q1 + \overline{Q2} \cdot I$$

6 product terms
15 literals

Contemporary Logic Design FSM Optimization

Q ₂ Q ₁		Q ₀ I			
		00	01	11	10
00	00	0	0	X	X
01	01	1	1	1	1
11	11	0	0	1	1
10	10	0	0	1	1

Q₂⁺

Q ₂ Q ₁		Q ₀ I			
		00	01	11	10
00	00	1	1	X	X
01	01	1	0	1	0
11	11	0	0	1	0
10	10	0	0	0	0

Q₁⁺

Q ₂ Q ₁		Q ₀ I			
		00	01	11	10
00	00	1	0	X	X
01	01	1	1	1	1
11	11	0	0	0	0
10	10	0	0	0	0

Q₀⁺

J-K Implementation

Present State	Next State		Remapped Next State			
	I=0	I=1	J	K	J	K
			I=0	I=0	I=1	I=1
000	011	010	011	XXX	010	XXX
001	XXX	XXX	XXX	XXX	XXX	XXX
010	111	101	1X1	X0X	1X1	X1X
011	101	111	1XX	X10	1XX	X00
100	000	000	X00	1XX	X00	1XX
101	100	100	X0X	0X1	X0X	0X1
110	000	000	XX0	11X	XX0	11X
111	100	110	XXX	011	XXX	001

Remapped Next State Table

Choice of Flipflops

J-K Implementation (continued)

$$J_{Q2+} = Q1$$

$$K_{Q2+} = \overline{Q0}$$

$$J_{Q1+} = \overline{Q2}$$

$$K_{Q1+} = \overline{Q0} \cdot I + Q0 \cdot \overline{I} + Q2 \cdot \overline{Q0}$$

$$J_{Q0+} = \overline{Q2} \cdot Q1 + \overline{Q2} \cdot \overline{I}$$

$$K_{Q0+} = Q2$$

9 unique terms
14 literals

$Q_2 Q_1$		$Q_0 I$			
		00	01	11	10
00	0	0	X	X	
01	1	1	1	1	
11	X	X	X	X	
10	X	X	X	X	

J_{Q_2+}

$Q_2 Q_1$		$Q_0 I$			
		00	01	11	10
00	X	X	X	X	
01	X	X	X	X	
11	1	1	0	0	
10	1	1	0	0	

K_{Q_2+}

$Q_2 Q_1$		$Q_0 I$			
		00	01	11	10
00	1	1	X	X	
01	X	X	X	X	
11	X	X	X	X	
10	0	0	0	0	

J_{Q_1+}

$Q_2 \ Q_1$		$Q_0 \ I$			
		00	01	11	10
00	X	X	X	X	
01	0	1	0	1	
11	1	1	0	1	
10	X	X	X	X	

K_{Q_1+}

$Q_2 \backslash Q_1$		Q_0			
		00	01	11	10
00	1	0	X	X	
01	1	1	X	X	
11	0	0	X	X	
10	0	0	X	X	

J_{Q_0+}

$Q_2 Q_1$		$Q_0 I$			
		00	01	11	10
00	X	X	X	X	
01	X	X	0	0	
11	X	X	1	1	
10	X	X	1	1	



K_{Q_0+}

Why Partition?

mapping FSMs onto programmable logic components:

limited number of input/output pins

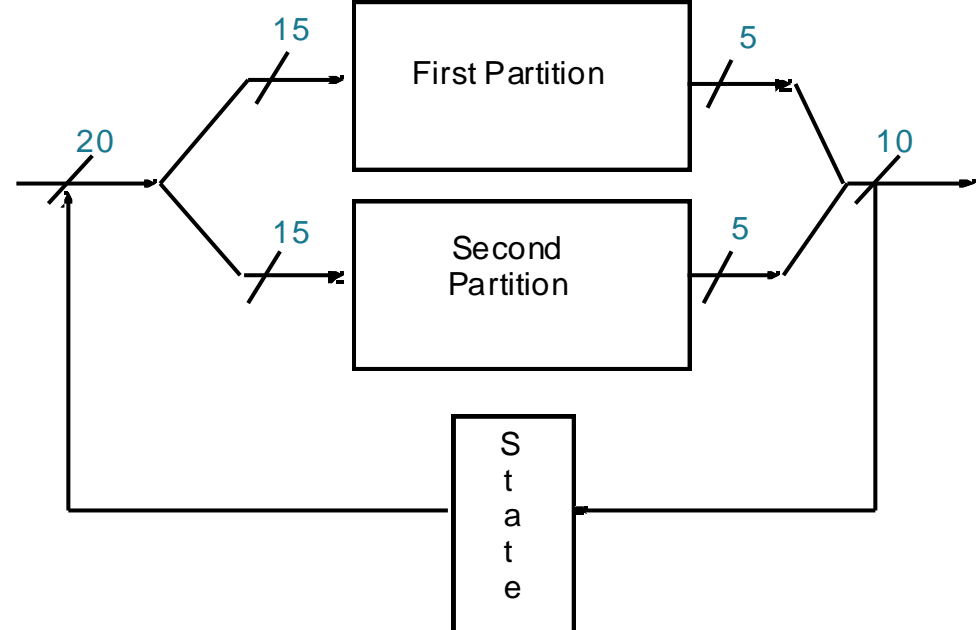 limited number of product terms or other programmable resources




Example of Input/Output Partitioning:

5 outputs depend on 15 inputs

5 outputs depend on different overlapping set of 15 inputs



Introduction of Idle States

Before Partitioning

 


Introduction of Idle States

After Partitioning

  


Rules for Partitioning

 Rule #1: Source State Transformation; SA is the Idle State




 Rule #2: Destination State Transformation




Rules for Partitioning

 Rule #3: Multiple Transitions with Same Source or Destination




Rule #4: Hold Condition for Idle State

 

Finite State Machine Partitioning

Another Example

 


6 state up/down counter

building block has 2 FFs + combinational logic

Finite State Machine Partitioning

6 State Up/Down Counter

 

Introduction of the two idle state SA, SB

Count sequence S0, S1, S2, S3, S4, S5:

S2 goes to SA and holds, leaves after S5

S5 goes to SB and holds, leaves after S2

Down sequence is similar

Chapter Summary

- ***Optimization of FSM***

State Reduction Methods: Row Matching, Implication Chart

State Assignment Methods: Heuristics and Computer Tools

- ***Implementation Issues***

Choice of Flipflops

Finite State Machine Partitioning