

Chapter # 5: Arithmetic Circuits

Contemporary Logic Design

**Randy H. Katz
University of California, Berkeley**

June 1993

Motivation

Arithmetic circuits are excellent examples of comb. logic design

- ***Time vs. Space Trade-offs***

Doing things fast requires more logic and thus more space

Example: carry lookahead logic

- ***Arithmetic Logic Units***

Critical component of processor datapath

Inner-most "loop" of most computer instructions

Chapter Overview

- ***Binary Number Representation***
Sign & Magnitude, Ones Complement, Twos Complement
- ***Binary Addition***
Full Adder Revisited
- ***ALU Design***
- ***BCD Circuits***
- ***Combinational Multiplier Circuit***
- ***Design Case Study: 8 Bit Multiplier***

Number Systems

Representation of Negative Numbers

Representation of positive numbers same in most systems

Major differences are in how negative numbers are represented

Three major schemes:

sign and magnitude

ones complement

twos complement

Assumptions:

we'll assume a 4 bit machine word

16 different values can be represented


roughly half are positive, half are negative

Special Powers of 2

- 2^{10} (1024) is Kilo, denoted "K"
 - 2^{20} (1,048,576) is Mega, denoted "M"
 - 2^{30} (1,073, 741,824) is Giga, denoted "G"
-
- http://myweb.utapei.edu.tw/~cyang/class/Digital_System/ch_01.pdf

Number Systems

Sign and Magnitude Representation

 

High order bit is sign: 0 = positive (or zero), 1 = negative

Three low order bits is the magnitude: 0 (000) thru 7 (111)

Number range for n bits = $\pm 2^{n-1} - 1$

Representations for 0

Number Systems

Sign and Magnitude

Cumbersome addition/subtraction

Must compare magnitudes to determine sign of result

Ones Complement

N is positive number, then \overline{N} is its negative 1's complement

$$\overline{N} = (2^n - 1) - N$$

Example: 1's complement of 7

Shortcut method:

simply compute bit wise complement

$$0111 \rightarrow 1000$$

$$2^4 = 10000$$

$$-1 = \underline{00001}$$

$$1111$$


$$-7 = \underline{0111}$$

$$1000$$

= -7 in 1's comp.

Number Systems

Ones Complement

 

$\begin{array}{c} + \\ \swarrow \\ 0 \ 100 = +4 \end{array}$
 $\begin{array}{c} 1 \ 011 = -4 \\ \searrow \\ - \end{array}$

Subtraction implemented by addition & 1's complement


Still two representations of 0! This causes some problems

Some complexities in addition

Number Representations

Twos Complement

 *like 1's comp
except shifted
one position
clockwise*



$0\ 100 = +4$
 $1\ 100 = -4$

Only one representation for 0

One more negative number than positive number

Number Systems

Twos Complement Numbers

$$N^* = 2^n - N$$

Example: Twos complement of 7

$$2^4 = 10000$$

$$\text{sub } 7 = \underline{0111}$$

1001 = repr. of -7

Example: Twos complement of -7

$$2^4 = 10000$$

$$\text{sub } -7 = \underline{1001}$$

0111 = repr. of 7

Shortcut method:

Twos complement = bitwise complement + 1

0111 → 1000 + 1 → 1001 (representation of -7)

1001 → 0110 + 1 → 0111 (representation of 7)

Number Representations

Addition and Subtraction of Numbers

Sign and Magnitude

result sign bit is the
same as the operands'
sign

$$\begin{array}{r}
 4 \quad 0100 \\
 + 3 \quad 0011 \\
 \hline
 7 \quad 0111
 \end{array}$$

$$\begin{array}{r}
 -4 \quad 1100 \\
 + (-3) \quad 1011 \\
 \hline
 -7 \quad 1111
 \end{array}$$

when signs differ,
operation is subtract,
sign of result depends
on sign of number with
the larger magnitude

$$\begin{array}{r}
 4 \quad 0100 \\
 - 3 \quad 1011 \\
 \hline
 1 \quad 0001
 \end{array}$$

$$\begin{array}{r}
 -4 \quad 1100 \\
 + 3 \quad 0011 \\
 \hline
 -1 \quad 1001
 \end{array}$$

Number Systems

Addition and Subtraction of Numbers

Ones Complement Calculations

$$\begin{array}{r} 4 \quad 0100 \\ + 3 \quad 0011 \\ \hline \end{array}$$

$$7 \quad 0111$$

End around carry

$$\begin{array}{r} -4 \quad 1011 \\ + (-3) \quad 1100 \\ \hline \end{array}$$

$$-7 \quad 10111$$

1

$$1000$$

$$\begin{array}{r} 4 \quad 0100 \\ - 3 \quad 1100 \\ \hline \end{array}$$

$$1 \quad 10000$$

End around carry

1

$$0001$$

$$\begin{array}{r} -4 \quad 1011 \\ + 3 \quad 0011 \\ \hline \end{array}$$

$$-1 \quad 1110$$

Number Systems

Addition and Subtraction of Binary Numbers

Ones Complement Calculations

Why does end-around carry work?

Its equivalent to subtracting 2^n and adding 1

$$M - N = M + \overline{N} = M + (2^n - 1 - N) = (M - N) + 2^n - 1 \quad (M > N)$$

$$\begin{aligned} -M + (-N) &= \overline{M} + \overline{N} = (2^n - M - 1) + (2^n - N - 1) \\ &= 2^n + [2^n - 1 - (M + N)] - 1 \end{aligned} \quad M + N < 2^{n-1}$$

after end around carry:

$$= 2^n - 1 - (M + N)$$

this is the correct form for representing $-(M + N)$ in 1's comp!

Number Systems

Addition and Subtraction of Binary Numbers

Twos Complement Calculations

$$\begin{array}{r} 4 \quad 0100 \\ + 3 \quad 0011 \\ \hline 7 \quad 0111 \end{array}$$

$$\begin{array}{r} -4 \quad 1100 \\ + (-3) \quad 1101 \\ \hline -7 \quad 11001 \end{array}$$

If carry-in to sign =
carry-out then ignore
carry

if carry-in differs from
carry-out then overflow

$$\begin{array}{r} 4 \quad 0100 \\ - 3 \quad 1101 \\ \hline 1 \quad 10001 \end{array}$$

$$\begin{array}{r} -4 \quad 1100 \\ + 3 \quad 0011 \\ \hline -1 \quad 1111 \end{array}$$

**Simpler addition scheme makes twos complement the most common
choice for integer number systems within digital systems**

Number Systems

Addition and Subtraction of Binary Numbers

Twos Complement Calculations

Why can the carry-out be ignored?

$-M + N$ when $N > M$:

$$M^* + N = (2^n - M) + N = 2^n + (N - M)$$

Ignoring carry-out is just like subtracting 2^n

$-M + -N$ where $N + M < \text{or} = 2^{n-1}$



$$\begin{aligned} -M + (-N) &= M^* + N^* = (2^n - M) + (2^n - N) \\ &= 2^n - (M + N) + 2^n \end{aligned}$$

After ignoring the carry, this is just the right twos compl. representation for $-(M + N)$!

Number Systems

Overflow Conditions

  Add two positive numbers to get a negative number
or two negative numbers to get a positive number



Number Systems

Overflow Conditions

5 0 1 1 1
 0 1 0 1

3 0 0 1 1

-8 1 0 0 0

Overflow

5 0 0 0 0
 0 1 0 1

2 0 0 1 0

7 0 1 1 1

No overflow

-7 1 0 0 0
 1 0 0 1

-2 1 1 0 0

7 1 0 1 1 1

Overflow

-3 1 1 1 1
 1 1 0 1

-5 1 0 1 1

-8 1 1 0 0 0

No overflow

Overflow when carry in to sign does not equal carry out

RADIX OR BASE:-

The radix or base of a number system is defined as the number of different digits which can occur in each position in the number system.

RADIX POINT :-

The generalized form of a decimal point is known as radix point. In any positional number system the radix point divides the integer and fractional part.

$$N_r = [\text{Integer part} \cdot \text{Fractional part}]$$

↑
Radix point

- http://astorissa.in/Docs/Study_Materials/Electrical/4th_Semester/DIGITAL_ELECTRONICS.pdf

• General form of base-r system

$$a_n \cdot r^n + a_{n-1} \cdot r^{n-1} + \cdots + a_2 \cdot r^2 + a_1 \cdot r^1 + a_0 + a_{-1} \cdot r^{-1} + a_{-2} \cdot r^{-2} + \cdots + a_{-m} \cdot r^{-m}$$

Coefficient: $a_j = 0 \text{ to } r - 1$

Number Systems

Example: Base-2 number

$$(11010.11)_2 = (26.75)_{10}$$

$$= 1 \times 2^4 + 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 0 \times 2^0 + 1 \times 2^{-1} + 1 \times 2^{-2}$$

Example: Base-5 number

$$(4021.2)_5$$

$$= 4 \times 5^3 + 0 \times 5^2 + 2 \times 5^1 + 1 \times 5^0 + 2 \times 5^{-1} = (511.5)_{10}$$

Example: Base-8 number

$$(127.4)_8$$

$$= 1 \times 8^3 + 2 \times 8^2 + 1 \times 8^1 + 7 \times 8^0 + 4 \times 8^{-1} = (87.5)_{10}$$

Example: Base-16 number

$$(B65F)_{16} = 11 \times 16^3 + 6 \times 16^2 + 5 \times 16^1 + 15 \times 16^0 = (46,687)_{10}$$

- http://myweb.utapei.edu.tw/~cyang/class/Digital_System/ch_01.pdf

Half Adder

With two's complement numbers, addition is sufficient


A _i	B _i	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

A _i \ B _i	0	1
0	0	1
1	1	0

A _i \ B _i	0	1
0	0	0
1	0	1

$$\begin{aligned}\text{Sum} &= \overline{A_i} B_i + A_i \overline{B_i} \\ &= A_i \oplus B_i\end{aligned}$$

$$\text{Carry} = A_i B_i$$

 


Half-adder Schematic

Networks for Binary Addition

Full Adder

**Cascaded Multi-bit
Adder**

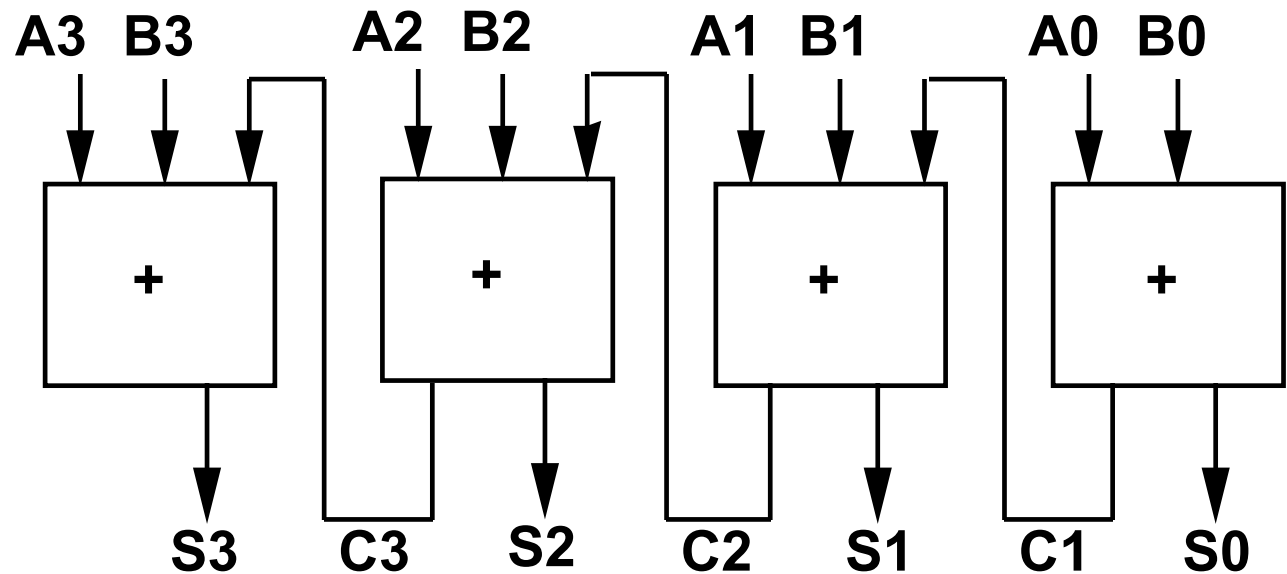

usually interested in adding more than two bits

this motivates the need for the full adder

Networks for Binary Addition

Full Adder

A	B	CI	S	CO
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

		A B			
CI	S	00	01	11	10
		0	1	0	1
1	S	1	0	1	0


		A B			
CI	CO	00	01	11	10
		0	0	1	0
1	CO	0	1	1	1

$$S = CI \text{ xor } A \text{ xor } B$$


$$CO = B \text{ CI} + A \text{ CI} + A B = CI (A + B) + A B$$

Full Adder/Half Adder


Standard Approach: 6 Gates

 

Alternative Implementation: 5 Gates

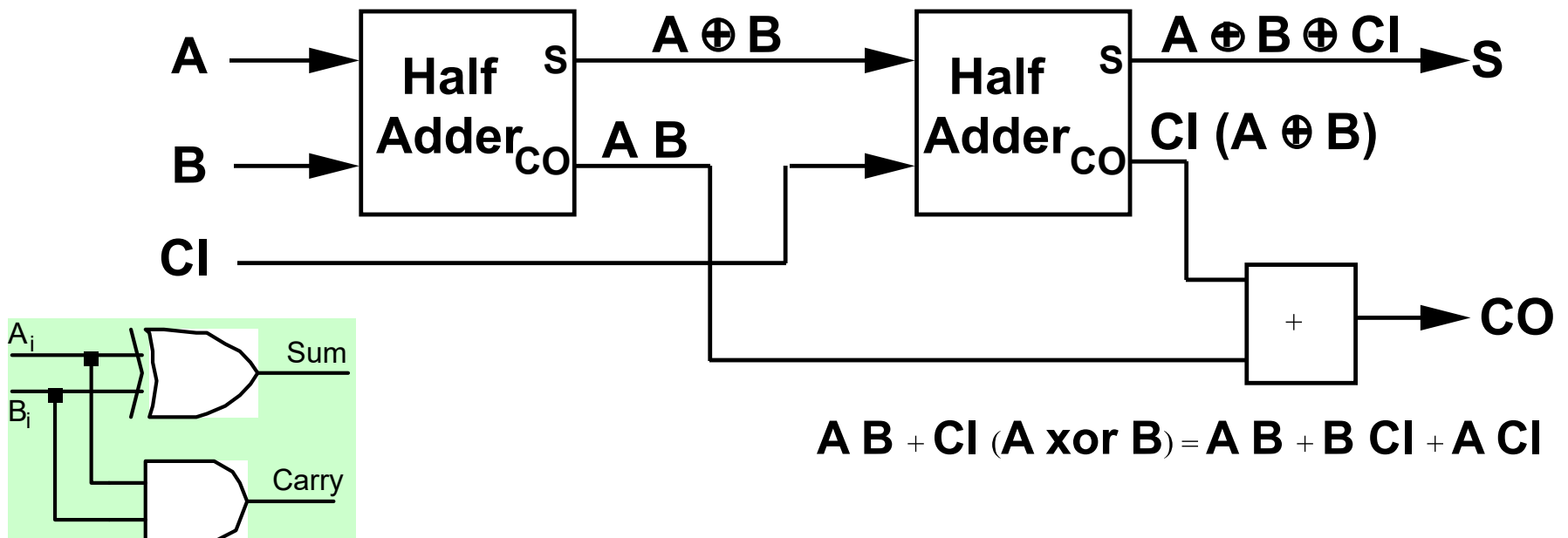

Adder/Subtractor


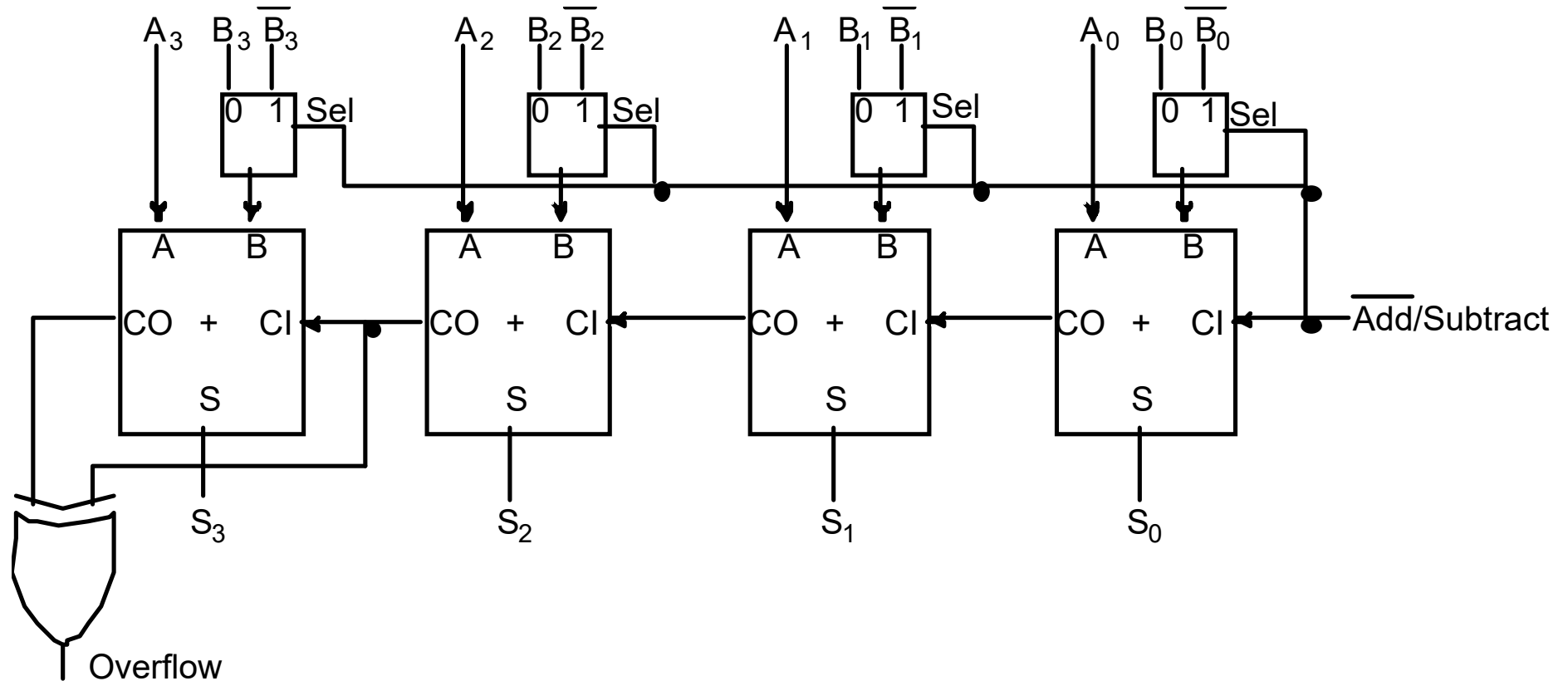


$$\mathbf{A - B = A + (-B) = A + \overline{B} + 1}$$

Subtraction in 2's complement number systems

Carry Lookahead Circuits

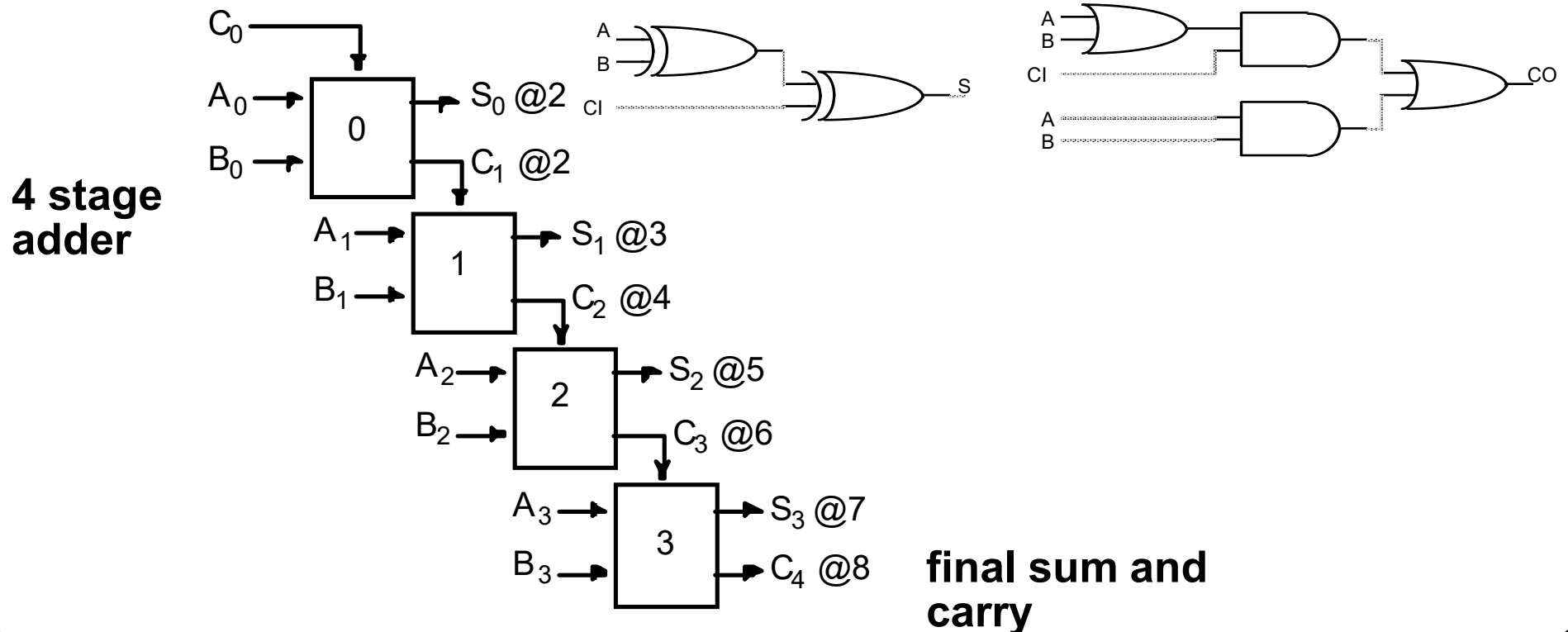 
Critical delay: the propagation of carry from low to high order stages



Networks for Binary Addition

Carry Lookahead Circuits

 Critical delay: the propagation of carry from low to high order stages



T0: Inputs to the adder are valid

T2: Stage 0 carry out (C1)

T4: Stage 1 carry out (C2)

T6: Stage 2 carry out (C3)

T8: Stage 3 carry out (C4)

2 delays to compute sum

**but last carry not ready
until 6 delays later**

Networks for Binary Addition

Carry Lookahead Logic

Carry Generate $G_i = A_i B_i$ *must generate carry when $A = B = 1$*

Carry Propagate $P_i = A_i \text{ xor } B_i$ *carry in will equal carry out here*

Sum and Carry can be reexpressed in terms of generate/propagate:

$$S_i = A_i \text{ xor } B_i \text{ xor } C_i = P_i \text{ xor } C_i$$

$$C_{i+1} = A_i B_i + A_i C_i + B_i C_i$$

$$= A_i B_i + C_i (A_i + B_i)$$

$$= A_i B_i + C_i (A_i \text{ xor } B_i)$$

$$= G_i + C_i P_i$$

Networks for Binary Addition

Carry Lookahead Logic

Reexpress the carry logic as follows:

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$


$$C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

Each of the carry equations can be implemented in a two-level logic network

Variables are the adder inputs and carry in to stage 0:





Networks for Binary Addition

Carry Lookahead Implementation

 

Adder with Propagate and Generate Outputs

Increasingly complex logic

    


Carry Lookahead Logic

Cascaded Carry Lookahead


Carry lookahead
logic generates
individual carries

sums computed
much faster

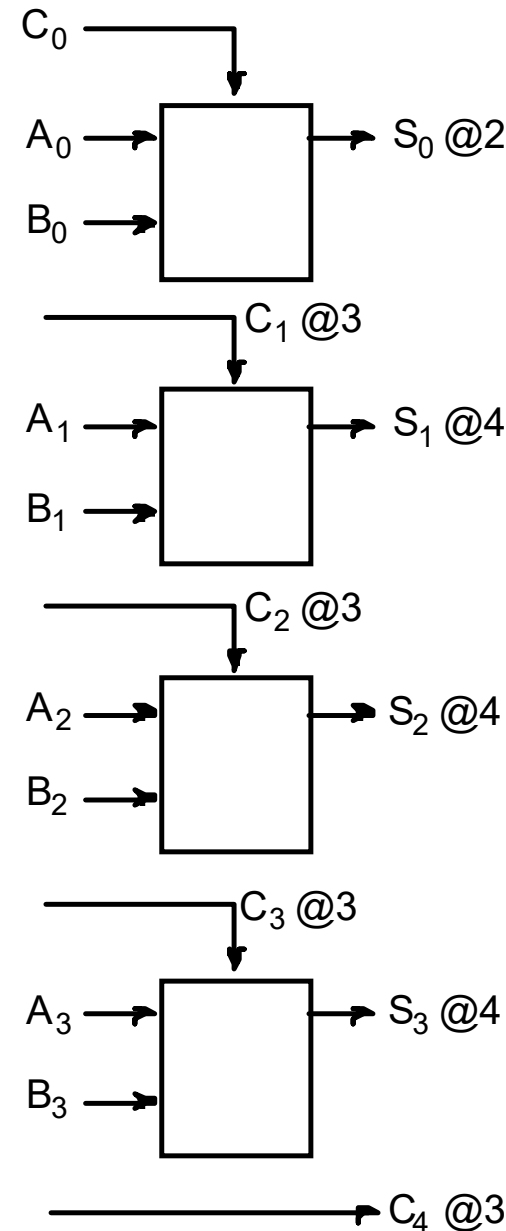

Carry Lookahead Logic

Cascaded Carry Lookahead

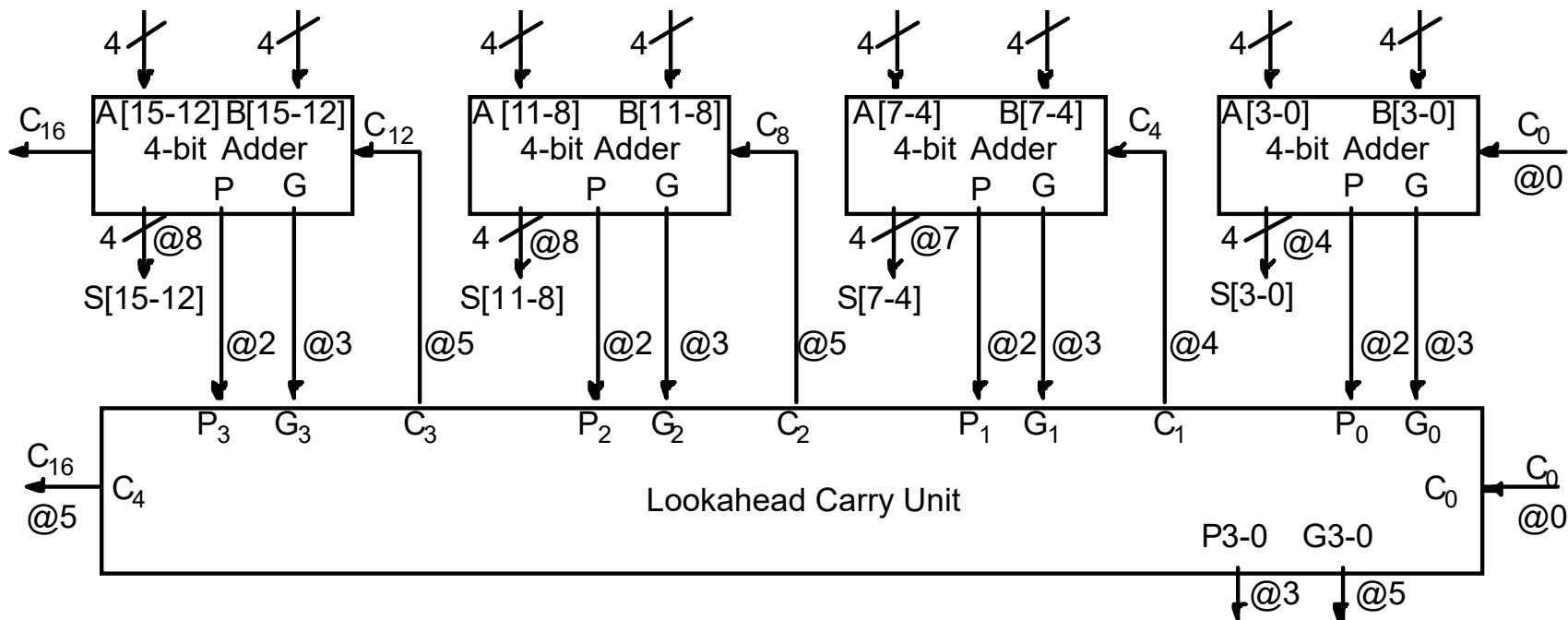


4 bit adders with internal carry lookahead


second level carry lookahead unit, extends lookahead to 16 bits

ahead logic. Each 4-bit adder computes its own "group" carry propagate and generate: the group propagate is the AND of P_3, P_2, P_1, P_0 , while the group generate is the expression $G_3 + G_2P_3 + G_1P_3P_2 + G_0P_3P_2P_1$.

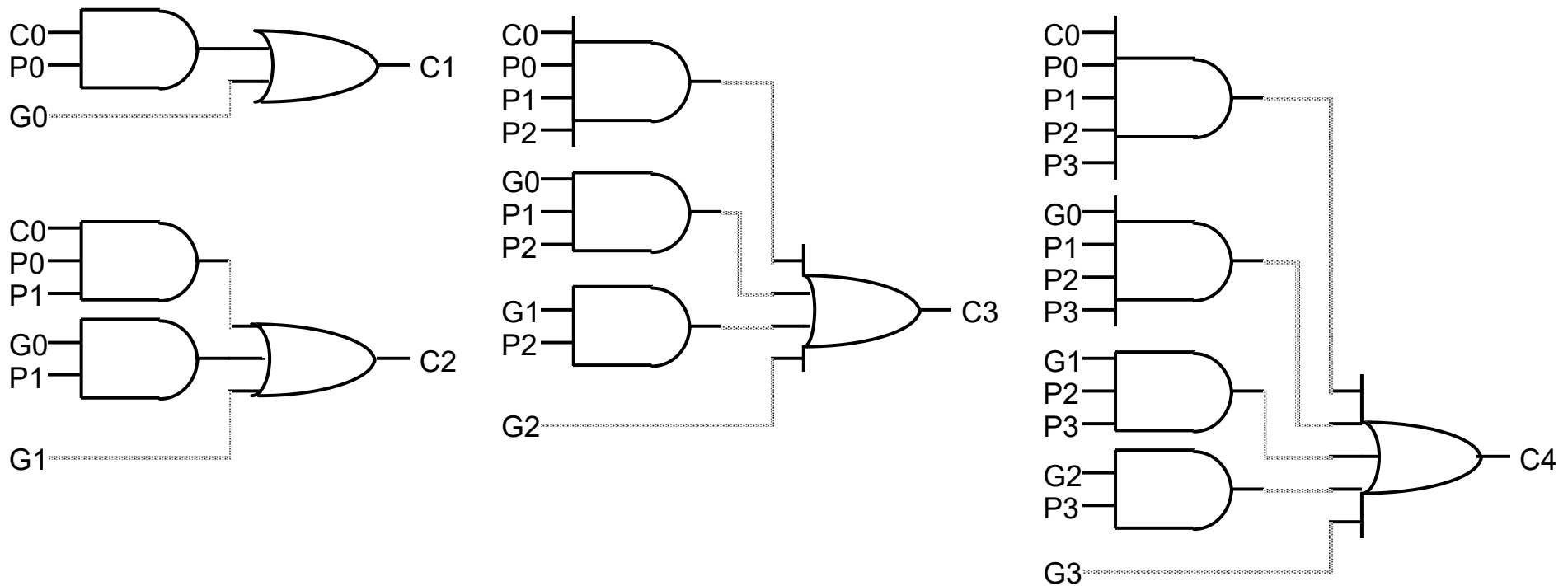Calculating C1-4, C5-8, C9-12 etc. in each block



 How each block computes 'group' G and P, case by case.





ahead logic. Each 4-bit adder computes its own “group” carry propagate and generate: the group propagate is the AND of P_3, P_2, P_1, P_0 , while the group generate is the expression $G_3 + G_2P_3 + G_1P_3P_2 + G_0P_3P_2P_1$.

Carry-lookahead adder with cascaded carry-lookahead logic


■ Carry-lookahead adder

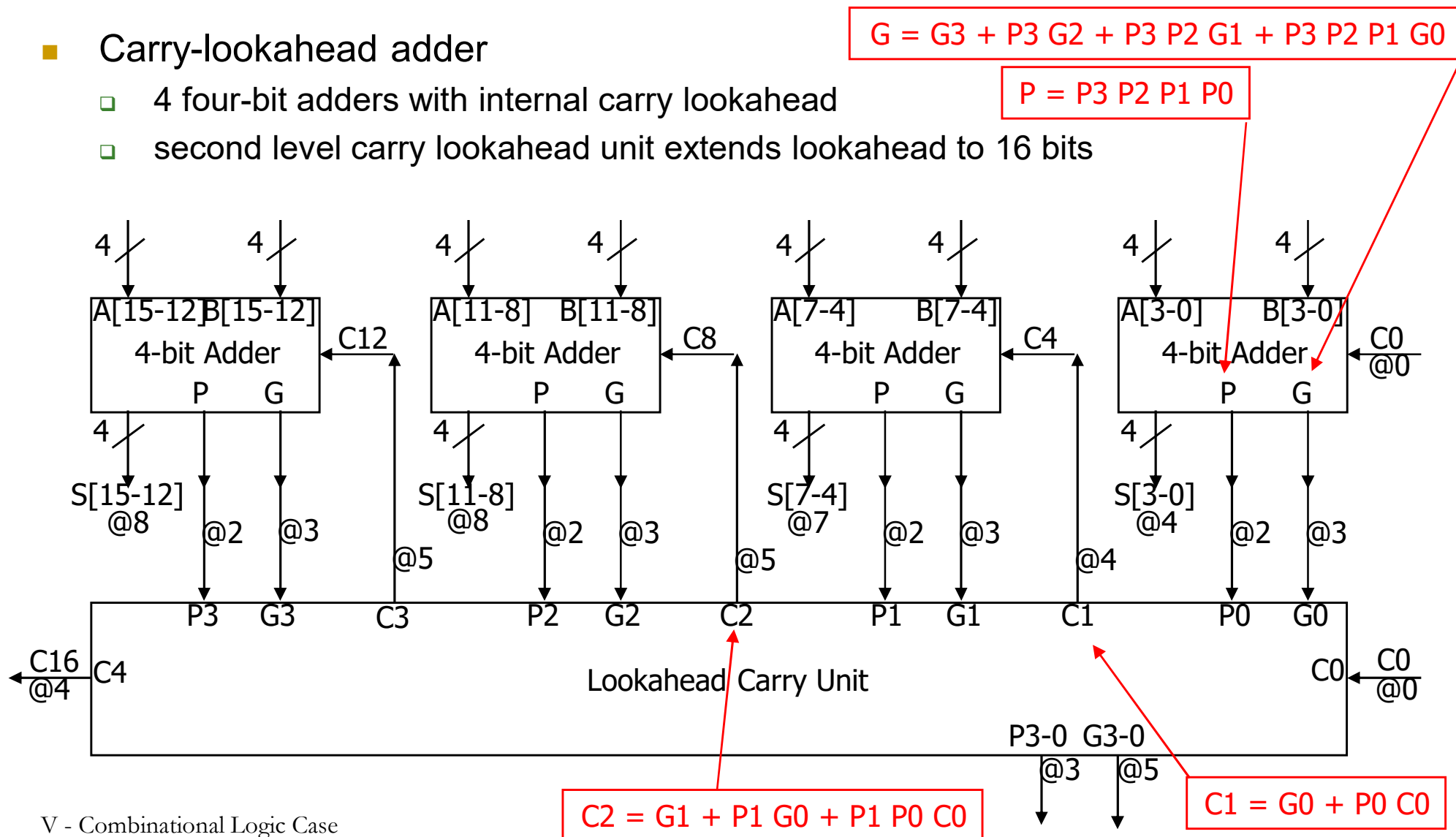- 4 four-bit adders with internal carry lookahead
- second level carry lookahead unit extends lookahead to 16 bits




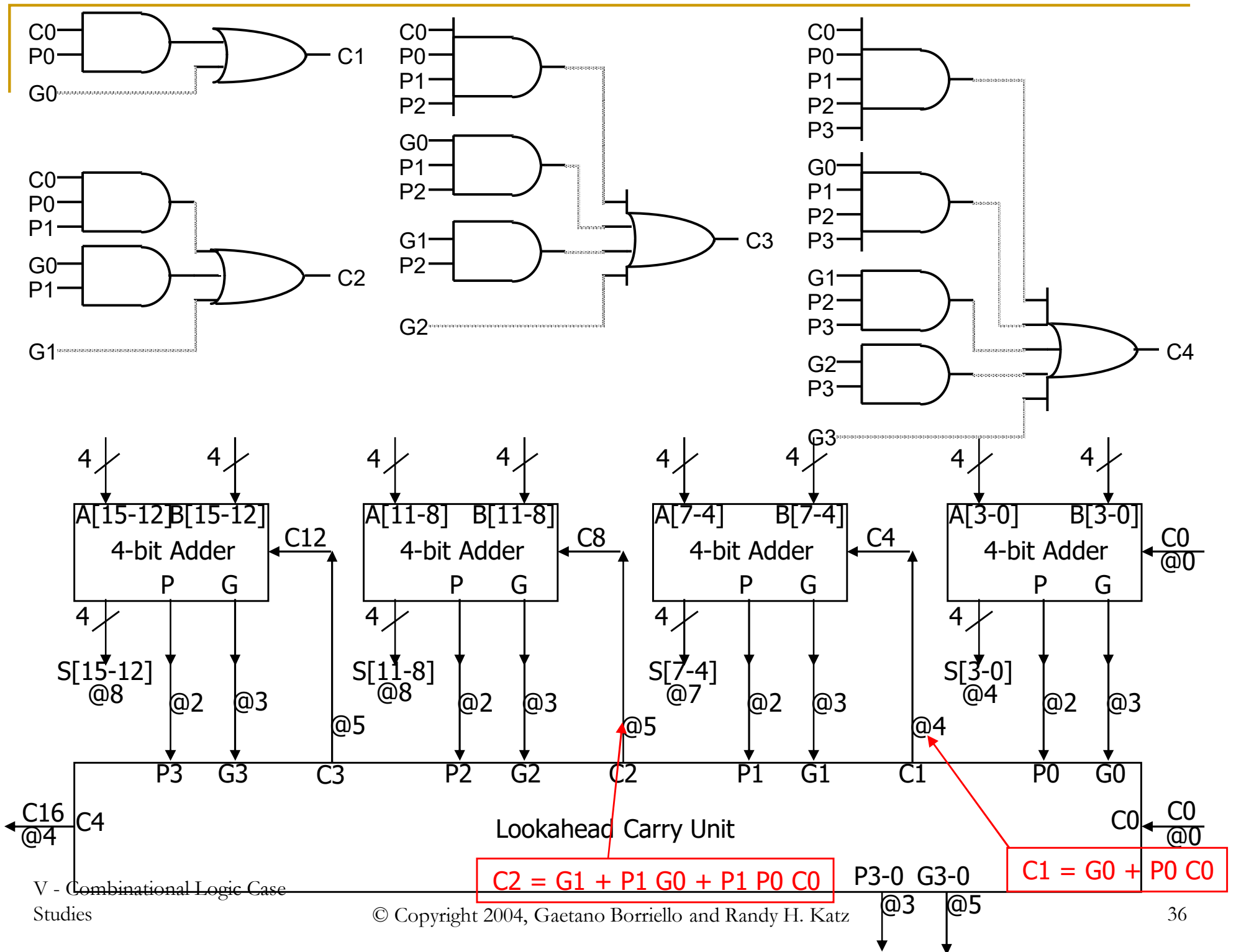


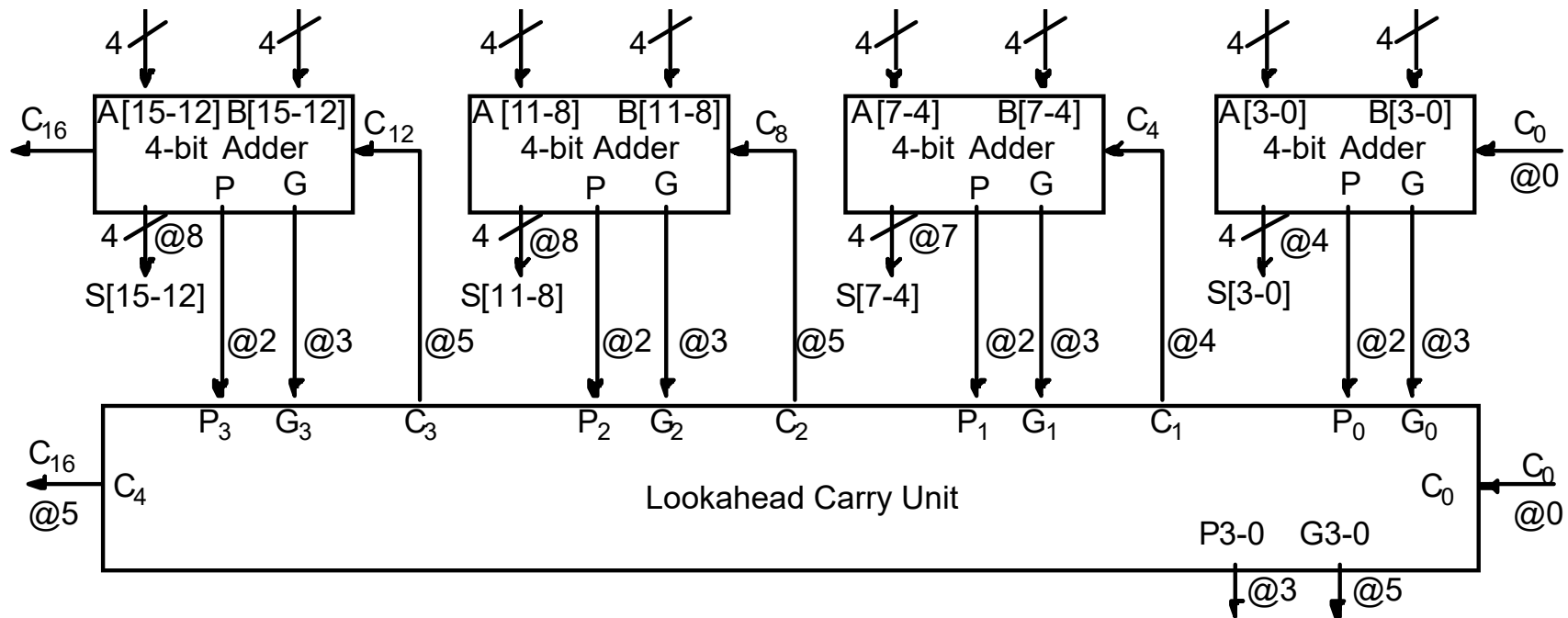Carry Lookahead Logic Cascaded Carry Lookahead



Carry Select Adder

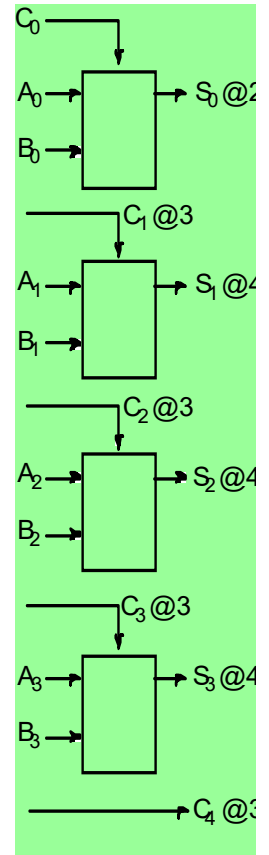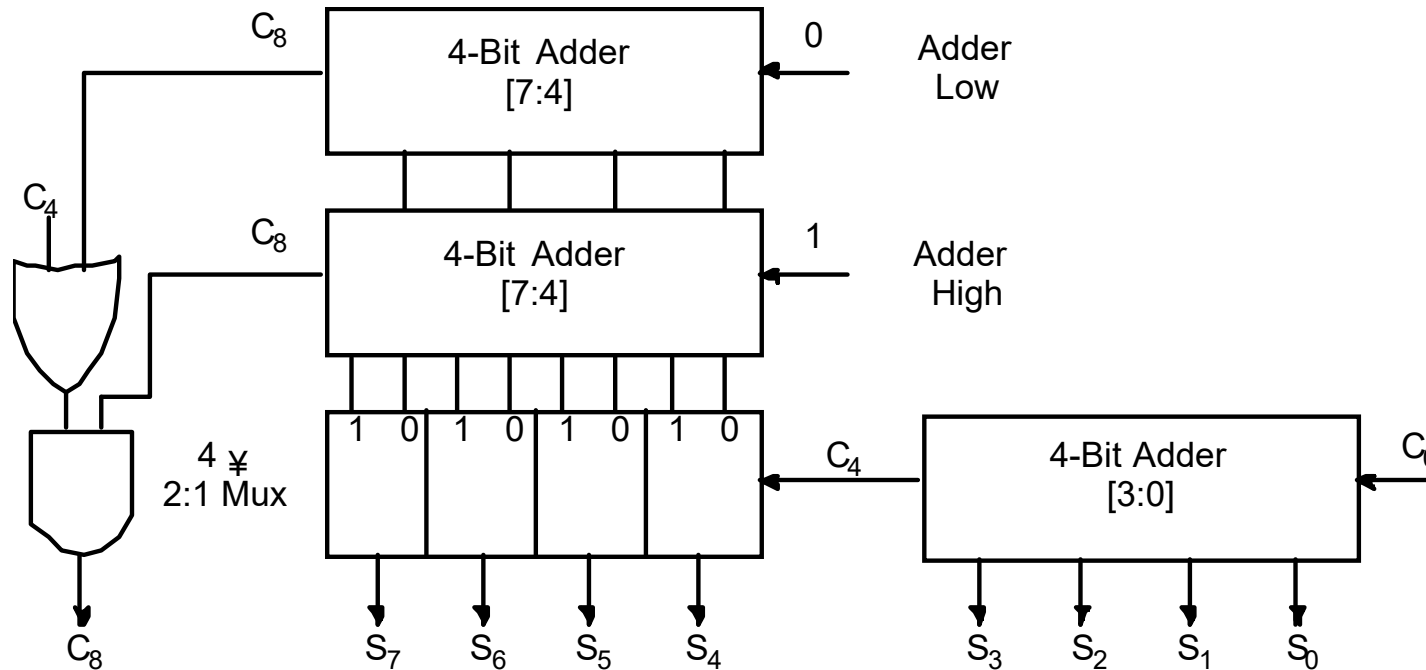Redundant hardware to make carry calculation go faster



compute the high order sums in parallel

one addition assumes carry in = 0

the other assumes carry in = 1

Arithmetic Logic Unit Design

Sample ALU

M = 0, Logical Bitwise Operations

S1	S0	Function	Comment
0	0	$F_i = A_i$	Input A_i transferred to output
0	1	$F_i = \text{not } A_i$	Complement of A_i transferred to output
1	0	$F_i = A_i \text{ xor } B_i$	Compute XOR of A_i, B_i
1	1	$F_i = A_i \text{ xnor } B_i$	Compute XNOR of A_i, B_i

M = 1, C0 = 0, Arithmetic Operations

0	0	$F = A$	Input A passed to output
0	1	$F = \text{not } A$	Complement of A passed to output
1	0	$F = A \text{ plus } B$	Sum of A and B
1	1	$F = (\text{not } A) \text{ plus } B$	Sum of B and complement of A

M = 1, C0 = 1, Arithmetic Operations

0	0	$F = A \text{ plus } 1$	Increment A
0	1	$F = (\text{not } A) \text{ plus } 1$	Twos complement of A
1	0	$F = A \text{ plus } B \text{ plus } 1$	Increment sum of A and B
1	1	$F = (\text{not } A) \text{ plus } B \text{ plus } 1$	B minus A

Logical and Arithmetic Operations

Not all operations appear useful, but "fall out" of internal logic

Arithmetic Logic Unit Design

Sample ALU

Traditional Design Approach

Truth Table & Espresso

23 product terms!

Equivalent to
25 gates

```
.i 6
.o 2
.ilb m s1 s0 ci ai bi
.ob fi co
.p 23
11110110
11011110
1-010010
1-111010
10010-10
10111-10
-1000110
010-0110
-1101110
011-1110
--100010
0-1-0010
--001010
0-0-1010
-0100-10
001-0-10
-0001-10
000-1-10
-1-1-101
--1-0101
--0-1101
--110-01
--011-01
.e
```




Contemporary Logic Design Arithmetic Circuits

M	S1	S0	Ci	Ai	Bi	Fi	Ci+1
0	0	0	X	0	X	0	X
			X	1	X	1	X
	0	1	X	0	X	1	X
			X	1	X	0	X
	1	0	X	0	0	0	X
			X	0	1	1	X
			X	1	0	1	X
			X	1	1	0	X
	1	1	X	0	0	1	X
			X	0	1	0	X
			X	1	0	0	X
			X	1	1	1	X
1	0	0	0	0	X	0	X
			0	1	X	1	X
	0	1	0	0	X	1	X
			0	1	X	0	X
	1	0	0	0	0	0	0
			0	0	1	1	0
			0	1	0	1	0
			0	1	1	0	1
	1	1	0	0	0	1	0
			0	0	1	0	1
			0	1	0	0	0
			0	1	1	1	0
1	0	0	1	0	X	1	0
			1	1	X	0	1
	0	1	1	0	X	0	1
			1	1	X	1	0
	1	0	1	0	0	1	0
			1	0	1	0	1
			1	1	0	0	1
			1	1	1	1	1
	1	1	1	0	0	0	1
			1	0	1	1	1
			1	1	0	1	0
			1	1	1	0	1

Sample ALU

Multilevel Implementation

   
```
.model aluespresso
.inputs m s1 s0 ci ai bi
.outputs fi co
.names m ci co [30][33][35] fi
110---1
-1-11-1
--01-11
--00-01
.names m ci [30][33] co
-1-111
--111
111-1
.names s0 ai [30]
011
101
.names m s1 bi [33]
1111
.names s1 bi [35]
0-1
-01
.end
```



12 Gates

Sample ALU

Clever Multi-level Logic Implementation

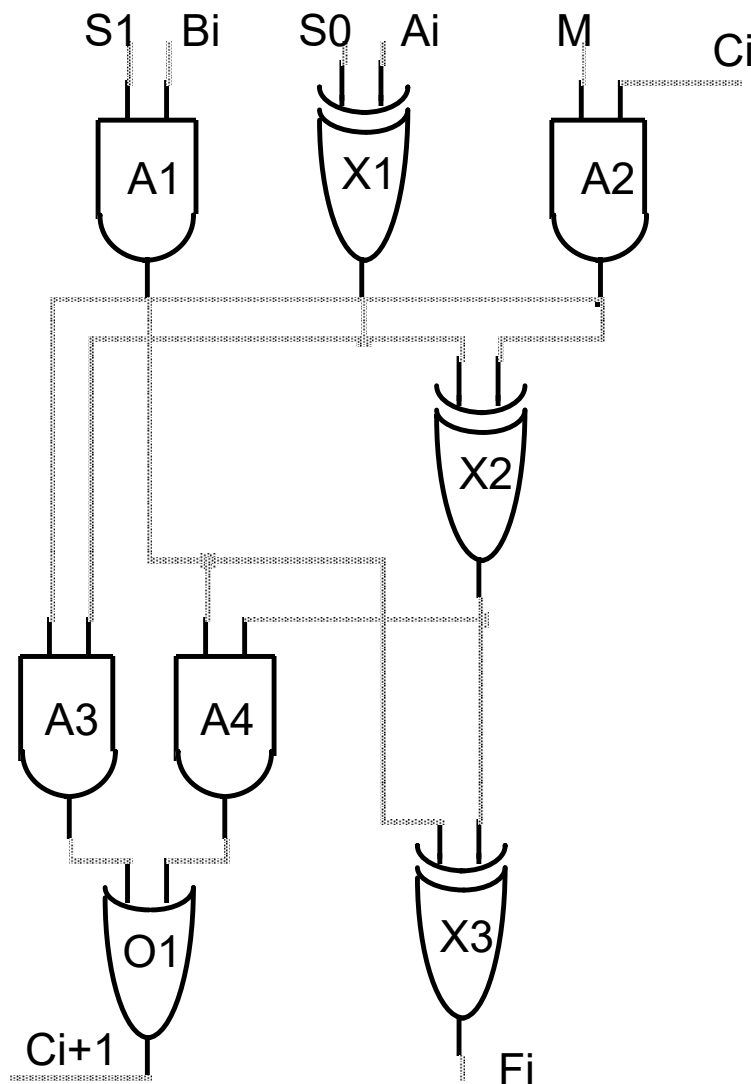

8 Gates (but 3 are XOR)

$S1 = 0$ blocks Bi
Happens when operations involve Ai only

Same is true for Ci when $M = 0$

Addition happens when $M = 1$

Bi , Ci to Xor gates X2, X3

$S0 = 0$, X1 passes A

$S0 = 1$, X1 passes \overline{A}

Arithmetic Mode:

Or gate inputs are Ai Ci and Bi (Ai xor Ci)

Logic Mode:

Cascaded XORs form output from Ai and Bi

Arithmetic Logic Unit Design

first-level gates

use S0 to complement Ai

S0 = 0 causes gate X1 to pass Ai

S0 = 1 causes gate X1 to pass Ai'

use S1 to block Bi

S1 = 0 causes gate A1 to make Bi go forward as 0
(don't want Bi for operations with just A)

S1 = 1 causes gate A1 to pass Bi

use M to block Ci

M = 0 causes gate A2 to make Ci go forward as 0
(don't want Ci for logical operations)

M = 1 causes gate A2 to pass Ci

other gates

for M=0 (logical operations, Ci is ignored)

$$F_i = S_1 B_i \text{ xor } (S_0 \text{ xor } A_i)$$

$$= S_1' S_0' (A_i) + S_1' S_0 (A_i') +$$

$$S_1 S_0' (A_i B_i' + A_i' B_i) + S_1 S_0 (A_i' B_i' + A_i B_i)$$

for M=1 (arithmetic operations)

$$F_i = S_1 B_i \text{ xor } ((S_0 \text{ xor } A_i) \text{ xor } C_i) =$$

$$C_{i+1} = C_i (S_0 \text{ xor } A_i) + S_1 B_i ((S_0 \text{ xor } A_i) \text{ xor } C_i) =$$

just a full adder with inputs S0 xor Ai, S1 Bi, and Ci

M	S1	S0	Ci	Ai	Bi	Fi	Ci+1
0	0	0	X	0	X	0	X
			X	1	X	1	X
	0	1	X	0	X	1	X
			X	1	X	0	X
	1	0	X	0	0	0	X
			X	0	1	1	X
			X	1	0	1	X
			X	1	1	0	X
	1	1	X	0	0	1	X
			X	0	1	0	X
			X	1	0	0	X
			X	1	1	1	X
1	0	0	0	0	X	0	X
			0	1	X	1	X
	0	1	0	0	X	1	X
			0	1	X	0	X
	1	0	0	0	0	0	0
			0	0	1	1	0
			0	1	0	1	0
			0	1	1	0	1
	1	1	0	0	0	1	0
			0	0	1	0	1
			0	1	0	0	0
			0	1	1	1	0
1	0	0	1	0	X	1	0
			1	1	X	0	1
	0	1	1	0	X	0	1
			1	1	X	1	0
	1	0	1	0	0	1	0
			1	0	1	0	1
			1	1	0	0	1
			1	1	1	1	1
	1	1	1	0	0	0	1
			1	0	1	1	1
			1	1	0	1	0
			1	1	1	0	1

Sample ALU – clever multi-level implementation

M = 0, Logical Bitwise Operations


S1	S0	Function	Comment
0	0	$F_i = A_i$	Input A_i transferred to output
0	1	$F_i = \text{not } A_i$	Complement of A_i transferred to output
1	0	$F_i = A_i \text{ xor } B_i$	Compute XOR of A_i, B_i
1	1	$F_i = A_i \text{ xnor } B_i$	Compute XNOR of A_i, B_i

M = 1, C0 = 0, Arithmetic Operations

0	0	$F = A$	Input A passed to output
0	1	$F = \text{not } A$	Complement of A passed to output
1	0	$F = A \text{ plus } B$	Sum of A and B
1	1	$F = (\text{not } A) \text{ plus } B$	Sum of B and complement of A

M = 1, C0 = 1, Arithmetic Operations

0	0	$F = A \text{ plus } 1$	Increment A
0	1	$F = (\text{not } A) \text{ plus } 1$	Twos complement of A
1	0	$F = A \text{ plus } B \text{ plus } 1$	Increment sum of A and B
1	1	$F = (\text{not } A) \text{ plus } B \text{ plus } 1$	B minus A

 

first-level gates

use S0 to complement A_i

$S_0 = 0$ causes gate X1 to pass A_i

$S_0 = 1$ causes gate X1 to pass A_i'

use S1 to block B_i

$S_1 = 0$ causes gate A1 to make B_i go forward as 0 (don't want B_i for operations with just A)

$S_1 = 1$ causes gate A1 to pass B_i

use M to block C_i

$M = 0$ causes gate A2 to make C_i go forward as 0 (don't want C_i for logical operations)

$M = 1$ causes gate A2 to pass C_i

other gates

for $M=0$ (logical operations, C_i is ignored)

$$F_i = S_1 B_i \text{ xor } (S_0 \text{ xor } A_i)$$

$$= S_1 S_0' (A_i) + S_1 S_0' (A_i') +$$

$$S_1 S_0' (A_i B_i' + A_i' B_i) + S_1 S_0 (A_i' B_i' + A_i B_i)$$

for $M=1$ (arithmetic operations)

$$F_i = S_1 B_i \text{ xor } ((S_0 \text{ xor } A_i) \text{ xor } C_i) =$$

$$C_{i+1} = C_i (S_0 \text{ xor } A_i) + S_1 B_i ((S_0 \text{ xor } A_i) \text{ xor } C_i) =$$


just a full adder with inputs $S_0 \text{ xor } A_i$, $S_1 B_i$, and C_i

74181 TTL ALU

Selection				M = 1	M = 0, Arithmetic Functions	
S3	S2	S1	S0	Logic Function	Cn = 0	Cn = 1
0	0	0	0	$F = \text{not } A$	$F = A \text{ minus } 1$	$F = A$
0	0	0	1	$F = A \text{ nand } B$	$F = A B \text{ minus } 1$	$F = A B$
0	0	1	0	$F = (\text{not } A) + B$	$F = A (\text{not } B) \text{ minus } 1$	$F = A (\text{not } B)$
0	0	1	1	$F = 1$	$F = \text{minus } 1$	$F = \text{zero}$
0	1	0	0	$F = A \text{ nor } B$	$F = A \text{ plus } (A + \text{not } B)$	$F = A \text{ plus } (A + \text{not } B) \text{ plus } 1$
0	1	0	1	$F = \text{not } B$	$F = A B \text{ plus } (A + \text{not } B)$	$F = A B \text{ plus } (A + \text{not } B) \text{ plus } 1$
0	1	1	0	$F = A \text{ xnor } B$	$F = A \text{ minus } B \text{ minus } 1$	$F = (A + \text{not } B) \text{ plus } 1$
0	1	1	1	$F = A + \text{not } B$	$F = A + \text{not } B$	$F = A \text{ minus } B$
1	0	0	0	$F = (\text{not } A) B$	$F = A \text{ plus } (A + B)$	$F = (A + \text{not } B) \text{ plus } 1$
1	0	0	1	$F = A \text{ xor } B$	$F = A \text{ plus } B$	$F = A \text{ plus } (A + B) \text{ plus } 1$
1	0	1	0	$F = B$	$F = A (\text{not } B) \text{ plus } (A + B)$	$F = A (\text{not } B) \text{ plus } (A + B) \text{ plus } 1$
1	0	1	1	$F = A + B$	$F = (A + B)$	$F = (A + B) \text{ plus } 1$
1	1	0	0	$F = 0$	$F = A$	$F = A \text{ plus } A \text{ plus } 1$
1	1	0	1	$F = A (\text{not } B)$	$F = A B \text{ plus } A$	$F = A B \text{ plus } A \text{ plus } 1$
1	1	1	0	$F = A B$	$F = A (\text{not } B) \text{ plus } A$	$F = A (\text{not } B) \text{ plus } A \text{ plus } 1$
1	1	1	1	$F = A$	$F = A$	$F = A \text{ plus } 1$


74181 TTL ALU

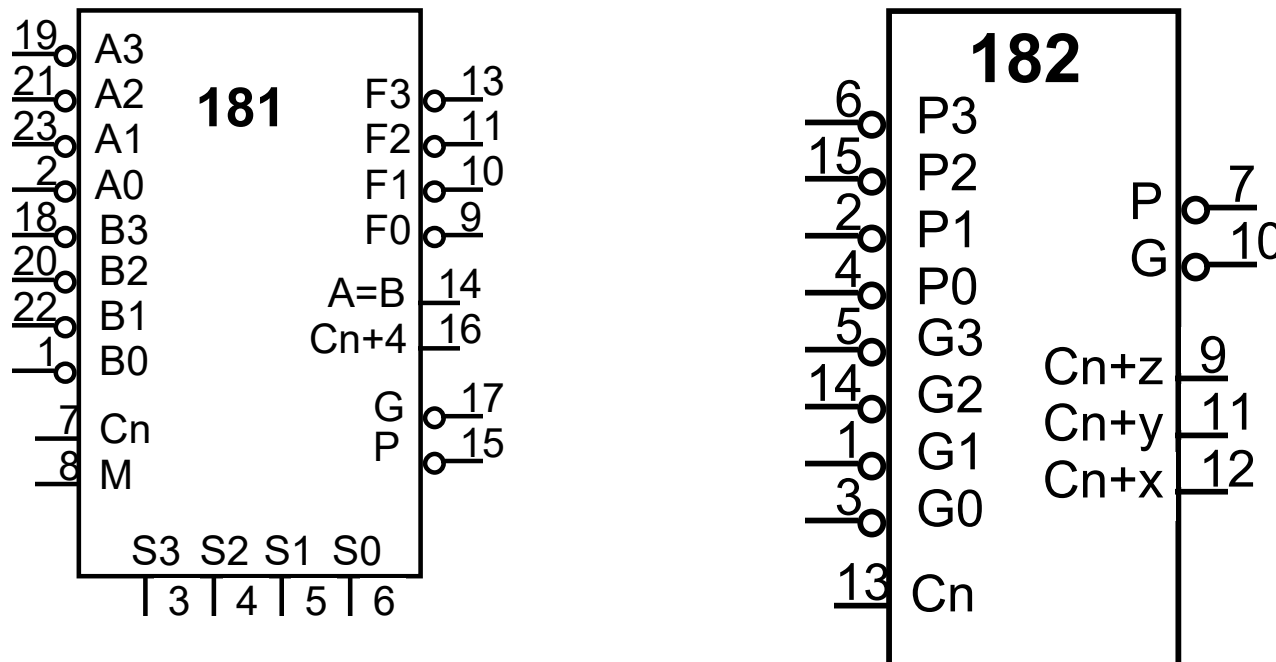Note that the sense of the carry in and out are
OPPOSITE from the input bits



Fortunately, carry lookahead generator
maintains the correct sense of the signals

16-bit ALU with Carry Lookahead

 

BCD Addition

BCD Number Representation

Decimal digits 0 thru 9 represented as 0000 thru 1001 in binary

Addition:

$$5 = 0101$$

$$3 = \underline{0011}$$

$$1000 = 8$$

$$5 = 0101$$

$$8 = \underline{1000}$$

$$1101 = 13!$$

**Problem
when digit
sum exceeds 9**

Solution: add 6 (0110) if sum exceeds 9!

$$5 = 0101$$

$$8 = \underline{1000}$$

$$1101$$

$$6 = \underline{0110}$$

$$1\ 0011 = 13 \text{ in BCD}$$

$$9 = 1001$$


$$7 = \underline{0111}$$

$$1\ 0000 = 16 \text{ in binary}$$

$$6 = \underline{0110}$$

$$1\ 0110 = 16 \text{ in BCD}$$

Adder Design

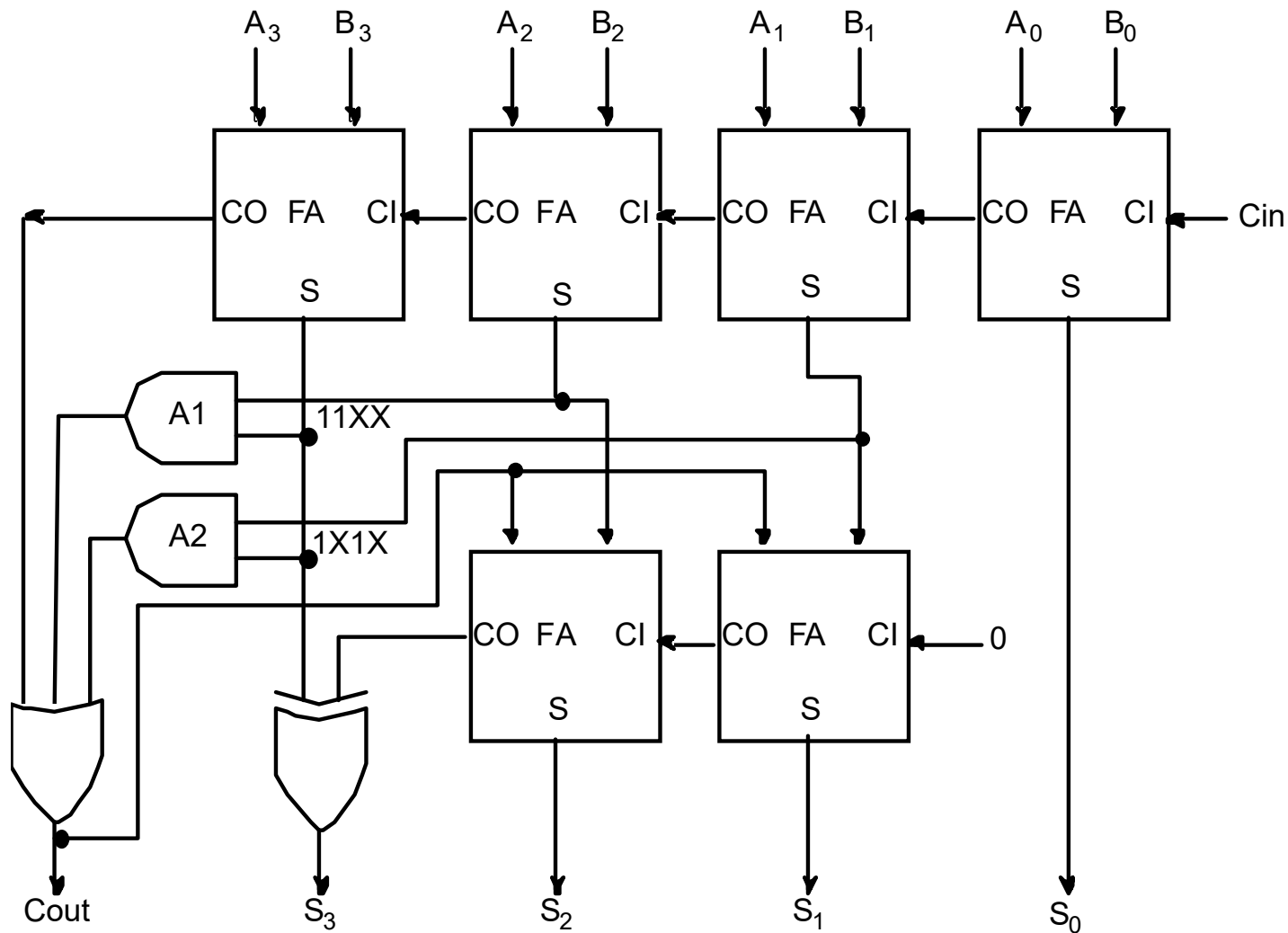

Add 0110 to sum whenever it exceeds 1001 (11XX or 1X1X)

Combinational Multiplier

Basic Concept

multiplicand 1101 (13)

multiplier * 1011 (11)

Partial products

1101

1101

0000

1101

10001111 (143)


product of 2 4-bit numbers
is an 8-bit number

Combinational Multiplier

Partial Product Accumulation

				A3	A2	A1	A0
				B3	B2	B1	B0
				A3 B0	A2 B0	A1 B0	A0 B0
			A3 B1	A2 B1	A1 B1	A0 B1	
		A3 B2	A2 B2	A1 B2	A0 B2		
A3 B3	A2 B3	A1 B3	A0 B3				
S7	S6	S5	S4	S3	S2	S1	S0

Partial Product Accumulation

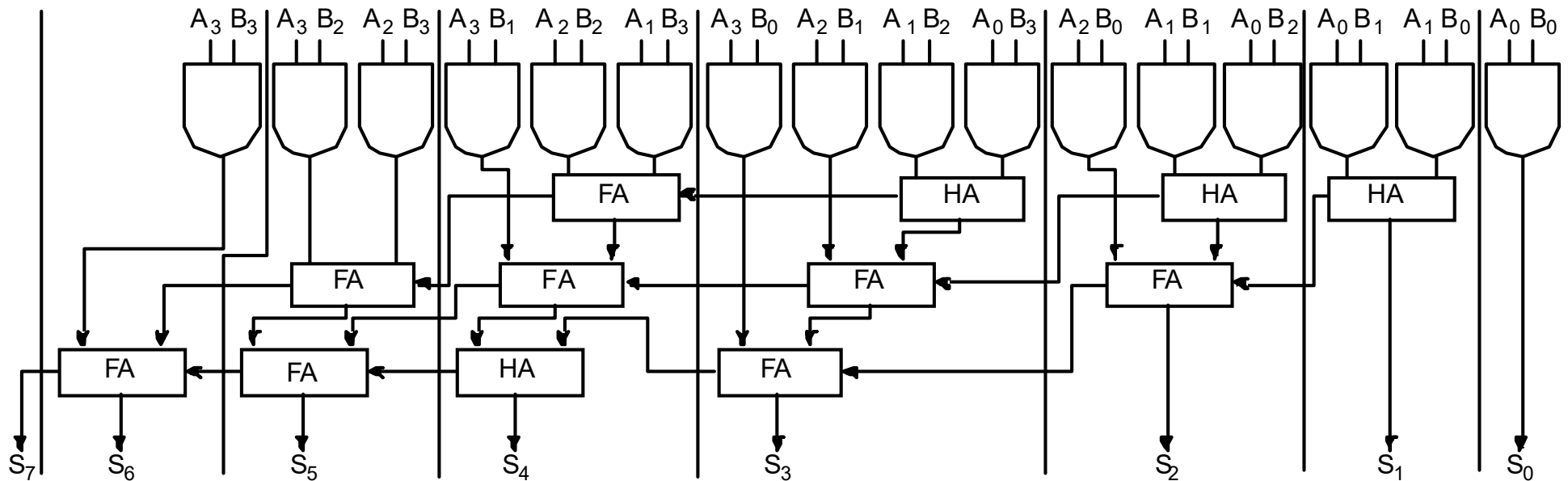

Note use of parallel carry-outs to form higher order sums

12 Adders, if full adders, this is 6 gates each = 72 gates


16 gates form the partial products

total = 88 gates!

Combinational Multiplier


Another Representation of the Circuit

Building block: full adder + and

 


Partial Product Accumulation

				A3	A2	A1	A0
				B3	B2	B1	B0
				A2 B0	A2 B0	A1 B0	A0 B0
A3 B1				A2 B1	A1 B1	A0 B1	
A3 B2				A2 B2	A1 B2	A0 B2	
A3 B3	A2 B3	A1 B3	A0 B3				
S7	S6	S5	S4	S3	S2	S1	S0

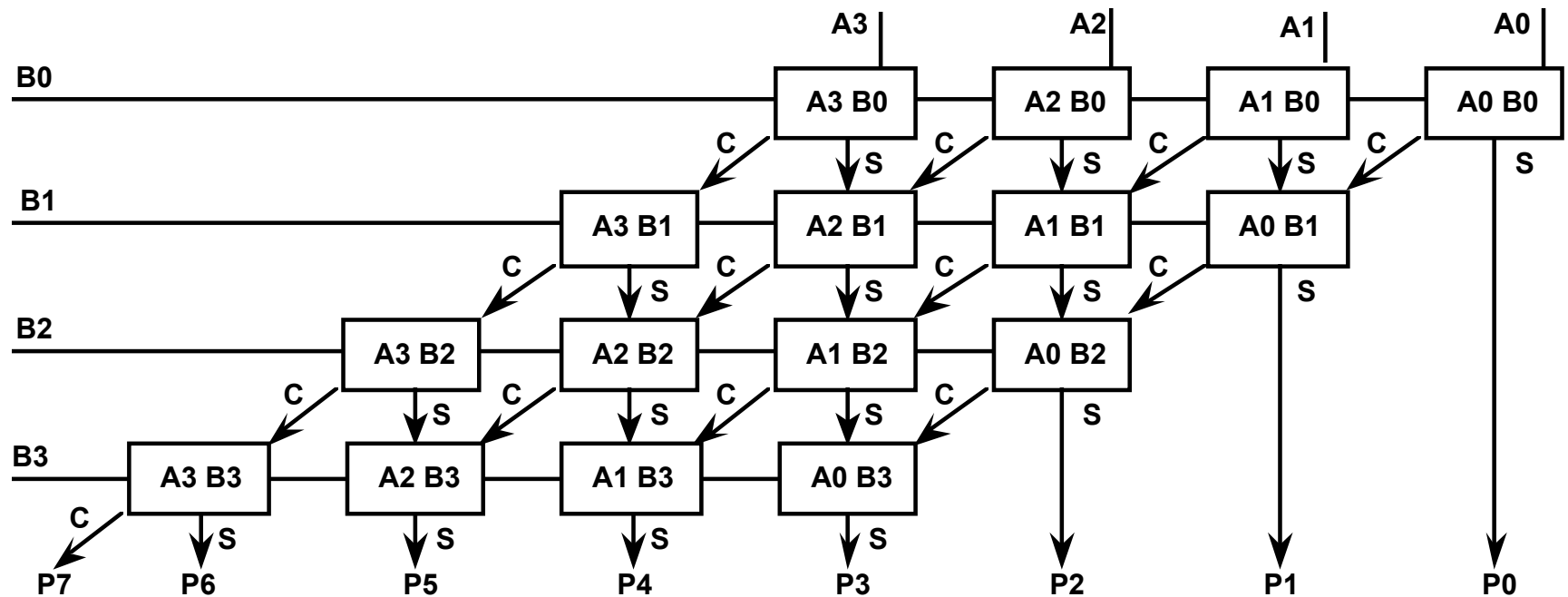


4 x 4 array of building blocks

 

(a) Basic building block

Partial Product Accumulation


A3	A2	A1	A0
B3	B2	B1	B0
A3 B0	A2 B0	A1 B0	A0 B0
A3 B1	A2 B1	A1 B1	A0 B1
A3 B2	A2 B2	A1 B2	A0 B2
A3 B3	A2 B3	A1 B3	A0 B3

 

(b) 4 × 4 combinational multiplier

Case Study: 8 x 8 Multiplier

TTL Multipliers

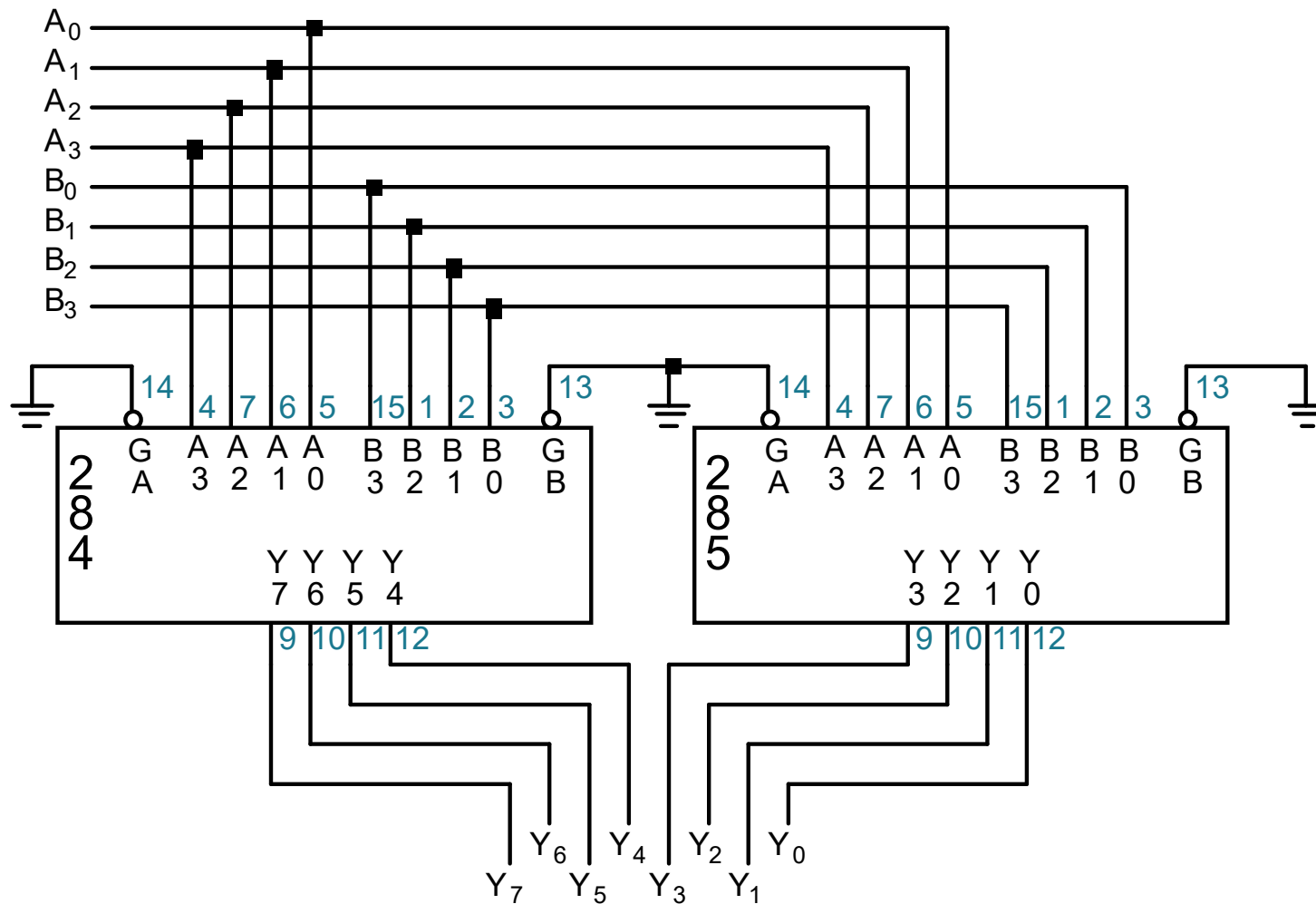


Two chip implementation of 4 x 4 multiplier

Case Study: 8 x 8 Multiplier

 Problem Decomposition

How to implement 8 x 8 multiply in terms of 4 x 4 multiplies?



$$\begin{array}{r}
 1111 \ 0010 \\
 * \ 1000 \ 1100 \\
 \hline
 0001 \ 1000 \\
 1011 \ 0100 \\
 0001 \ 0000 \\
 0111 \ 1000 \\
 \hline
 1000 \ 0100 \ 0101 \ 1000
 \end{array}$$

= PP0
= PP1
= PP2
= PP3

= 0010 * 1100
= 1111 * 1100
= 0010 * 1000
= 1111 * 1000

P15-12 P11-8 P7-4 P3-0

$$P_{3-0} = PP_{0 \ 3-0}$$


$$P_{7-4} = PP_{0 \ 3-0} + PP_{1 \ 3-0} + PP_{2 \ 3-0} + \text{Carry-in}$$

$$P_{11-8} = PP_{1 \ 7-4} + PP_{2 \ 7-4} + PP_{3 \ 3-0} + \text{Carry-in}$$

$$P_{15-12} = PP_{3 \ 7-4} + \text{Carry-in}$$

Case Study: 8 x 8 Multiplier

Calculation of Partial Products

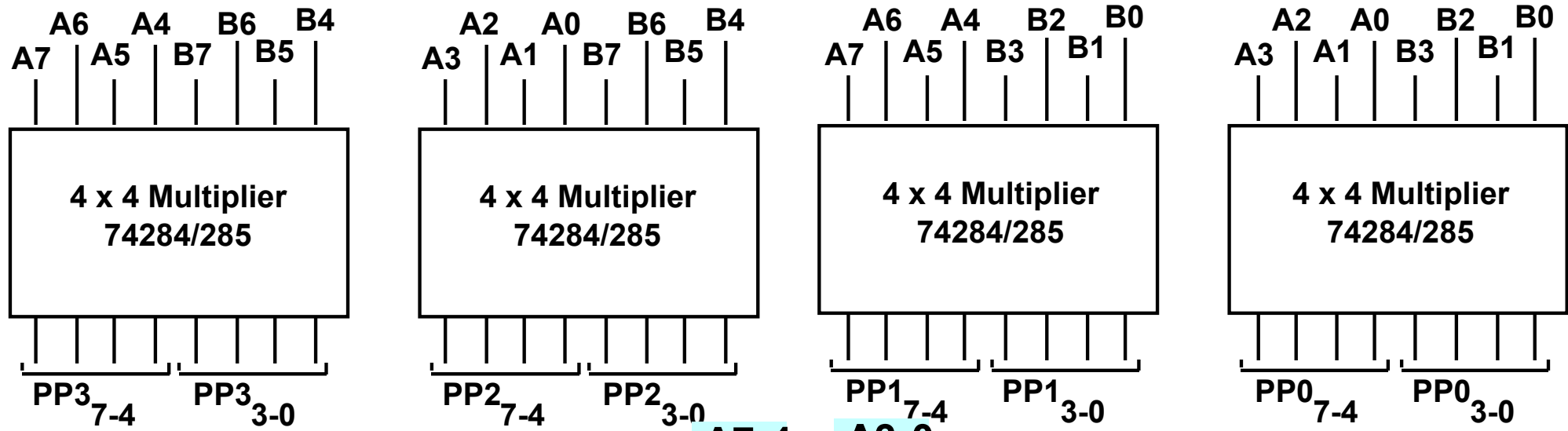

Use 4 74284/285 pairs to create 4 partial products

A7-4 * B7-4
A3-0 * B3-0

8 bit products

A3-0 * B3-0

= PP0

A7-4 * B3-0

= PP1



A3-0 * B7-4

= PP2

A7-4 * B7-4


= PP3

P15-12 P11-8 P7-4 P3-0

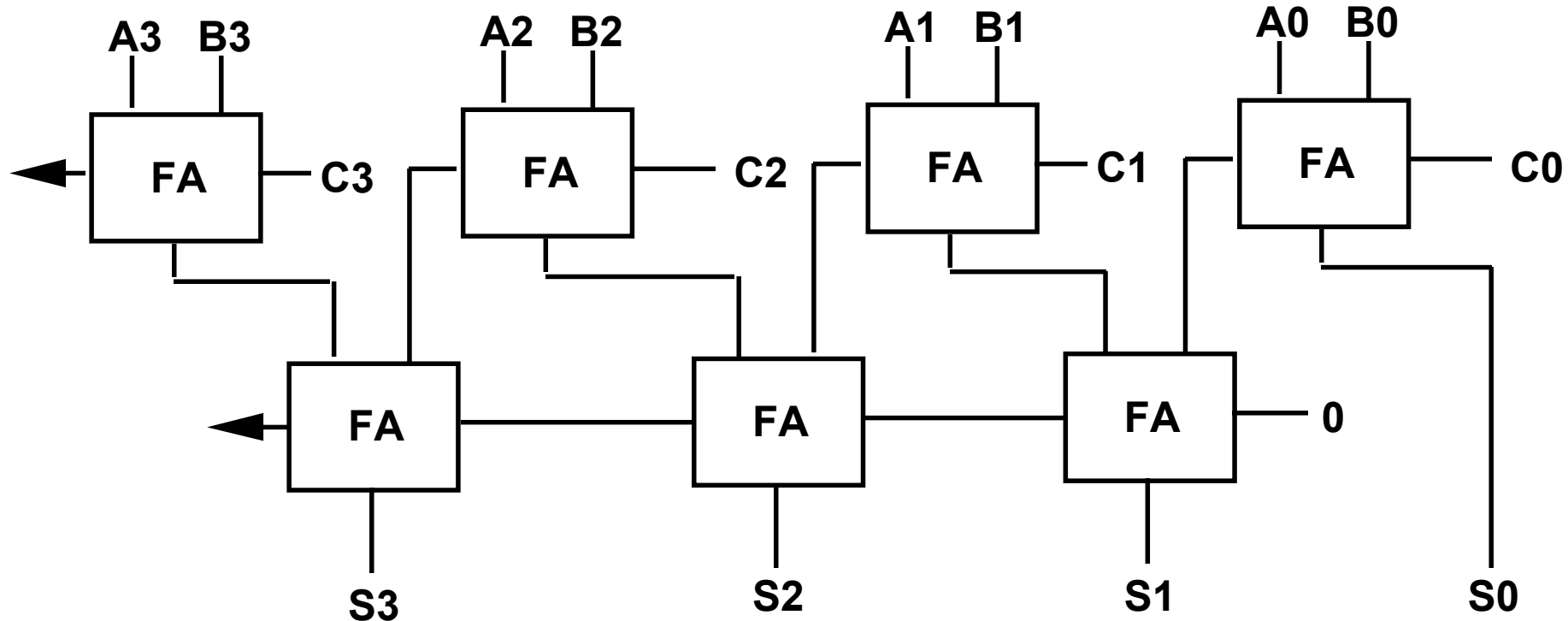 Case Study: 8 x 8 Multiplier***Three-At-A-Time Adder*****Clever use of the Carry Inputs****Sum $A[3-0]$, $B[3-0]$, $C[3-0]$:****Two Level Full Adder Circuit****Note: Carry lookahead schemes also possible!**

Case Study: 8 x 8 Multiplier

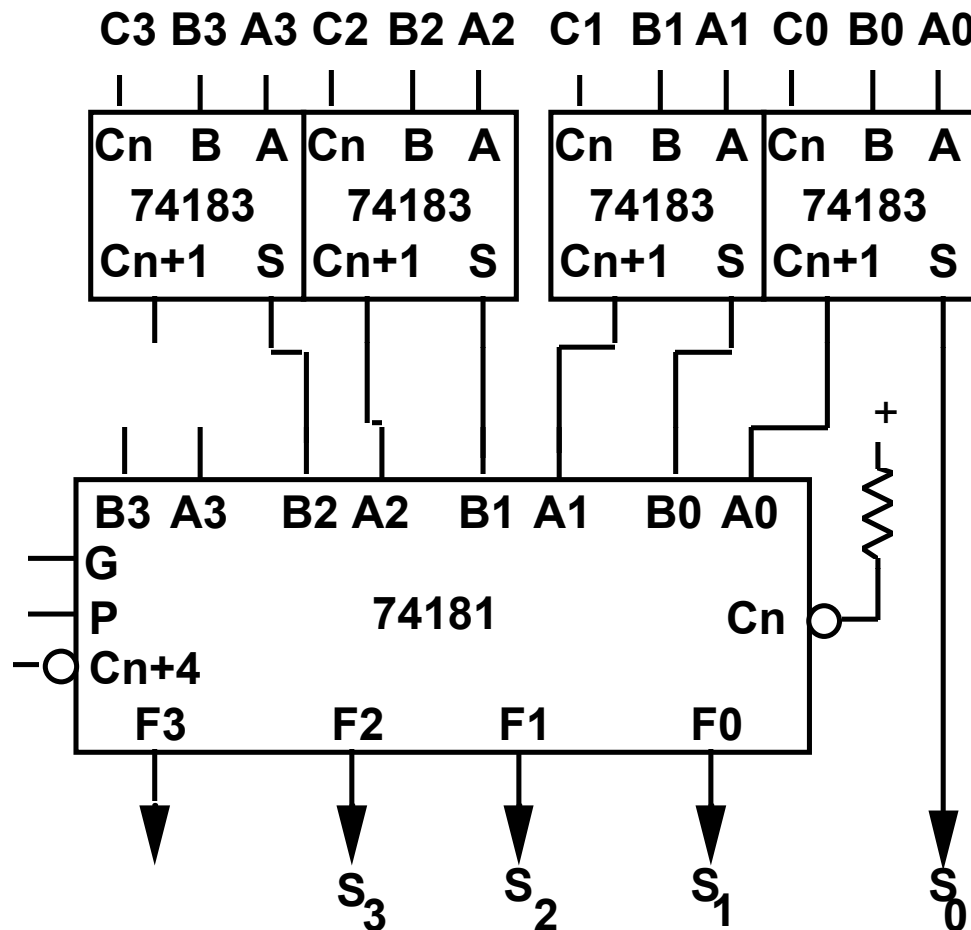
Three-At-A-Time Adder with TTL Components



Full Adders
(2 per package)



**Standard ALU configured as 4-bit
cascaded adder**
(with internal carry lookahead)

Note the off-set in the outputs

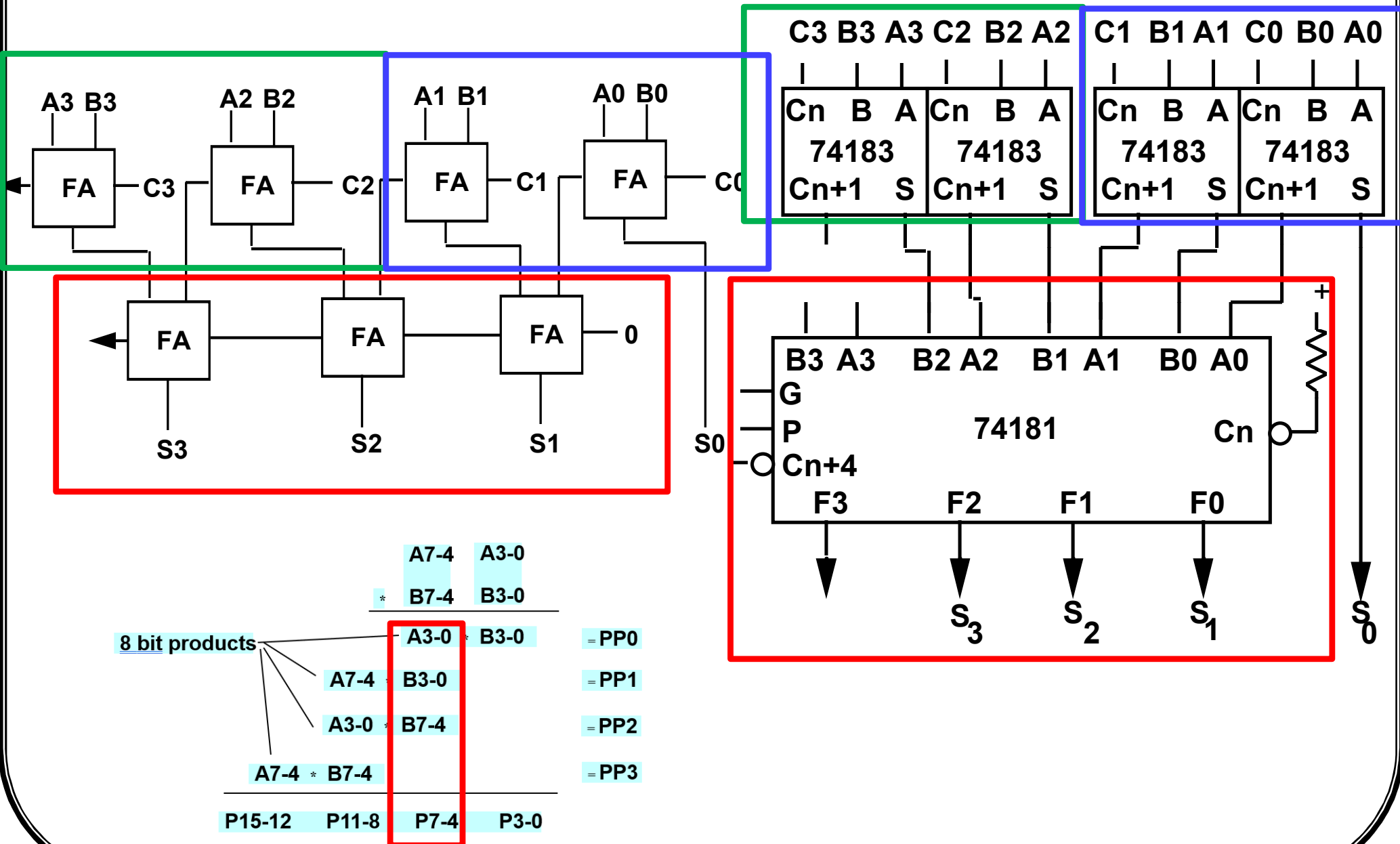

Case Study: 8 x 8 Multiplier

Accumulation of Partial Products

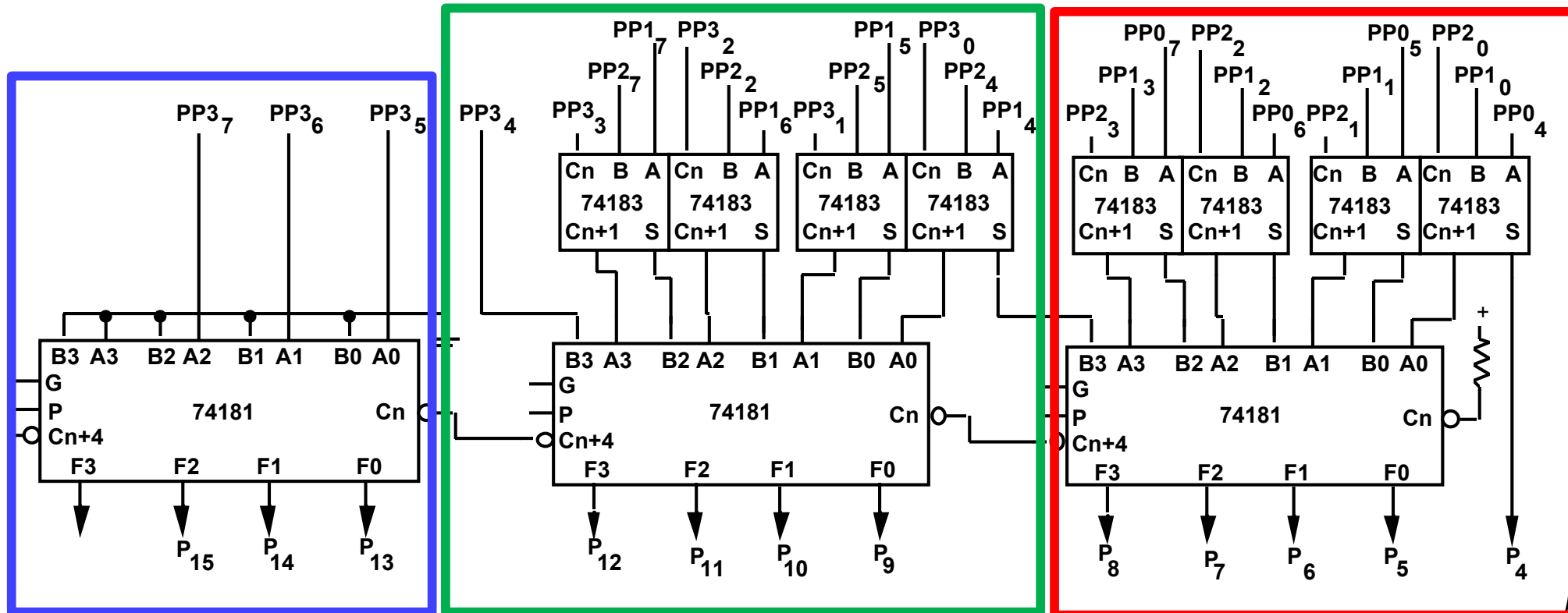 

Just a case of cascaded three-at-a-time adders!

The Complete System



Case Study: 8 x 8 Multiplier

Package Count and Performance

4 74284/74285 pairs = 8 packages
4 74183, 3 74181, 1 74182 = 8 packages
16 packages total

Partial product calculation (74284/285) = 40 ns typ, 60 ns max

Intermediate sums (74183) = 9 ns/20ns = 15 ns average, 33 ns max

Second stage sums w/carry lookahead

74LS181: carry G and P = 20 ns typ, 30 ns max

74182: second level carries = 13 ns typ, 22 ns max

74LS181: formations of sums = 15 ns typ, 26 ns max

103 ns typ, 171 ns max

Chapter Review

We have covered:

- ***Binary Number Representation***
positive numbers the same
difference is in how negative numbers are represented
twos complement easiest to handle:
one representation for zero, slightly
complicated complementation, simple addition
- ***Binary Networks for Additions***
basic HA, FA
carry lookahead logic
- ***ALU Design***
specification and implementation
- ***BCD Adders***
Simple extension of binary adders
- ***Multipliers***
4 x 4 multiplier: partial product accumulation
extension to 8 x 8 case